

# Principles of Engineering Sciences

Dept. of Mechanical-Mechatronics Engineering

Type: UG core

Branch: All

Semester: 3<sup>rd</sup>

Instructor: Shanker Ganesh R

Room no: 2135, 2688003

[rshankerganesh@lnmiit.ac.in](mailto:rshankerganesh@lnmiit.ac.in)


## Syllabus:

- Three phase systems: Generation of three phase voltages- advantages of three phase systems, star and delta connection, 3 wire and four wire systems, relation between line and phase voltages & currents.
- Transformers: construction, types, emf equation, losses and efficiency
- DC Machines: DC generator- construction, types, emf equation, D.C motor- types, characteristics, applications.
- AC machines: Three phase induction motor, single phase induction motor, three-phase alternator- construction, principle of operation, characteristics, methods of starting.

## Text Books



1. Thereja B. L., *Fundamentals of Electrical Engineering and Electronics –I*, S. Chand & Co, New Delhi, 2012.
2. Chakrabarti A., et.al, *Basic Electrical Engineering*, TMH, 2012.
3. Hughes, *Electrical and Electronic Technology*, Pearson Education South Asia, 2011

# Single-Phase signal

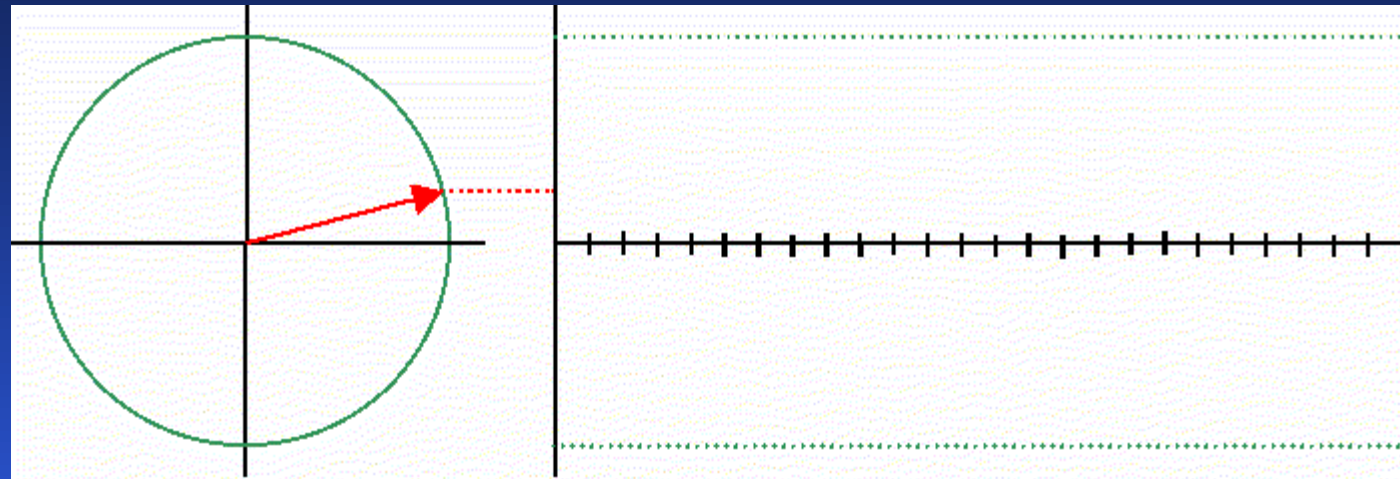

Rotating Phasor


Single phase signal

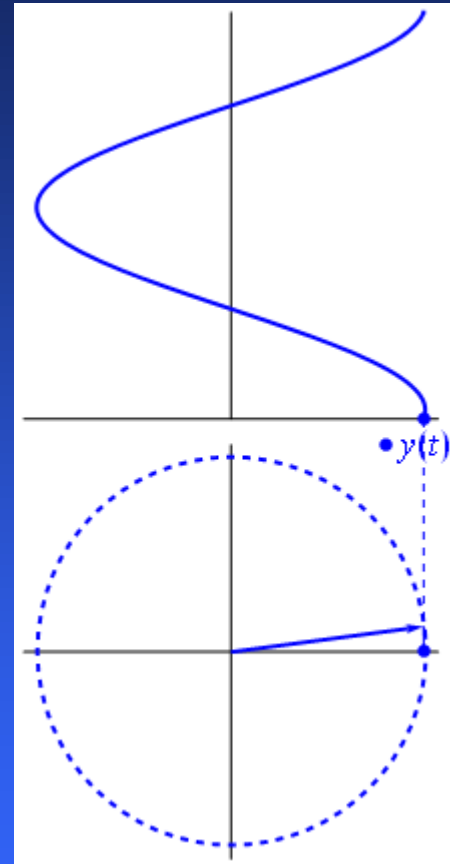
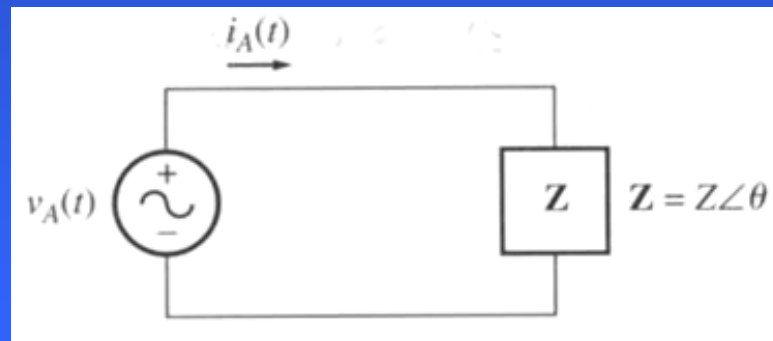


# Generating three-phase

## Applying constraints

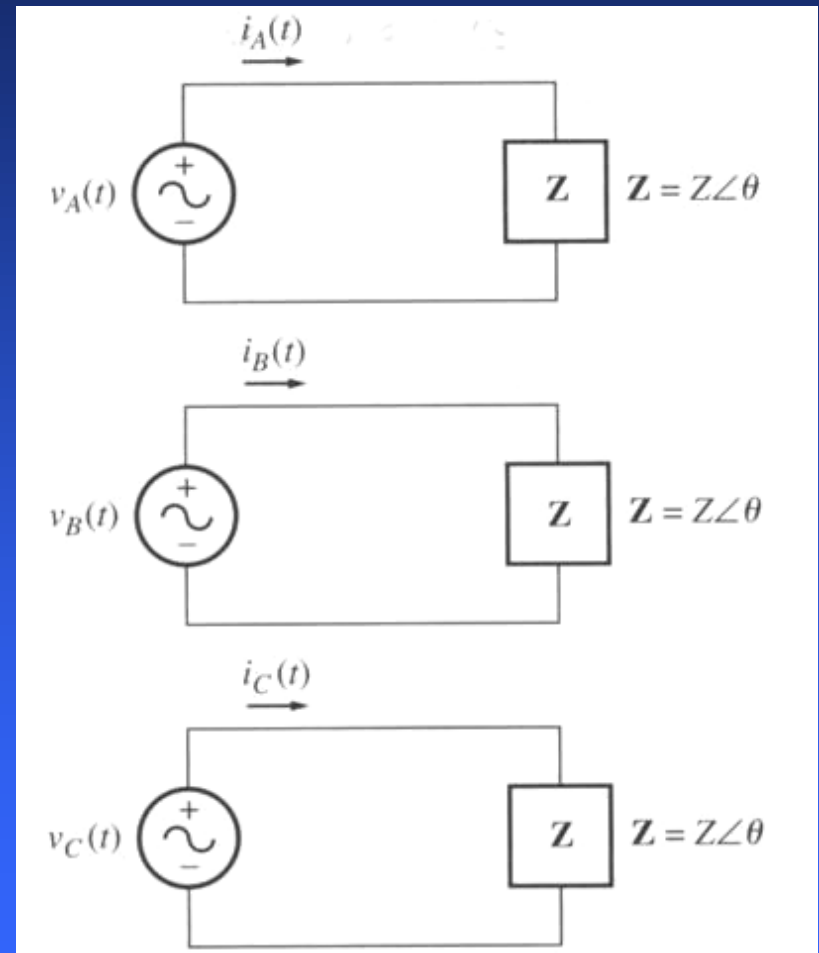1. Amplitude of  $v_A$   $v_B$   $v_C$  are equal.
2. The voltages have a  $120^\circ$  phase difference between each other.
3. Connect identical loads to each supply.



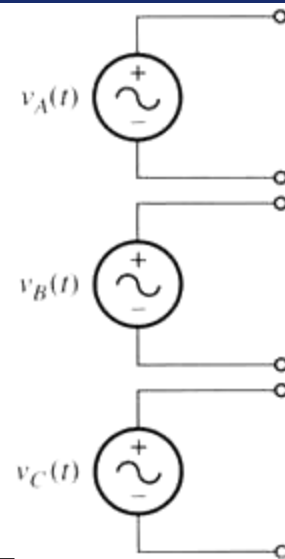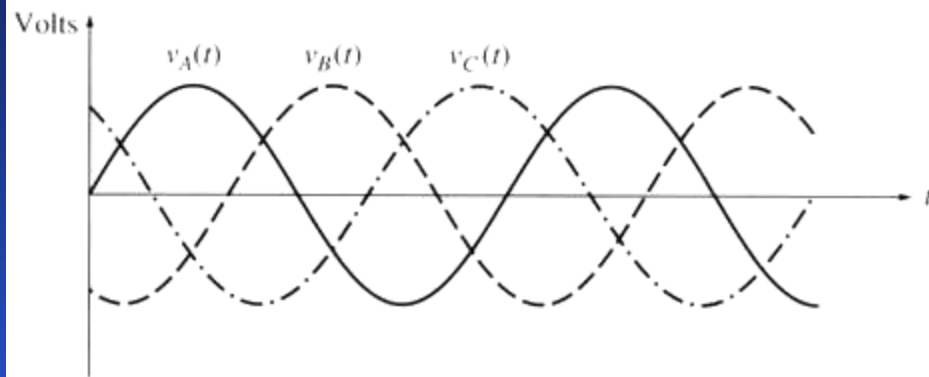

$$v_A(t) = \sqrt{2} V \sin \omega t \text{ V}$$


$$\mathbf{V}_A = V \angle 0^\circ \text{ V}$$

$$v_B(t) = \sqrt{2} V \sin (\omega t - 120^\circ) \text{ V}$$



$$\mathbf{V}_B = V \angle -120^\circ \text{ V}$$

$$v_C(t) = \sqrt{2} V \sin (\omega t - 240^\circ) \text{ V}$$
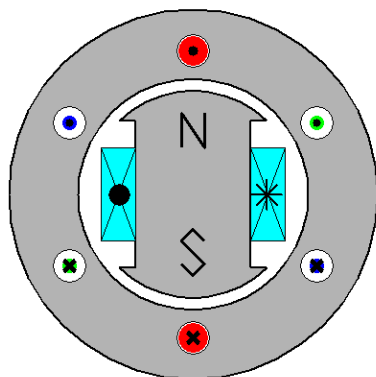
$$\mathbf{V}_C = V \angle -240^\circ \text{ V}$$



Phase A      Phase B      Phase C

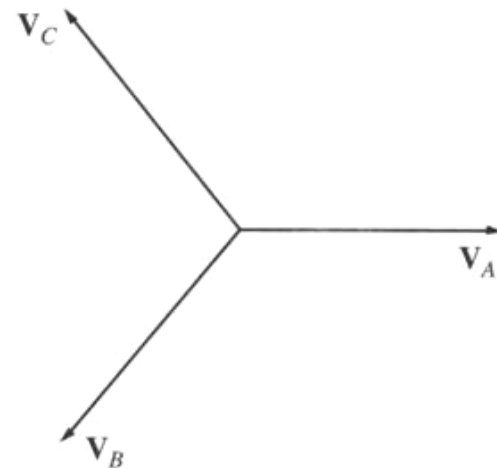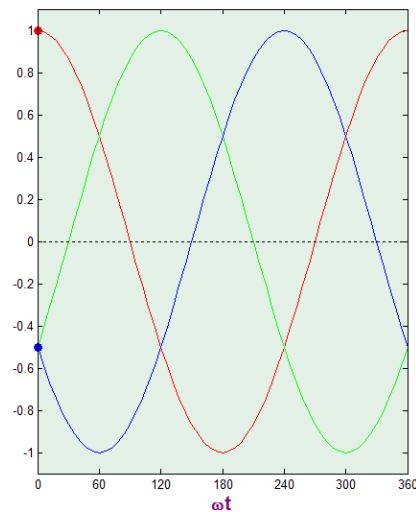


The current flowing to each load can be found as  $I = V/Z$

$$I_A = \frac{V \angle 0^\circ}{Z \angle \theta} = I \angle -\theta$$

$$I_B = \frac{V \angle -120^\circ}{Z \angle \theta} = I \angle -120 - \theta$$

$$I_C = \frac{V \angle -240^\circ}{Z \angle \theta} = I \angle -240 - \theta$$

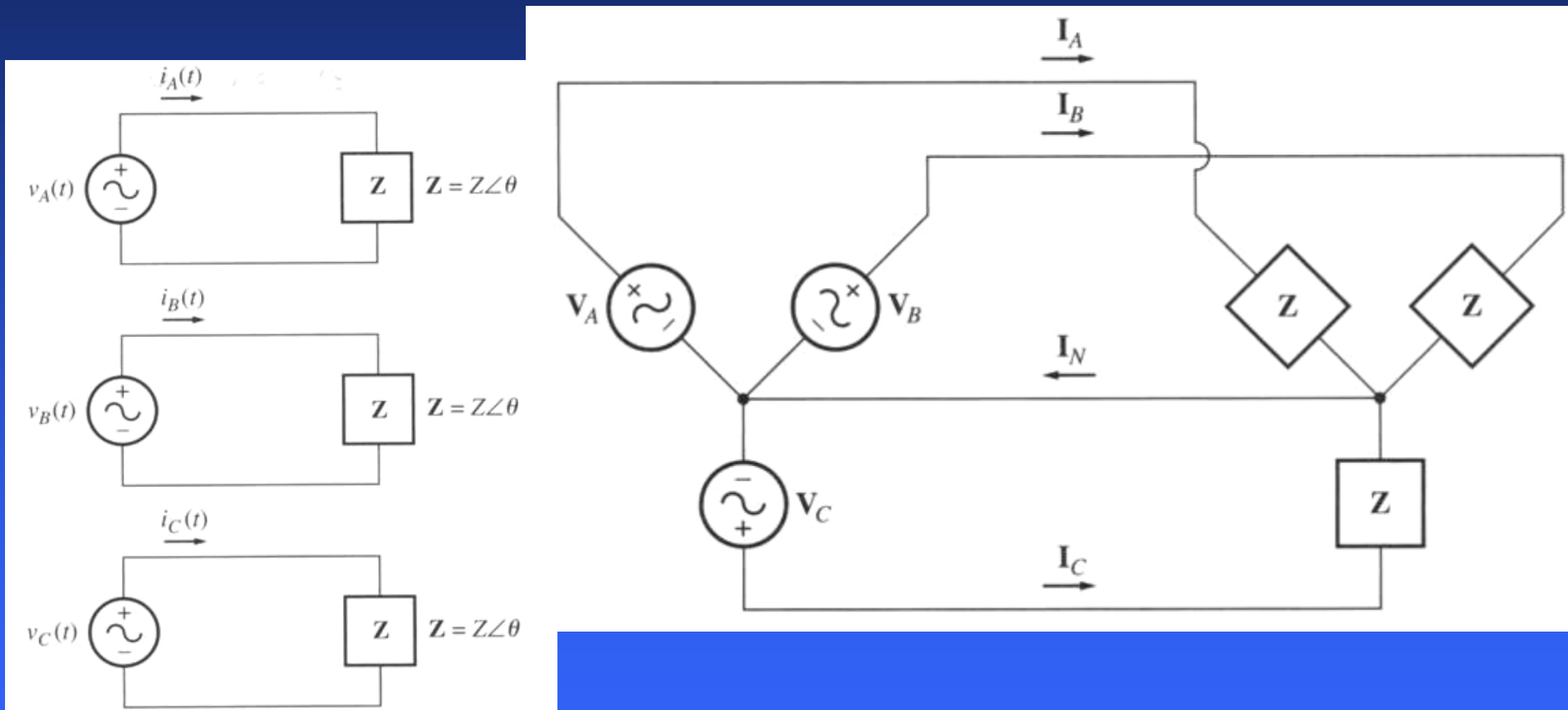Connect the grounds together using a single wire so the 3 circuits will have a single return path.



Therefore,  $I_N = I_A + I_B + I_C$

$I_N = ?$



$$\begin{aligned}
I_N &= I_A + I_B + I_C = I \angle -\theta + I \angle -\theta - 120^\circ + I \angle -\theta - 240^\circ \\
&= I \cos(-\theta) + jI \sin(-\theta) + I \cos(-\theta - 120^\circ) + jI \sin(-\theta - 120^\circ) + I \cos(-\theta - 240^\circ) + jI \sin(-\theta - 240^\circ) \\
&= I \left[ \cos(-\theta) + \cos(-\theta - 120^\circ) + \cos(-\theta - 240^\circ) \right] + jI \left[ \sin(-\theta) + \sin(-\theta - 120^\circ) + \sin(-\theta - 240^\circ) \right] \\
&= I \left[ \cos(-\theta) + \cos(-\theta) \cos(120^\circ) + \sin(-\theta) \sin(120^\circ) + \cos(-\theta) \cos(240^\circ) + \sin(-\theta) \sin(240^\circ) \right] \\
&\quad + jI \left[ \sin(-\theta) + \sin(-\theta) \cos(120^\circ) - \cos(-\theta) \sin(120^\circ) + \sin(-\theta) \cos(240^\circ) - \cos(-\theta) \sin(240^\circ) \right]
\end{aligned}$$

$$\begin{aligned}
I_N &= I \left[ \cos(-\theta) - \frac{1}{2} \cos(-\theta) + \frac{\sqrt{3}}{2} \sin(-\theta) - \frac{1}{2} \cos(-\theta) - \frac{\sqrt{3}}{2} \sin(-\theta) \right] \\
&\quad + jI \left[ \sin(-\theta) - \frac{1}{2} \sin(-\theta) + \frac{\sqrt{3}}{2} \cos(-\theta) - \frac{1}{2} \sin(-\theta) - \frac{\sqrt{3}}{2} \cos(-\theta) \right] \\
&= 0
\end{aligned}$$

The current through the neutral line can be found as zero as long as the load is balanced.


Therefore is the neutral line necessary?

In a balanced system, neutral is unnecessary!
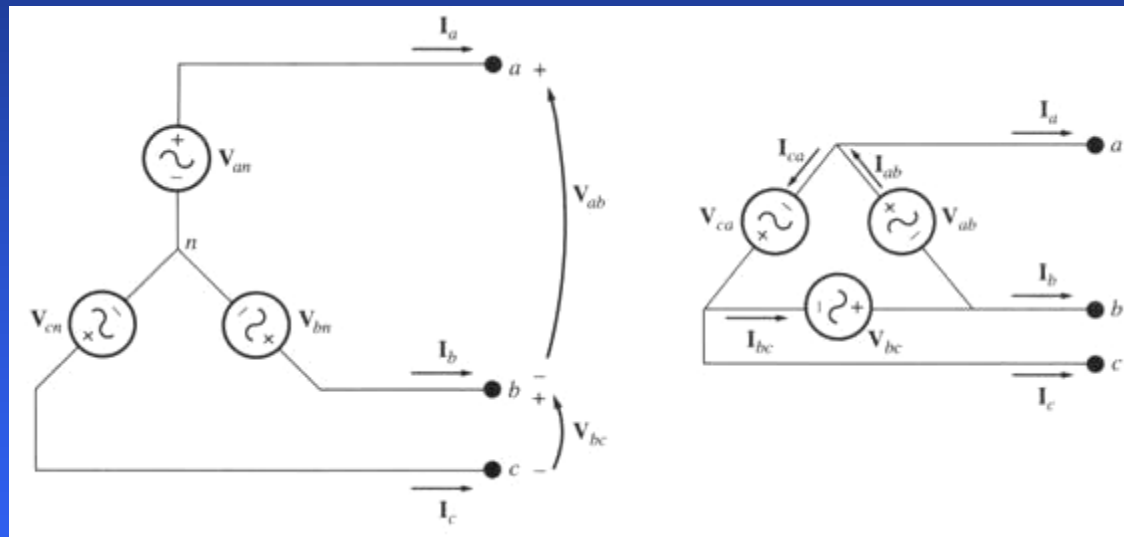
# Definitions

- Represented as  $3\Phi$
- 4 wires
  - 3 “active” phases, A(R), B(Y), C(B)
  - 1 “ground”, or “neutral”
- Color Code
  - Phase A      Red
  - Phase B      Yellow
  - Phase C      Blue
  - Neutral      Black
- Phase sequence(RYB) – order of phases in which individual voltages peak.

- There are two types of connections in three-phase circuits: Y (star) and  $\Delta$  (delta)




Phase quantities - voltages and currents in a given phase.

Line quantities – voltages between the lines and currents in the lines connected to the generators.

# Voltages and currents

## 1. Y-connection

Assuming a  
resistive  
load...

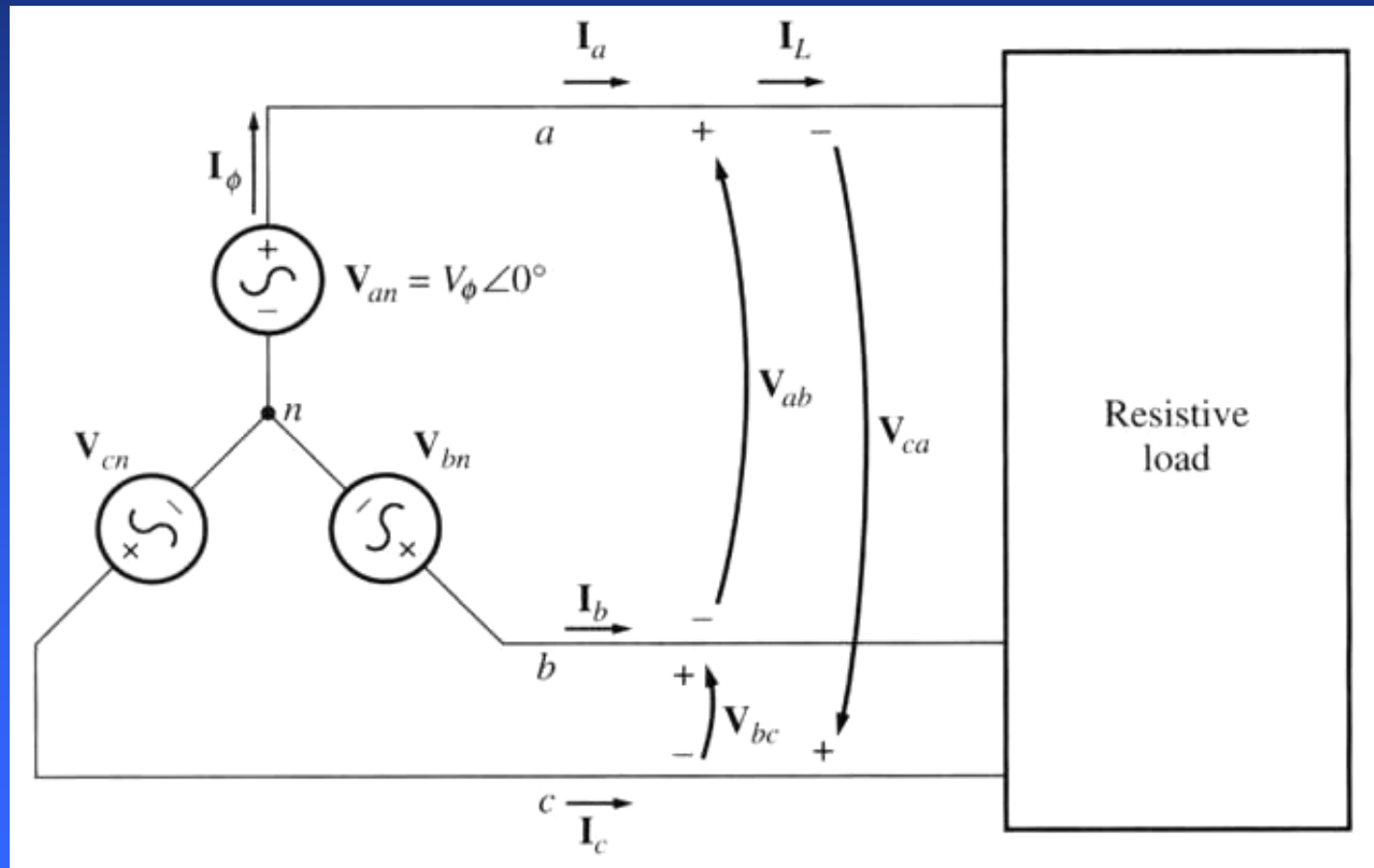

# Voltages and currents

## 1. Y-connection (cont)

$$V_{an} = V_{\phi} \angle 0^{\circ}$$

$$V_{bn} = V_{\phi} \angle -120^{\circ}$$

$$V_{cn} = V_{\phi} \angle -240^{\circ}$$

Since we assume a resistive load:

$$I_a = I_{\phi} \angle 0^{\circ}$$

$$I_b = I_{\phi} \angle -120^{\circ}$$

$$I_c = I_{\phi} \angle -240^{\circ}$$

## 1. Y-connection (cont 2)

The current in any line is the same as the current in the corresponding phase.

$$I_L = I_\phi$$

Voltages are:

$$\begin{aligned} V_{ab} &= V_a - V_b = V_\phi \angle 0^\circ - V_\phi \angle -120^\circ = V_\phi - \left( -\frac{1}{2}V_\phi - j\frac{\sqrt{3}}{2}V_\phi \right) = \frac{3}{2}V_\phi + j\frac{\sqrt{3}}{2}V_\phi \\ &= \sqrt{3}V_\phi \left( \frac{\sqrt{3}}{2} + j\frac{1}{2} \right) = \sqrt{3}V_\phi \angle 30^\circ \end{aligned}$$

# Voltages and currents


## 1. Y-connection (cont 3)

Magnitudes of the line-to-line voltages and the line-to-neutral voltages are related as:

$$V_{LL} = \sqrt{3}V_{\phi}$$

In addition, the line voltages are shifted by  $30^\circ$  with respect to the phase voltages.

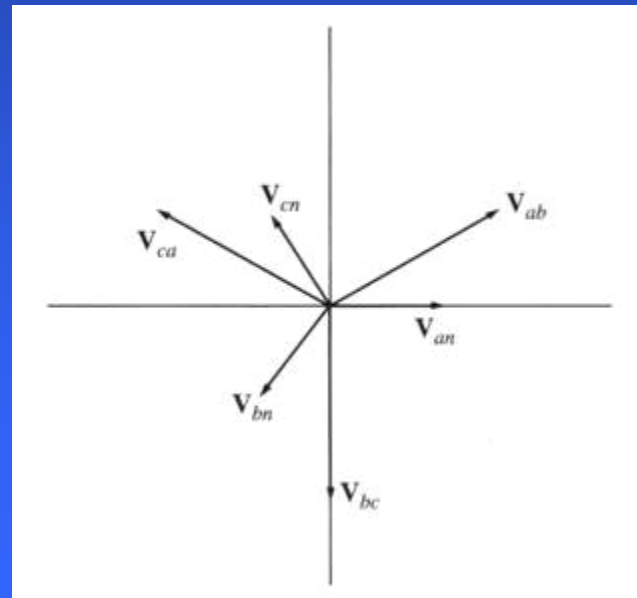In a connection with *abc* sequence, the voltage of a line leads the phase voltage.






# Voltages and currents

## 1. $\Delta$ -connection

assuming a  
resistive load:

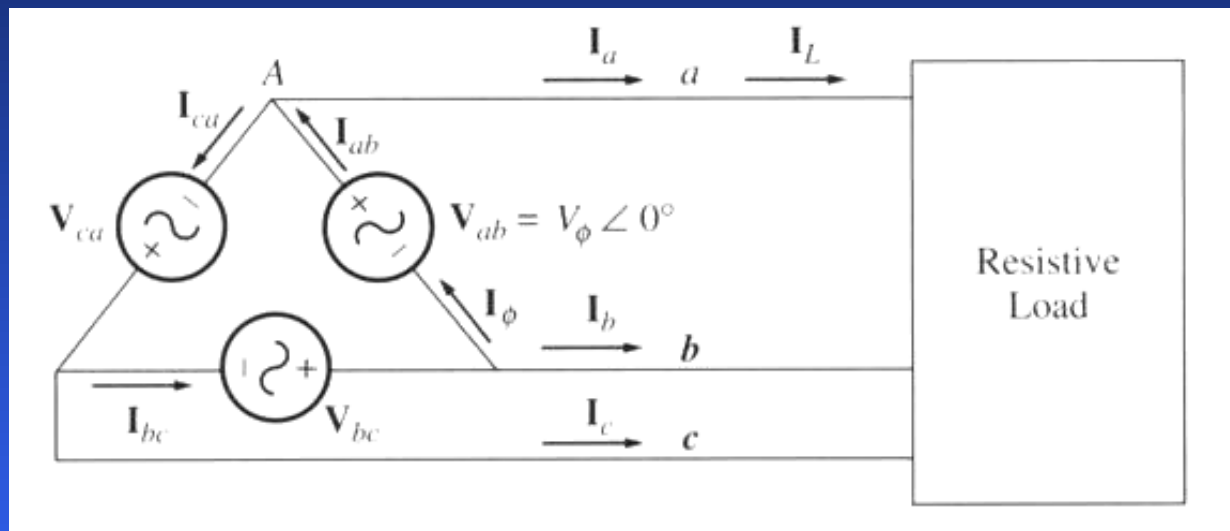

$$V_{ab} = V_\phi \angle 0^\circ$$

$$V_{bc} = V_\phi \angle -120^\circ$$

$$V_{ca} = V_\phi \angle -240^\circ$$

$$I_{ab} = I_\phi \angle 0^\circ$$

$$I_{bc} = I_\phi \angle -120^\circ$$

$$I_{ca} = I_\phi \angle -240^\circ$$

# Voltages and currents

## 1. $\Delta$ -connection (cont)

$$V_{LL} = V_{\phi}$$

The currents are:


$$\begin{aligned} I_a &= I_{ab} - I_{ca} = I_{\phi} \angle 0^\circ - I_{\phi} \angle 240^\circ = I_{\phi} - \left( -\frac{1}{2} I_{\phi} + j \frac{\sqrt{3}}{2} I_{\phi} \right) \\ &= \frac{3}{2} I_{\phi} - j \frac{\sqrt{3}}{2} I_{\phi} = \sqrt{3} I_{\phi} \left( \frac{\sqrt{3}}{2} - j \frac{1}{2} \right) = \sqrt{3} I_{\phi} \angle -30^\circ \end{aligned}$$

The magnitudes:

$$I_L = \sqrt{3} I_{\phi}$$
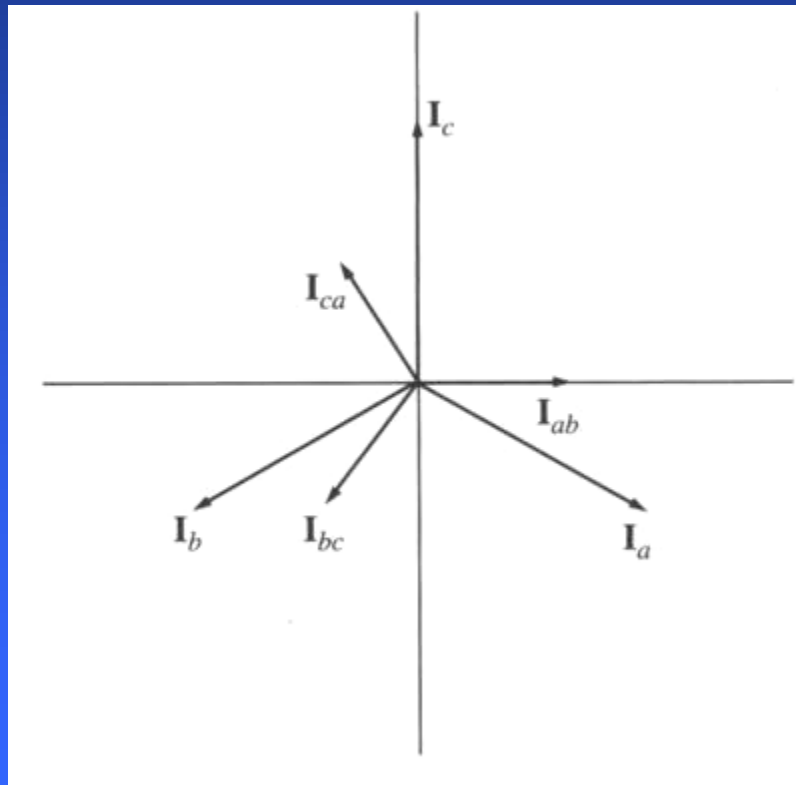
# Voltages and currents

For the connections with the *abc* phase sequences, the current of a line **lags** the corresponding phase current by  $30^\circ$  (see Figure below).



# Power relationships

For a balanced Y-connected load with the impedance  $Z_\phi = Z\angle\theta$ :

and voltages:

$$v_{an}(t) = \sqrt{2}V \sin \omega t$$

$$v_{bn}(t) = \sqrt{2}V \sin(\omega t - 120^\circ)$$


$$v_{cn}(t) = \sqrt{2}V \sin(\omega t - 240^\circ)$$

The currents can be found:

$$i_a(t) = \sqrt{2}I \sin(\omega t - \theta)$$

$$i_b(t) = \sqrt{2}I \sin(\omega t - 120^\circ - \theta)$$
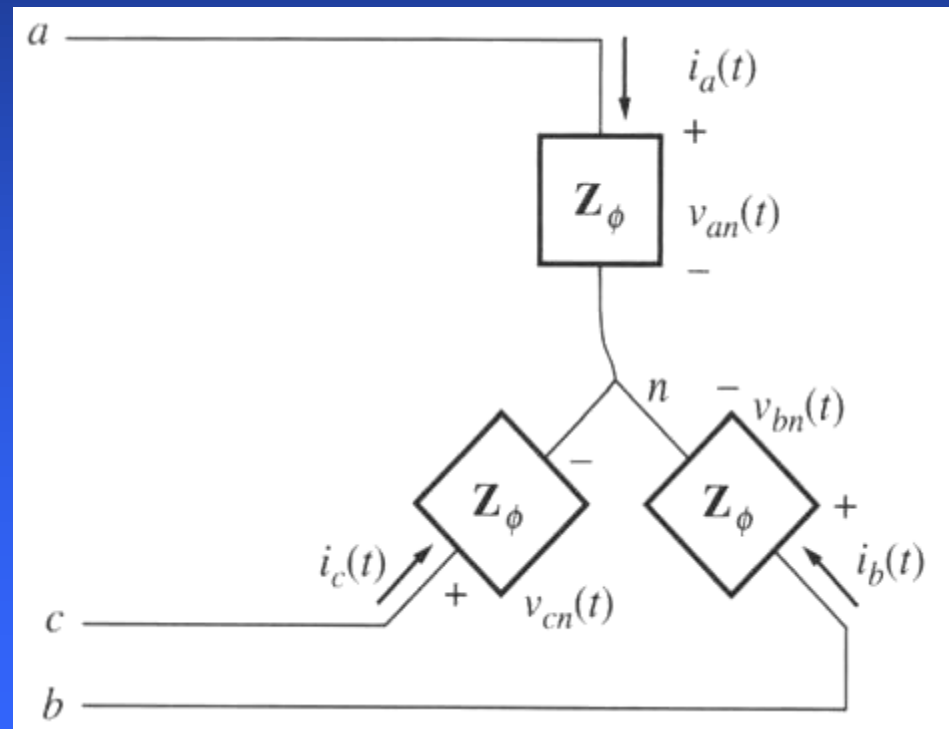
$$i_c(t) = \sqrt{2}I \sin(\omega t - 240^\circ - \theta)$$



# Power relationships

The instantaneous power is:

$$p(t) = v(t)i(t)$$

Therefore, the instantaneous power supplied to each phase is:

$$p_a(t) = v_{an}(t)i_a(t) = 2VI \sin(\omega t) \sin(\omega t - \theta)$$

$$p_b(t) = v_{bn}(t)i_b(t) = 2VI \sin(\omega t - 120^\circ) \sin(\omega t - 120^\circ - \theta)$$

$$p_c(t) = v_{cn}(t)i_c(t) = 2VI \sin(\omega t - 240^\circ) \sin(\omega t - 240^\circ - \theta)$$

Since

$$\sin \alpha \sin \beta = \frac{1}{2} [\cos(\alpha - \beta) - \cos(\alpha + \beta)]$$

# Power relationships

Therefore

$$p_a(t) = VI [\cos \theta - \cos(2\omega t - \theta)]$$

$$p_b(t) = VI [\cos \theta - \cos(2\omega t - 240^\circ - \theta)]$$

$$p_c(t) = VI [\cos \theta - \cos(2\omega t - 480^\circ - \theta)]$$


The total power on the load

$$p_{tot}(t) = p_a(t) + p_b(t) + p_c(t) = 3VI \cos \theta$$
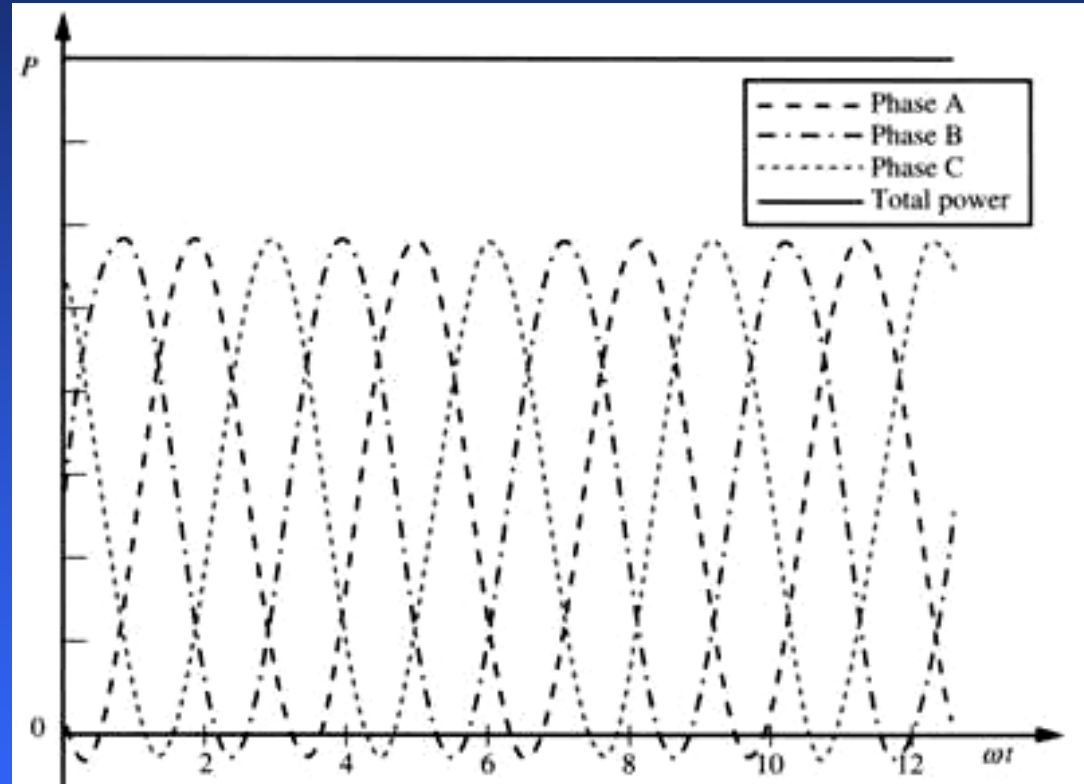
# Power relationships

The instantaneous power in phases.

The total power supplied to the load is constant.



# Power relationships

Line quantities: Y-connection.

Power consumed by a load:

$$P = 3V_{\phi}I_{\phi} \cos \theta$$

Since for this load

$$I_L = I_{\phi} \text{ and } V_{LL} = \sqrt{3}V_{\phi}$$

Therefore:

$$P = 3 \frac{V_{LL}}{\sqrt{3}} I_L \cos \theta$$

Finally:

$$P = \sqrt{3}V_{LL}I_L \cos \theta$$

Note: these equations are valid for balanced loads only.



# Power relationships

Line quantities:  $\Delta$ -connection.

Power consumed by a load:

$$P = 3V_{\phi}I_{\phi} \cos \theta$$

Since for this load

$$I_L = \sqrt{3}I_{\phi} \text{ and } V_{LL} = V_{\phi}$$

Therefore:

$$P = 3 \frac{I_L}{\sqrt{3}} V_{LL} \cos \theta$$

Finally:

$$P = \sqrt{3}V_{LL}I_L \cos \theta$$

Same as for a Y-connected load!

Note: these equations were derived for a balanced load.

# Problems