

[Electrical Engineering Assignment](#)

- [Home](#)
- [About Us](#)
- [Electrical Engineering Topics](#)
- [Blog](#)
- [Submit Your Assignment](#)
- [Make Payment](#)

USA:  +1-585-535-1023UK:  +44-208-133-5697AUS:  +61-280-07-5697

12. UNBALANCED DELTA CONNECTED LOAD

[Home](#) → 12. UNBALANCED DELTA CONNECTED LOAD

When the load impedance in the three phases are not equal in magnitude or phase or both, the load is said to be *unbalanced*. If three unequal loads are connected to form a delta and connected across a 3-phase supply the currents in the three loads will not be equal in magnitude and/or phase. The three-phase currents and the line currents will also be unbalanced.

Example 40. A 440 V, 50 Hz, 3-phase supply has delta-connected load having 50 Ω between R and Y, 159 mH between Y and B and 15.9 μF between B and R. Find;

(i) The line current for the sequence RYB.

(ii) The value of star-connected balanced resistors for the same power.


Solution. Phase voltage (E_{ph}) = line voltage (E_L) = 440 V

The potential difference across three-phases are given by

$$E_{RY} = 440(1 + j0) = 4400^\circ \text{ V}$$

$$E_{YB} = 440(-0.5 - j0.866) \text{ or } 440 - 120^\circ \text{ V}$$
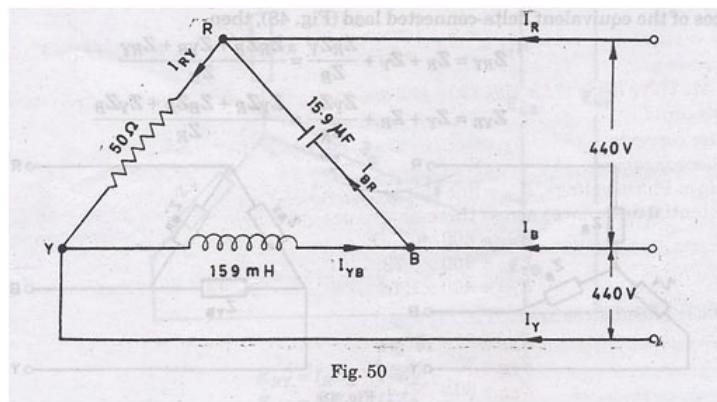
$$E_{BR} = 440(-0.5 + j0.866) \text{ or } 440 120^\circ \text{ V}$$



$$\text{Impedance, } Z_{RY} = (50 + j0) = 50 0^\circ \Omega$$

$$\begin{aligned} \text{Impedance, } Z_{YB} &= (0 + j2\pi fL) = (0 + j2\pi \times 50 \times 159 \times 10^{-3}) \\ &= (0 + j50) \text{ or } 50 90^\circ \Omega \end{aligned}$$

$$\text{Impedance } Z_{BR} = \left(0 - \frac{j}{2\pi f C}\right)$$

$$= \left(0 - \frac{1}{2\pi \times 50 \times 15.9 \times 10^{-6}}\right) = (0 - j200) = 200\angle -90^\circ$$

(i) Phase currents :

$$\text{Phase current, } I_{RY} = \frac{E_{RY}}{Z_{RY}} = \frac{440\angle 0^\circ}{50\angle 0^\circ} = 8.1(1+j0)A$$

$$\text{Phase current, } I_{YB} = \frac{E_{YB}}{Z_{YB}} = \frac{440\angle -120^\circ}{50\angle 0^\circ} = 8.8\angle -120^\circ$$

$$\text{Phase current, } I_{BR} = \frac{E_{BR}}{Z_{BR}} = \frac{440\angle 120^\circ}{200\angle -90^\circ} = 2.2\angle 210^\circ = 2.2(-0.866 - j0.5)A.$$

Line currents:

$$\text{Line current } I_R = I_{RY} - I_{BR} = 8.8(1+j0) - 2.2(-0.866 - j0.5)$$

$$= 8.8 + j0 + 1.905 + j1.1 = 10.7 + j1.1 = 10.75 \angle 5.8^\circ A. \text{ (Ans.)}$$

$$\text{Line current } I_Y = I_{YB} - I_{RY} = 8.8(-0.866 + j0.5) - 8.8(1+j0)$$

$$= -7.62 + j4.4 - 8.8 - j0$$

$$= -16.42 + j4.4 = 16.99 \angle 164.9^\circ A. \text{ (Ans.)}$$

$$\text{Line current } I_B = I_{BR} = I_{RY} = 2.2(-0.866 - j0.5) - 8.8(-0.866 + j0.5)$$

$$= -1.905 - j1.1 + 7.62 - j4.4 = 5.715 - j5.5$$

$$= 7.93 \angle -43.9^\circ A. \text{ (Ans.)}$$

(ii) Power supplied:

$$P = I_R^2 \times R = 8.8^2 \times 50 = 3872 W$$

Let the resistance per phase be R_{ph} which when connected in star across 440 V, 3-phase supply take power of 3872 W.

$$\text{Line current, } I_L = I_{ph} = \frac{E_L/\sqrt{3}}{R_{ph}} = \frac{440/\sqrt{3}}{R_{ph}}$$

$$\text{Power supplied, } P = \sqrt{3} E_L I_L$$

$$\therefore 3872 = \sqrt{3} \times 440 \times \frac{440/\sqrt{3}}{R_{ph}}$$

$$\therefore R_{ph} = \frac{\sqrt{3} \times 440 \times 440/\sqrt{3}}{3872} = \frac{440 \times 440}{3872} = 50 \Omega \text{ (Ans.)}$$

Example 41. A 440 V, 50 Hz, 3-phase supply has delta-connected load having 50 Ω between R and y, 159 mH between Y and B and 15.9 μF between B and R. Find;

(i) The line current for the sequence RYB.

(ii) The value of star-connected balanced resistors for the same power.

Solution.

Phase voltage (E_{ph}) = line voltage, (E_L) = 400 V

The potential differences across three-phases are given by:

$$E_{RY} = 400 \text{ } 0^\circ$$

$$E_{YB} = 400 \text{ } -120^\circ$$

$$E_{BR} = 400 \text{ } 120^\circ$$

The phase impedances are:

$$Z_{RY} = 31 + j59 = 66.6 \text{ } 62.3^\circ$$

$$Z_{YB} = 30 - j40 = 50 - 53.1^\circ$$

$$Z_{BR} = 80 + j60 = 100 \text{ } 36.9^\circ$$

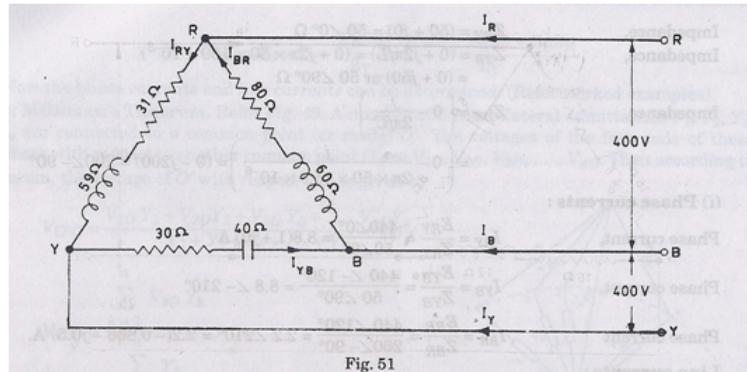


Fig. 51

Phase currents:

$$I_{RY} = \frac{E_{RY}}{Z_{RY}} = \frac{400\angle 0^\circ}{66.6\angle 62.3^\circ} = 6\angle -62.3^\circ \text{ A. Ans.}$$

$$I_{YB} = \frac{E_{YB}}{Z_{YB}} = \frac{400\angle -120^\circ}{50\angle -53.1^\circ} = 8\angle -66.9^\circ \text{ A. Ans.}$$

$$I_{BR} = \frac{E_{BR}}{Z_{BR}} = \frac{400\angle 120^\circ}{100\angle 36.9^\circ} = 4\angle 83.1^\circ \text{ A. Ans.}$$

Line currents:

$$\begin{aligned} I_R &= I_{RY} - I_{BR} = 6\angle -62.3^\circ - 4\angle 83.1^\circ \\ &= 6(0.465 - j0.885) - 4(0.12 + j0.993) \\ &= 2.79 - j5.31 - 0.48 - j3.97 = 2.31 - j9.28 = 9.56 \angle -76^\circ \text{ A. (Ans.)} \end{aligned}$$

$$\begin{aligned} I_Y &= I_{IB} - I_{RY} = 8\angle -66.9^\circ - 6\angle -62.3^\circ \\ &= 8(0.392 - j0.92) - 6(0.465 - j0.885) \\ &= (3.136 - j7.36) - (2.79 - j5.31) \\ &= 0.346 - j2.05 = 2.07 \angle -80.4^\circ \text{ A. (Ans.)} \end{aligned}$$

$$\begin{aligned} I_B &= I_{BR} - I_{IB} = 4\angle 83.1^\circ - 8\angle -66.9^\circ \\ &= 4(0.12 + j0.993) - 8(0.392 - j0.92) \\ &= 0.48 + j3.97 - 3.136 + j7.36 \\ &= -2.656 + j11.33 = 11.637 \angle 103.2^\circ \text{ A. (Ans.)} \end{aligned}$$

Total power is the sum of power in different phases

$$\begin{aligned} P &= E_{RY} \times I_{RY} + E_{IB} \times I_{IB} + E_{BR} \times I_{BR} \\ &= 400 \angle 0^\circ \times 6 \angle -62.3^\circ + 400 \angle -120^\circ \times 8 \angle -66.9^\circ \\ &\quad + 400 \angle 120^\circ \times 4 \angle 83.1^\circ \\ &= 400 \times 6 \cos(-62.3^\circ) + 400 \times 8 \cos(53.1^\circ) + 400 \times 4 \cos(-36.9^\circ) \\ &= 1115.6 + 1921.3 + 1279.5 = 4316.4 \text{ W} \end{aligned}$$

$$\begin{aligned} OR \quad P &= I_{RY}^2 R_{RY} + I_{IB}^2 R_{IB} + I_{BR}^2 R_{BR} \\ &= 6^2 \times 31 + 8^2 \times 30 + 42 \times 80 = 1116 + 1920 + 1280 = 4316 \text{ W} \end{aligned}$$

Hence, total power = 4316.4 W. (Ans.)

Example 42. For the unbalanced delta-connected load of Fig 52, find the phase currents, line currents and total power consumed by the load, when phase sequence is:

- (i) RYB
- (ii) RBY

(AMIE Advanced Electrical M/c Winter, 1998)

Solution.

- (i) Phase sequence RYB :

The potential differences across three phases are:

$$E_{RY} = 200 \text{ } 0^\circ$$


$$E_{YB} = 200 \text{ } -120^\circ$$

$$E_{BR} = 200 \text{ } 120^\circ$$

$$\text{Impedance, } Z_{RY} = 12 + j16 = 20 \text{ } 53.13^\circ$$

$$\text{Impedance, } Z_{YB} = 16 + j12 = 20 \text{ } 36.8^\circ$$
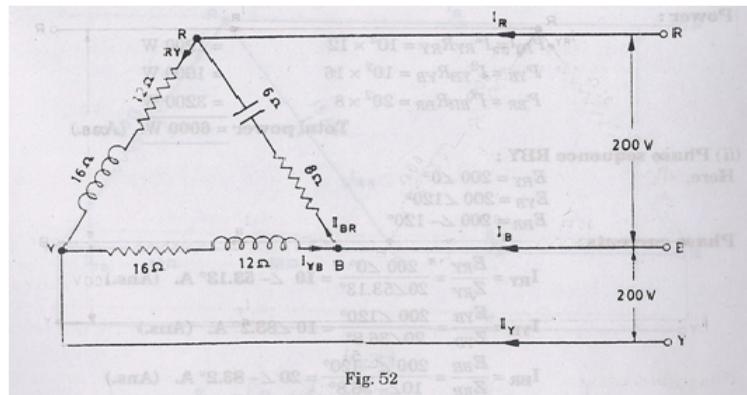
$$\text{Impedance, } Z_{BR} = 8 - j6 = 10 - 36.8^\circ$$



$$\text{Phase current, } I_{RY} = \frac{E_{RY}}{Z_{RY}} = \frac{200\angle 0^\circ}{20\angle 53.13^\circ} = 10\angle -53.13^\circ \text{ A. (Ans.)}$$

$$\text{Similarly, } I_{YB} = \frac{E_{YB}}{Z_{YB}} = \frac{200\angle -120^\circ}{20\angle 36.8^\circ} = 10\angle -156.8^\circ \text{ A. (Ans.)}$$

$$I_{BR} = \frac{E_{BR}}{Z_{BR}} = \frac{200\angle -120^\circ}{10\angle -36.8^\circ} = 20\angle 156.8^\circ \text{ A. (Ans.)}$$

Line currents:

$$\begin{aligned} \text{Line current, } I_R &= I_{RY} - I_{BR} = 10\angle -53.13^\circ - 10\angle 156.8^\circ \\ &= 10(0.60 - j0.8) - 20(-0.72 + j0.394) = 6.0 - j8 + 18A - j7.88 \\ &= 24.4 - j15.88 = 29.11\angle -33^\circ \text{ A. (Ans.)} \end{aligned}$$

$$\begin{aligned} \text{Similarly, } I_V &= I_{IB} - I_{RY} = 10\angle -156.8^\circ - 10\angle -53.13^\circ \\ &= 10(-0.919 - j0.394) - 10(0.6 - j0.8) = -9.19 - j3.94 - 6 + j8 \\ &= 15.19 + j1.06 = 15.72\angle 165^\circ \text{ A. (Ans.)} \end{aligned}$$

$$\begin{aligned} I_B &= I_{BR} - I_{IB} = 20\angle 156.8^\circ - 10\angle -156.8^\circ \\ &= 20(0.919 - j0.394) - 10(-0.919 - j0.394) \\ &= -18.38 + j7.88 + 9.19 + j3.94 = -9.19 + j11.82 = 14.97\angle 127.9^\circ \end{aligned}$$

[Check $\Sigma I = (24.4 - j15.88) + (-15.19 + j1.06) + (-9.19 + j11.82) = 0$]

Power:

$$P_{RY} = I_{RY}^2 R_{RY} = 10^2 \times 12 = 1200 \text{ W}$$

$$P_{YB} = I_{YB}^2 R_{YB} = 10^2 \times 16 = 1600 \text{ W}$$

$$P_{BR} = I_{BR}^2 R_{BR} = 20^2 \times 8 = 3200 \text{ W}$$

$$\text{Total power} = 6000 \text{ W} \quad (\text{Ans.})$$

Phase sequence RBY:

Here $E_{RY} = 200$

$E_{YB} = 200$

$$E_{BR} = 200$$

Phase currents:

$$I_{RY} = \frac{E_{RY}}{Z_{RY}} = \frac{200\angle 0^\circ}{20\angle 53.13^\circ} = 10\angle -53.13^\circ \text{ A. (Ans.)}$$

$$I_{YB} = \frac{E_{YB}}{Z_{YB}} = \frac{200\angle 120^\circ}{20\angle 36.8^\circ} = 10\angle 83.2^\circ \text{ A. (Ans.)}$$

$$I_{BR} = \frac{E_{BR}}{Z_{BR}} = \frac{200\angle -120^\circ}{20\angle -36.8^\circ} = 10\angle -83.2^\circ \text{ A. (Ans.)}$$

Line currents:

$$\begin{aligned} I_R &= I_{RY} - I_{BR} = 10\angle -53.13^\circ - 10\angle -83.2^\circ \\ &= 10(0.6 - j0.8) - 10(0.118 - j0.993) = 6 - j8 - 2.36 + j19.86 \\ &= 3.64 + j11.86 = 12.4 \angle 72.9^\circ \text{ A. (Ans.)} \end{aligned}$$

$$\begin{aligned} I_Y &= I_{YB} - I_{RY} = 10\angle 83.2^\circ - 10\angle -53.13^\circ \\ &= 10(0.118 + j0.993) - 10(0.6 - j0.8) \\ &= 1.18 + j9.93 - 6 + j8 = -4.82 + j17.93 = 18.56 \angle 105^\circ \text{ A. (Ans.)} \end{aligned}$$

$$\begin{aligned} I_B &= I_{BR} - I_{YB} = 10\angle -83.2^\circ - 10\angle 36.8^\circ \\ &= 10(0.118 - j0.993) - 10(0.118 + j0.993) \\ &= 2.36 - j19.86 - 1.18 - j9.93 = 1.18 - j29.79 = 29.81 \angle -87.7^\circ \text{ A. (Ans.)} \end{aligned}$$

$$P_{RY} = 10^2 \times 12 = 1200 \text{ W}$$

$$P_{YB} = 10^2 \times 16 = 1600 \text{ W}$$

$$P_{BR} = 20^2 \times 8 = 3200 \text{ W}$$

$$\text{Total power} = 6000 \text{ W. (Ans.)}$$

Example 43. A 3-phase, 400 V, 50 Hz system has the following load connected in delta:

Between R and Y lines: a non-reactive resistor of 50 Ω

Between Y and B lines: a coil having a resistance of 10 Ω and reactance of 30 Ω

Between B and R lines: a loss-free capacitor of 15 μF.

Calculate: (i) The phase currents (ii) The line currents.

Assume phase sequence to be RYB.

Solution.

$$E_{ph} = E_L = 400 \text{ V}$$

The potential difference across the three phases are:

$$E_{RY} = 400 \angle 0^\circ \text{ V}$$

$$E_{YB} = 400 \angle -120^\circ \text{ V}$$

$$E_{BR} = 400 \angle 120^\circ \text{ V}$$

$$E_{YB} = 400 \angle -120^\circ \text{ V}$$

$$E_{BR} = 400 \angle 120^\circ \text{ V}$$

Impedance

$$Z_{RY} = 50 + j0 = 50 \angle 0^\circ \Omega$$

$$Z_{YB} = 10 + j30 = 31.62 \angle 71.56^\circ \Omega$$

$$Z_{BR} = \left(0 - \frac{j}{2\pi f C} \right) = \left(0 - \frac{j}{2\pi \times 50 \times 15 \times 10^{-6}} \right)$$

Phase currents:

$$I_{RY} = \frac{E_{RY}}{Z_{RY}} = \frac{400 \angle 0^\circ}{50 \angle 0^\circ} = 8 \angle 0^\circ \text{ A. (Ans.)}$$

$$I_{YB} = \frac{E_{YB}}{Z_{YB}} = \frac{400 \angle -120^\circ}{31.62 \angle 71.56^\circ} = 12.65 \angle -191.56^\circ \text{ A. (Ans.)}$$

$$I_{BR} = \frac{E_{BR}}{Z_{BR}} = \frac{400 \angle 120^\circ}{212 \angle -90^\circ} = 1.886 \angle 210^\circ \text{ A. (Ans.)}$$

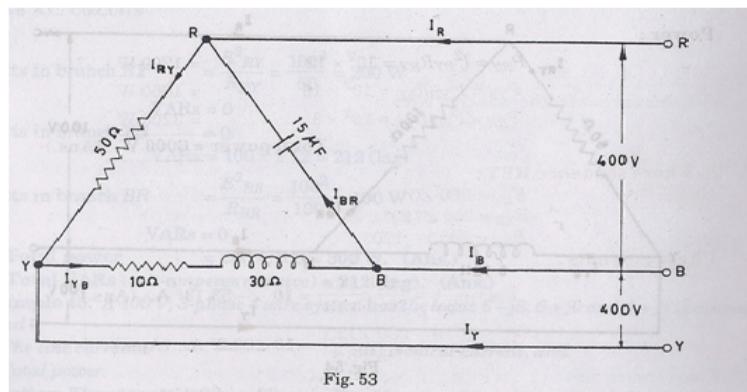


Fig. 53

Line Current

$$I_R = I_{RY} - I_{BR} = 8 \angle 0^\circ - 1.886 \angle 210^\circ$$

$$\begin{aligned} &= 8 - 1.886(-0.866 - j0.5) = 8 + 1.633 + j0.943 \\ &= 9.633 + j0.943 = \mathbf{9.68 \angle 5.6^\circ \text{ A. (Ans.)}} \end{aligned}$$

$$I_Y = I_{YB} - I_{RY} = 12.65 \angle -191.56^\circ - 8 \angle 0^\circ$$

$$\begin{aligned} &= 12.65(-0.979 + j0.2) - 8 = -12.38 + j2.53 - 8 \\ &= -20.38 + j2.53 = \mathbf{20.53 \angle 7.07^\circ \text{ A. (Ans.)}} \end{aligned}$$

$$\begin{aligned} I_B &= I_{BR} - I_{YB} = 1.886 \angle 210^\circ - 12.65 \angle -191.56^\circ \\ &= 1.886(-0.866 - j0.5) - 12.65(-0.979 + j0.2) \\ &= -1.633 - j0.943 + 12.38 - j2.53 \end{aligned}$$

$$= 10.747 - j3.473 = \mathbf{11.29 \angle 17.4^\circ \text{ A. (Ans.)}}$$

Example 45. A 400 V, 3-phase 4 wire system has the loads $6 - j8$, $6 + j0$ and $4 + j3 \Omega$ connected in star. Find:

(i) The line currents,

- (ii) Neutral current, and
 (iii) Total power.

Solution. The connections are shown in Fig. 56.

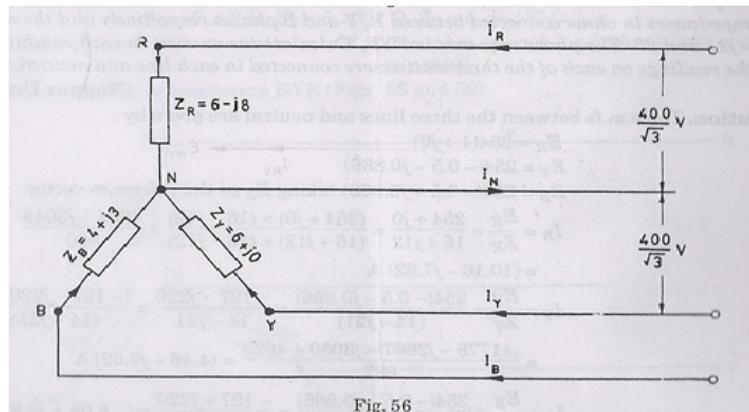


Fig. 56

The potential differences across the three phases are:

$$E_{RN} = \frac{400}{\sqrt{3}} \angle 0^\circ = 230.9 \angle 0^\circ V$$

$$E_{YN} = 230.9 \angle -120^\circ V$$

$$E_{BN} = 230.9 \angle 120^\circ V$$

Impedances:

$$Z_R = 6 - j8 = 10 \angle -53.13^\circ$$

$$Z_Y = 6 + j0 = 6 \angle 0^\circ$$

$$Z_B = 4 + j3 = 5 \angle 36.9^\circ$$

(i) **Line currents:**

$$I_R = I_{RN} = \frac{E_{RN}}{Z_R} = \frac{230.9 \angle 0^\circ}{10 \angle -53.13^\circ} = 23.09 \angle 53.13^\circ A. \quad (\text{Ans}).$$

$$I_Y = I_{YN} = \frac{E_{YN}}{Z_Y} = \frac{230.9 \angle -120^\circ}{6 \angle 0^\circ} = 38.48 \angle -120^\circ A. \quad (\text{Ans}).$$

$$I_B = I_{BN} = \frac{E_{BN}}{Z_B} = \frac{230.9 \angle 120^\circ}{5 \angle 36.9^\circ} = 46.18 \angle 83.1^\circ A. \quad (\text{Ans}).$$

(ii) **The current in the neutral wire:**

$$I_N = -(I_R + I_Y + I_B)$$

$$= -[23.09 \angle 53.13^\circ + 38.48 \angle -120^\circ + 46.18 \angle 83.1^\circ]$$

$$= -[23.09(0.6 + j0.8) + 36.18(-0.5 - j0.866) - 46.18(0.12 + j0.99)] = -[13.85 + j18.47 - 18.24 - j31.59 + 5.54 + j45.72]$$

$$= -(1.15 + j32.6) = -1.15 - j32.6 = 32.62 \angle -92^\circ A. \quad (\text{Ans.})$$

Power:

Power taken by phase R,

$$P_R = I_R^2 \times R_R = 23.09^2 \times 6 = 3199 \text{ W (app.)}.$$

$$\text{Similarly, } P_Y = I_Y^2 \times R_Y = 38.48^2 \times 6 = 8884 \text{ W (app.)}.$$

$$\text{and } P_B = I_B^2 \times R_B = 46.18^2 \times 4 = 8530 \text{ W (app.)}.$$

$$\text{Total power taken } P_R + P_Y + P_B = 3199 + 8884 + 8530 = 20613 \text{ W (Ans).}$$

Example 46. A 440/254 volt, 3 phase, 4-core supplies an unbalanced load represented by the following impedance in ohms connected between R, Y and B phases respectively and the neutral 16 + j12; 14 - j21 and 25. The phase sequence is RYE. Calculate the current in each conductor of the cable and the readings on each of the three wattmeters connected in each line and neutral.

Solution. The e.m.fs between the three lines and neutral are given by :

$$E_R = 254(1 + j0)$$

$$E_Y = 254(-0.5 - j0.866)$$

$$E_B = 254(-0.5 + j0.866) \text{ taking } E_R \text{ as the reference vector}$$

$$I_R = \frac{E_R}{Z_R} = \frac{254 + j0}{16 + j12} = \frac{(254 + j0) \times (16 - j12)}{(254 + j12) \times (16 - j12)} = \frac{4064 - j3048}{400} \\ = (10.16 - j7.62)A$$

$$I_Y = \frac{E_Y}{Z_Y} = \frac{254(-0.5 - j0.866)}{(14 - j21)} = \frac{-127 - j220}{14 - j21} = \frac{(-127 - j220) \times (14 + j21)}{(14 - j21)(14 + j21)} \\ = \frac{-1778 - j2667 - j3080 + 4620}{637} = (4.46 - j9.02)A$$

$$I_B = \frac{E_B}{Z_B} = \frac{254(-0.5 + j0.866)}{25} = \frac{-127 + j220}{25} = (-5.08 + j8.8)A$$

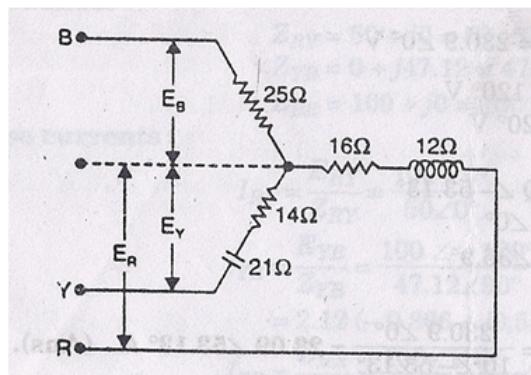


Fig.57 (a) Circuit Diagram

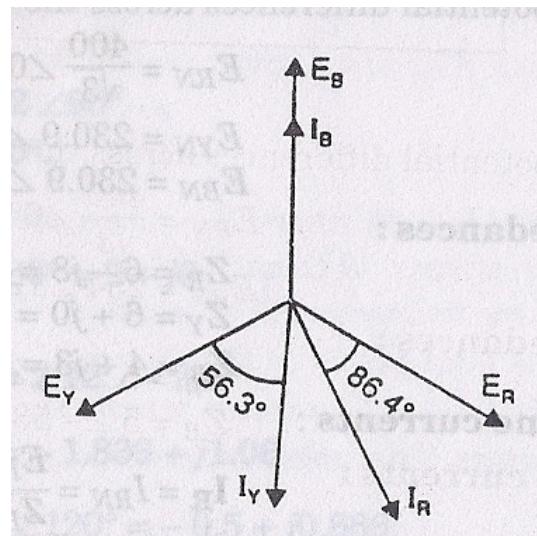


Fig.57 (b) Phasor Diagram

Now current in neutral wire,

$$\begin{aligned} I_N &= -(I_R + I_Y + I_B) \\ &= -[(10.16 - j7.62) + (4.46 - j9.02) + (-5.08 + j8.8)] \\ &= -9.54 + j7.84 \end{aligned}$$

Evaluating these currents, we get

$$I_R = \sqrt{10.16^2 + (-7.62)^2} = 12.7 \text{ A. (Ans.)}$$

$$I_Y = \sqrt{4.46^2 + (-9.02)^2} = 10.06 \text{ A. (Ans.)}$$

$$I_B = \sqrt{(-5.08)^2 + (8.8)^2} = 10.16 \text{ A. (Ans.)}$$

$$I_N = \sqrt{(-9.54)^2 + (7.84)^2} = 12.35 \text{ A. (Ans.)}$$

$$\text{Power in R-phase} = I_R^2 \times R_R = (-12.7)^2 \times 16 = 2580.6 \text{ W. (Ans.)}$$

$$\text{Power in Y-phase} = I_Y^2 \times R_Y = (10.06)^2 \times 14 = 1416.8 \text{ W. (Ans.)}$$


$$\text{Power in B-phase} = I_B^2 \times R_B = (10.16)^2 \times 25 = 2580.6 \text{ W. (Ans.)}$$

Example 47. A 3-phase, 4-wire system having a 440 V line to line has the following loads connected between the respective lines and neutral:
 $Z_R = 5 \angle 0^\circ \Omega$, $Z_Y = 5 \angle 37^\circ \Omega$, $Z_B = 5 \angle -53^\circ \Omega$.

Calculate the current in neutral wire and power taken by each load when phase sequence is:

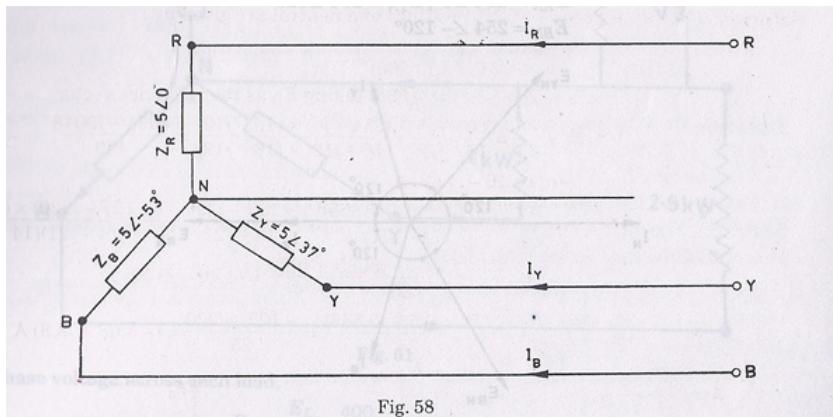- (i) RYB
- (ii) RBY.

Solution. (i) Phase sequence RYB (Figs. 58 and 59).



The potential differences across the three phases are:

$$E_{RN} = \frac{440}{\sqrt{3}} \angle 0^\circ = 254 \angle 0^\circ, E_{YN} = 254 \angle -120^\circ$$

$$E_{BN} = 254 \angle 120^\circ$$

Impedances:

$$Z_R = 5 \angle 0^\circ, Z_Y = 5 \angle 37^\circ$$

$$Z_B = 5 \angle -53^\circ$$

Line currents:

$$I_R = I_{RN} = \frac{E_{RN}}{Z_R} = \frac{254 \angle 0^\circ}{5 \angle 0^\circ} = 50.8 \angle 0^\circ$$

$$I_Y = I_{YN} = \frac{E_{YN}}{Z_Y} = \frac{254 \angle -120^\circ}{5 \angle 37^\circ} = 50.8 \angle -157^\circ$$

$$I_B = I_{BN} = \frac{E_{BN}}{Z_B} = \frac{254 \angle 120^\circ}{5 \angle -53^\circ} = 50.8 \angle 173^\circ$$

Current in the neutral:

$$I_N = -(I_R + I_Y + I_B)$$

$$= -(50.8 \angle 0^\circ + 50.8 \angle -157^\circ + 50.8 \angle 173^\circ)$$


$$= -[50.8 + 50.8(-0.92 - j0.39) + 50.8(-0.99 + j0.122)]$$

$$= -[50.8 - 46.74 - j19.81 - 50.3 + j6.2]$$

$$= -(-46.24 - j13.61) = 46.24 + j13.61$$

$$= 48.2 \angle 16.4^\circ. (\text{Ans.})$$

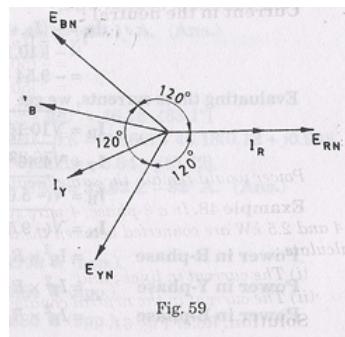Now $R_R = 5 \Omega$, $R_Y = 5 \cos 37^\circ = 4 \Omega$,



$$R_B = 5 \cos(-53^\circ) = 3 \Omega$$

Power taken by phase R,

$$P_R = 50.8^2 \times 5 = 12903 \text{ W. (Ans.)}$$


$$P_Y = 50.8^2 \times 4 = 10322 \text{ W. (Ans.)}$$

$$P_B = 50.8^2 \times 3 = 7742 \text{ W. (Ans.)}$$

Phase Sequence RBY (Fig. 60):

$$E_{RN} = 254 \angle 0^\circ, E_{YN} = 254 \angle 120^\circ$$

$$E_{BN} = 254 \angle -120^\circ$$

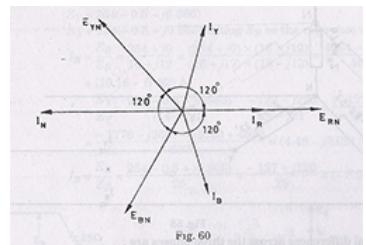

Line currents:

$$I_R = I_{RN} = \frac{E_{RN}}{Z_R} = \frac{254 \angle 0^\circ}{5 \angle 0^\circ} = 50.8 \angle 0^\circ$$

$$I_Y = I_{YN} = \frac{E_{YN}}{Z_Y} = \frac{254 \angle 120^\circ}{5 \angle 37^\circ} = 50.8 \angle 83^\circ$$

$$I_B = I_{BN} = \frac{E_{BN}}{Z_B} = \frac{254 \angle -120^\circ}{5 \angle -53^\circ} = 50.8 \angle -67^\circ$$

Current in the neutral:

$$I_N = -(I_R + I_Y + I_B)$$

$$= -(50.8 \angle 0^\circ + 50.8 \angle 83^\circ + 50.8 \angle -67^\circ)$$

$$= -[50.8 + 50.8(0.122 + j0.992) + 50.8(0.39 - j0.92)] = -(50.8 + 6.197 + j50.4 + 19.81 - j46.74)$$


$$= -(76.81 + j3.66) = -76.81 - j3.66$$

$$= 76.89 - 177.3^\circ \text{ A. (Ans.)}$$

Power would remain the same because magnitude of branch currents is unaltered.

Example 48. In a 3-phase, 4-wire system, the line voltage is 400 V and non-inductive loads of 5, 4 and 2.5 kW are connected between the three lines conductors and the neutral, as shown in Fig. 61. Calculate
 i. The current in lines; and
 ii. The current in the neutral conductor.

Solution. Refer Fig. 61.

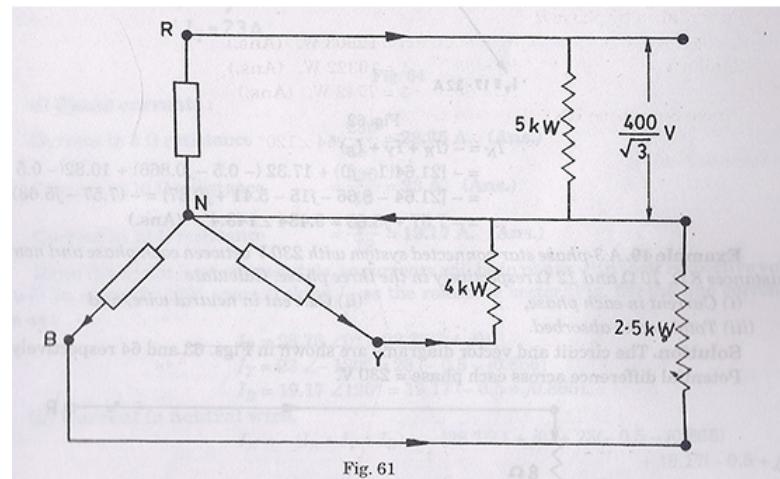

Phase voltage across each load,

$$E_{ph} = \frac{E_L}{\sqrt{3}} = \frac{400}{\sqrt{3}} = 231 \text{ V}$$

(i) Current in phase R,

$$I_R = (\text{line current}) = \frac{kW \times 1000}{E_{ph} \cos \phi} = \frac{5 \times 1000}{231 \times 1} = 21.64 \text{ A. (Ans.)}$$

$$\text{Current in phase Y, } I_Y = \frac{4 \times 1000}{231 \times 1} = 17.32 \text{ A. (Ans.)}$$

$$\text{Current in phase B, } I_B = \frac{2.5 \times 1000}{231 \times 1} = 10.82 \text{ A. (Ans.)}$$


These currents are mutually 120° out of phase as the circuit is purely resistive. Taking I_R as the reference vector, line currents may be given as

$$I_R = 21.64 \angle 0^\circ = 21.64 (1 + j0)$$

$$I_Y = 17.32 \angle -120^\circ = 17.32 (-0.5 - j0.866)$$

$$I_B = 10.82 \angle 120^\circ = 10.82 (-0.5 + j0.866)$$

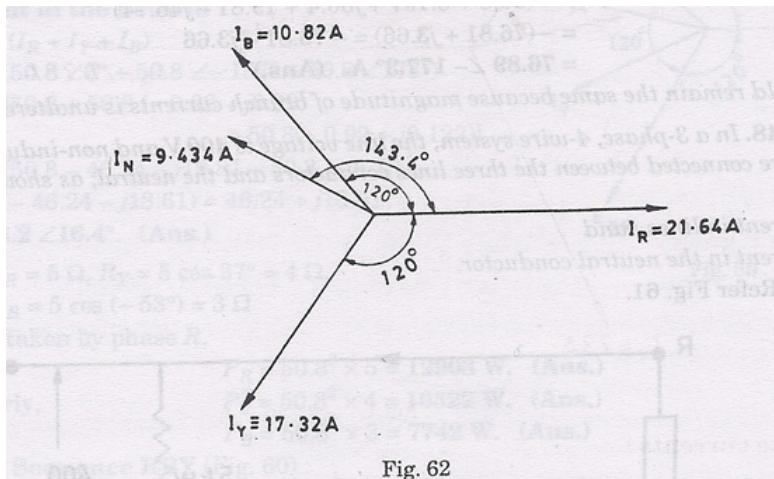(ii) Current in the neutral wire (Refer Fig. 62):



$$I_N = -(I_R + I_Y + I_B)$$


$$\begin{aligned} &= -[21.64(1-j0) + 17.32(-0.5-j0.866) + 10.82(-0.5+j0.866)] \\ &= -[21.64 - 8.66 - j15 - 5.41 + j9.371] = -(7.57 - j5.63) \\ &= -7.57 + j5.63 = \mathbf{9.434 \angle 143.4^\circ. (Ans.)} \end{aligned}$$


Example 49. A 3-phase star-connected system with 230 V between each phase and neutral has resistances 8 Ω, 10 Ω and 12 Ω respectively in the three phase. Calculate:

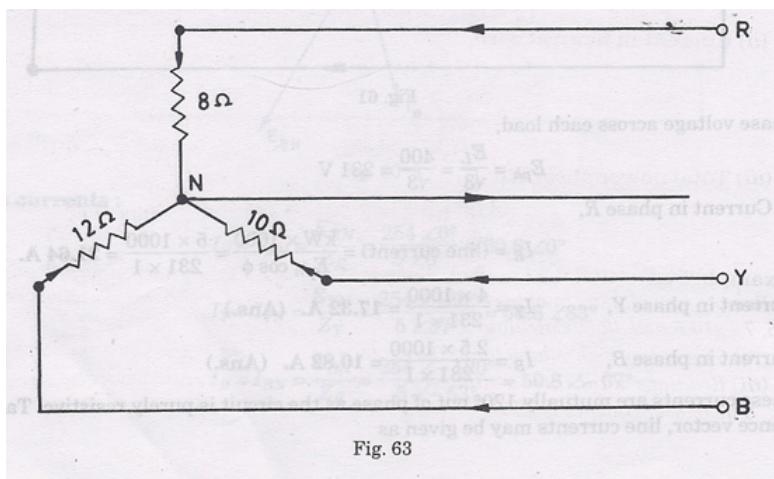- i. Current in each phase,
- ii. Current in neutral wire, and
- iii. Total power absorbed.

Solution. The circuit and vector diagrams are shown in Figs. 63 and 64 respectively.

Potential difference across each phase = 230 V



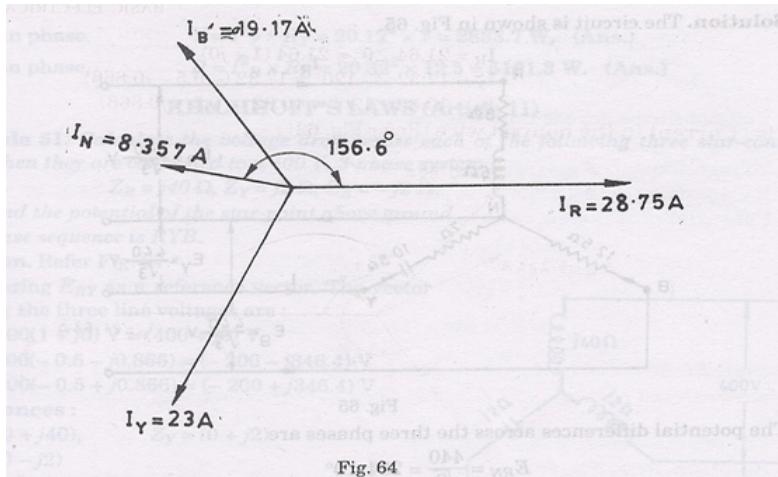

(i) Phase currents:

$$\text{Current in } 8 \Omega \text{ resistance} = \frac{230}{8} = 28.75 \text{ A. (Ans.)}$$

$$\text{Current in } 10 \Omega \text{ resistance} = \frac{230}{10} = 23 \text{ A. (Ans.)}$$

$$\text{Current in } 12 \Omega \text{ resistance} = \frac{230}{12} = 19.17 \text{ A. (Ans.)}$$

Since the circuit is purely resistive, so currents will be in phase with their respective voltages and will be mutually 120° apart. Taking I_R as the reference vector (Fig. 64) the line currents are given as:

$$I_R = 28.75 = 28.75(1+j0)$$

$$I_Y = 23 - 120^\circ = 23 (-0.5 - j0.866)$$

$$I_B = 19.17 120^\circ = 19.17 (-0.5 + j0.866).$$

(ii) Current in neutral wire,

$$\begin{aligned} I_N &= -(I_R + I_Y + I_B) = -[28.75(1+j0) + 23(-0.5 - j0.866) + 19.17(-0.5 + j0.866)] \\ &= -[28.75 - 11.5 - j19.92 - 9.58 + j16.6] \end{aligned}$$

$$= -[7.67 - j3.32] = -7.67 + j3.32 = 8.357 156.6^\circ \text{ A. (Ans.)}$$

(iii) Total power absorbed

$$\begin{aligned} &= I_R^2 \times 8 + I_Y^2 \times 10 + I_B^2 \times 12 = 28.75^2 \times 8 + 23^2 \times 10 + 19.17^2 \times 12 \\ &= 6612.5 + 5290 + 4409.8 = 16312.3 \text{ W. (Ans.)} \end{aligned}$$

Example 50. A 440 V (line-to-line), 3-phase, 4-core supplies an unbalanced load represented by the following impedances in ohms connected between R, Y and B phases respectively and the neutral $8 + j6$, $7 - j10.5$ and 12.5 . Calculate:

- (i) Current in each conductor of the cable,
- (ii) Current in the neutral wire, and
- (iii) Readings of the three wattmeters connected in each line and neutral.

The phase sequence is RYB.

Solution. The potential differences across the three phases are:

$$E_{RN} = \frac{440}{\sqrt{3}} = 254 \angle 0^\circ$$

$$E_{YN} = 254 \angle -120^\circ$$

$$E_{BN} = 254 \angle 120^\circ$$

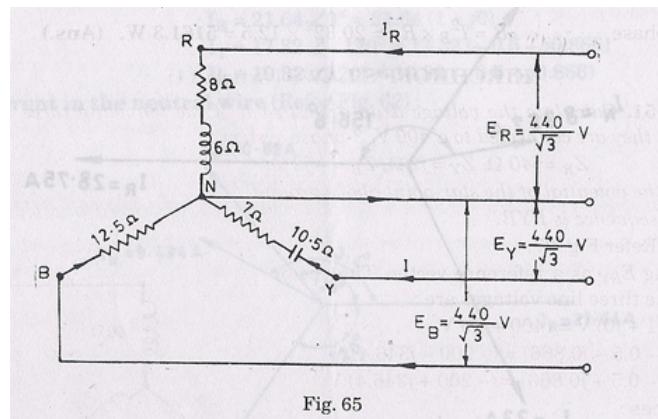


Fig. 65

Impedances:

$$Z_R = 8 + j6 = 10 \angle 36.9^\circ$$

$$Z_Y = 7 - j10.5 = 12.62 \angle -56.3^\circ$$

$$Z_B = 12.5 \angle 0^\circ$$

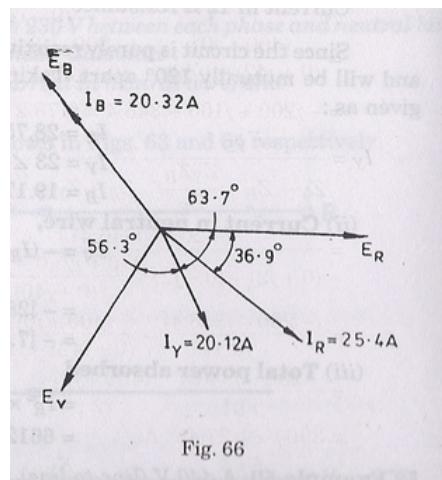


Fig. 66

(i) Phase currents:

$$I_R = I_{RN} = \frac{E_{RN}}{E_R} = \frac{254\angle 0^\circ}{10\angle 36.9^\circ} \\ = 25.4\angle -36.9^\circ \text{ A. (Ans.)}$$

$$I_Y = I_{YN} = \frac{E_{YN}}{Z_Y} = \frac{254\angle -120^\circ}{12.62\angle -56.3^\circ} \\ = 20.12\angle -63.7^\circ \text{ A. (Ans.)}$$

$$I_B = I_{BN} = \frac{E_{BN}}{Z_B} = \frac{254\angle 120^\circ}{12.5\angle 0^\circ} \\ = 20.32\angle 120^\circ \text{ A. (Ans.)}$$

(ii) Current in the neutral wire:

$$I_N = -(I_R + I_Y + I_B) \\ = -[25.4\angle -36.9^\circ + 20.12\angle -63.7^\circ + 20.32\angle 120^\circ] \\ = -[25.4(+0.8 - j0.6) + 20.12(0.44 - j0.896) + 20.32(-0.5 + j0.866)] \\ = -(20.32 - j15.24 + 8.85 - j18.03 - 10.16 + j17.6) \\ = -(19.01 - j15.67) = -19.01 + j15.67 = 24.64 \angle 39.5^\circ \text{ A. (Ans.)}$$

(iii) Readings of wattmeters:

$$\text{Power in phase, } R = I_R^2 \times R_R = 25.4^2 \times 8 = 5161.3 \text{ W. (Ans.)}$$

$$\text{Power in phase, } Y = I_Y^2 \times R_Y = 20.12^2 \times 7 = 2833.7 \text{ W. (Ans.)}$$

$$\text{Power in phase, } B = I_B^2 \times R_B = 20.32^2 \times 12.5 = 5161.3 \text{ W. (Ans.)}$$

KIRCHHOFF'S LAWS (Article 11)


Example 51. Calculate the voltage drop across each of the following three star-connected impedances when they are connected to a 400 V, 3-phase system:

$$Z_R = j40\Omega, Z_Y = j2\Omega, Z_B = -j2\Omega.$$

Also find the potential of the star-point above ground.

The phase sequence is RYB.

Solution. Refer Fig. 67.

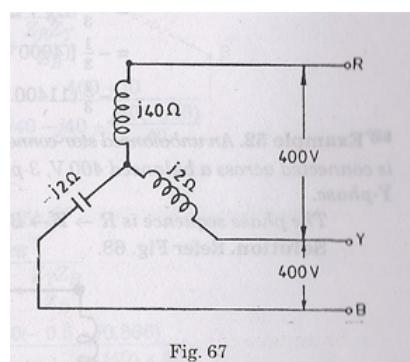

Considering E_{RY} as a reference vector. The vector expressions for the three line voltages are:

$$E_{RY} = 400(1 + j0) \text{ V} = (400 + j0) \text{ V}$$

$$E_{YB} = 400(-0.5 - j0.866) = (-200 - j346.4) \text{ V}$$

$$E_{BR} = 400(-0.5 + j0.866) = (-200 + j346.4) \text{ V}$$

Impedances:

$$Z_R = (0 + j40),$$

$$Z_Y = (0 + j2)$$

$$Z_B = (0 - j2)$$

Now for finding I_R , I_Y and I_B , using the relations:

$$\begin{aligned} I_R &= \frac{E_{RY}}{Z_R + Z_Y + \frac{Z_R Z_Y}{Z_B}} - \frac{E_{BR}}{Z_B + Z_R + \frac{Z_B Z_R}{Z_Y}} \\ &= \frac{400 + j0}{(0 + j40) + (0 + j2) + \frac{(0 + j40)(0 + j2)}{(0 - j2)}} - \frac{(-200 + j346.4)}{(0 - j2) + (0 + j40) + \frac{(0 - j2)(0 + j40)}{(0 + j2)}} \\ &= \frac{(400 + j0)}{(0 + j42) - j40} - \frac{(-200 + j346.4)}{(0 + j38) - j40} = \frac{400}{j2} - \frac{(-200 + j346.4)}{j2} \\ &= -j200 + j100 + 346.4 = (173.2 - j100)A \text{ or } 200 \angle -30^\circ A \end{aligned}$$

$$\begin{aligned} I_Y &= \frac{E_{YB}}{Z_Y + Z_B + \frac{Z_Y Z_B}{Z_R}} - \frac{E_{RY}}{Z_R + Z_Y + \frac{Z_R Z_Y}{Z_B}} \\ &= \frac{(-200 - j346.4)}{(0 + j2) + (0 - j2) + \frac{(0 + j2)(0 - j2)}{(0 + j40)}} - \frac{(400 + j0)}{(0 + j40) + (0 + j2) + \frac{(0 + j40)(0 + j2)}{(0 - j2)}} \\ &= \frac{(-200 - j346.4)}{-j0.1} - \frac{(400 + j0)}{(0 + j42) - j40} \\ &= \frac{-200 - j346.4}{-j0.1} - \frac{(400 + j0)}{j2} = j2000 + 3464 + j200 = 3464 - j1800 \\ &= 3904 \angle -27.45^\circ A \end{aligned}$$

$$\begin{aligned} I_B &= \frac{E_{BR}}{Z_B + Z_R + \frac{Z_B Z_R}{Z_Y}} - \frac{E_{YB}}{Z_Y + Z_B + \frac{Z_Y Z_B}{Z_R}} \\ &= \frac{(-200 + j346.4)}{(0 - j2) + (0 + j40) + \frac{(0 - j2)(0 + j40)}{(0 + j2)}} - \frac{(-200 - j346.4)}{(0 + j2) + (0 - j2) + \frac{(0 + j2)(0 - j2)}{(0 + j40)}} \\ &= \frac{(-200 - j346.4)}{j38 - j40} - \frac{(-200 - j346.4)}{-j0.1} = \frac{(-200 + j346.4)}{-j2} - \frac{(-200 - j346.4)}{-j0.1} \\ &= j100 - 173.2 + j2000 - 3464 = -3637.2 + j1900 = 4101 \angle 152.4^\circ A \end{aligned}$$

Voltage drops across impedances:

$$\text{Voltage drop, } E_R = I_R Z_R = (173.2 - j100) \times j40 = (4000 + j6928) \text{ V. (Ans.)}$$

$$\text{Voltage drop, } E_Y = I_Y Z_Y = (3464 - j1800)(j2) = (3600 + j6928) \text{ V. (Ans.)}$$

$$\text{Voltage drop, } E_B = I_B Z_B = (-3637.2 + j1900)(-j2) = (3800 + j7274.4) \text{ V. (Ans.)}$$

Potential of star point above ground:

$$= \frac{1}{3}(E_R + E_Y + E_B)$$


$$= \frac{1}{3}[(4000 + j6928) + (3600 + j6928) + (3800 + j7274.4)]$$

$$= \frac{1}{3}(11400 + j17656) = -(3800 + j7043.5) = -8003 \text{ V. (Ans.)}$$

Example 52. An unbalanced star-connected load shown in Fig. 68, $Z_R = j40 \Omega$, $Z_Y = -j40 \Omega$, $Z_B = 40 \Omega$ is connected across a balanced 400 V, 3-phase supply. Find the reading of the wattmeter connected in Y-phase.

The phase sequence is R → Y → B.

Solution. Refer Fig. 68.

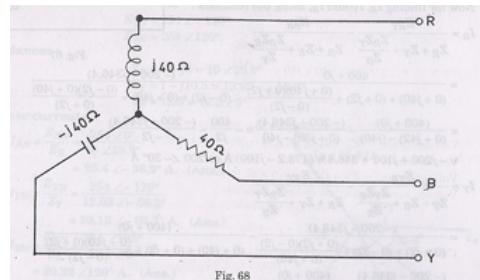

Taking E_{RY} as reference vector

$$E_{RY} = 400 \angle 0^\circ = 400(1 + j0)$$

$$E_{YB} = 400 \angle -120^\circ = 400(-0.5 - j0.866)$$

$$E_{BR} = 400 \angle 120^\circ = 400(-0.5 + j0.866)$$

Impedances are

$$Z_R = (0 + j40), Z_Y = (0 - j40), Z_B = (40 + j0)$$

$$\begin{aligned}
 I_R &= \frac{E_{RY}}{Z_R + Z_Y + \frac{Z_R Z_Y}{Z_B}} - \frac{E_{BR}}{Z_B + Z_R + \frac{Z_R Z_B}{Z_Y}} \\
 &= \frac{(400 + j0)}{j40 + j40 + \frac{j40 \times (-j40)}{40}} - \frac{400(-0.5 + j0.866)}{40 + j40 + \frac{40 \times j40}{-j40}} \\
 &= \frac{400}{40} - \frac{-200 + j346.4}{40 + j40 - 40} \\
 &= 10 - \frac{-200 + j346.4}{j40} = 10 - \frac{+j200 - j346.4}{40} \\
 &= 10 - j5 + 8.66 = (1.34 - j5)A
 \end{aligned}$$

$$\begin{aligned}
 I_Y &= \frac{E_{YB}}{Z_Y + Z_B + \frac{Z_Y Z_B}{Z_R}} - \frac{E_{RY}}{Z_R + Z_Y + \frac{Z_R Z_Y}{Z_B}} \\
 &= \frac{400(-0.5 + j0.866)}{-j40 + 40 + \frac{(-j40) \times 40}{j40}} - \frac{400 + j0}{j40 - j40 + \frac{j40(-j40)}{40}} \\
 &= \frac{-200 - j346.4}{-j40 + 40 - 40} - \frac{400 + j0}{40} \\
 &= j5 + 8.66 - 10 = (-1.34 - j5)A
 \end{aligned}$$

$$\begin{aligned}
 I_B &= \frac{E_{BR}}{Z_B + Z_R + \frac{Z_B Z_R}{Z_Y}} - \frac{E_{YB}}{Z_Y + Z_B + \frac{Z_Y Z_B}{Z_R}} \\
 &= \frac{400(0.5 + j0.866)}{40 + j40 + \frac{40 \times j40}{-j40}} - \frac{400(-0.5 - j0.866)}{-j40 + 40 + \frac{(-j40) \times 40}{j40}} \\
 &= \frac{200 + j346.4}{40 + j40 - 40} - \frac{-200 - j346.4}{-j40 + 40 - 40} = \frac{200 + j346.4}{j40} = \frac{-200 - j346.4}{-j40} \\
 &= 8.66 + j5 + j5 - 8.66 = j10 A
 \end{aligned}$$

Voltage drop, $E_R = I_R Z_R = (1.34 - j5) \times j40 = (200 + j53.6) V$

Voltage drop, $E_Y = I_Y Z_Y = (-1.34 - j5) \times (-j40) = (-200 + j53.6) V$

Voltage drop, $E_B = I_B Z_B = j10 \times 40 = (0 + j400) V$

Voltage cross potential coil of wattmeter

= voltage between supply neutral and load neutral

$$= \frac{1}{3} (E_R + E_Y + E_B) = \frac{1}{3} (200 + j53.6 - 200 + j53.6 + j400) = j169 V$$

Current through wattmeter current coil \times conjugate of voltage across wattmeter potential coil
 $= I_Y \times (-j169) = (-1.34 - j5) \times (-j169) = (-845 + j226.5)$

\therefore Wattmeter reading == - 845 W. (Ans.)

STAR-DELTA CONVERSION

Example 53. An unbalanced star-connected load has branch impedances of $Z_R = 10 \angle 30^\circ \Omega$, $Z_Y = 20 \angle 45^\circ \Omega$ and $Z_B = 20 \angle 60^\circ \Omega$ and is connected across a balanced 3-phase, 3-wire supply of 440 V. Find:

- Line currents, and
 - Voltage across each impedance
- Use star=delta conversion method.

Solution. Taking E_{RY} are reference vector

Then $E_{RY} = 440 \angle 0^\circ$

$E_{YB} = 440 \angle -120^\circ$

$E_{BR} = 440 \angle 120^\circ$

Refer Fig.69

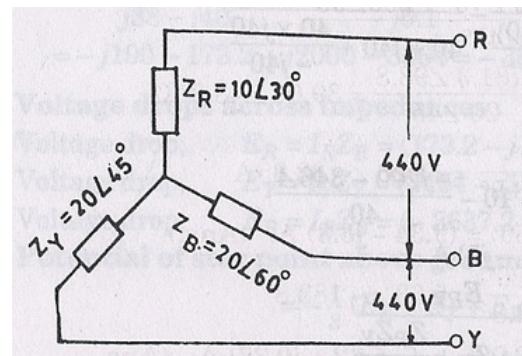


Fig. 69 (a)

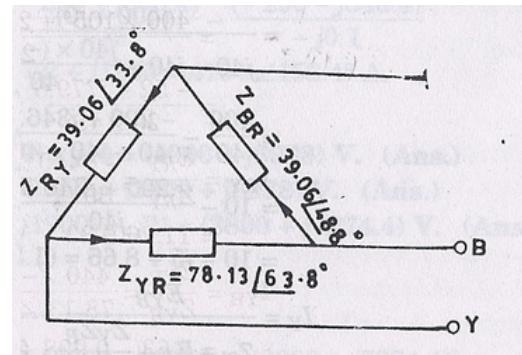


Fig. 69 (b)

$$\text{Also } Z_R = 10 \angle 30^\circ \quad (\text{given})$$

$$Z_Y = 20 \angle 45^\circ \quad (\text{given})$$

$$Z_B = 20 \angle 60^\circ \quad (\text{given})$$

Impedances of equivalent delta-connected load (Refer Fig.69):

$$\begin{aligned} \text{Now } Z_{RY} &= Z_R + Z_Y + \frac{Z_R Z_Y}{Z_B} = \frac{Z_R Z_B + Z_Y Z_B + Z_R Z_Y}{Z_B} \\ &= \frac{(10 \angle 30^\circ)(20 \angle 60^\circ) + (20 \angle 45^\circ)(20 \angle 60^\circ) + (10 \angle 30^\circ)(20 \angle 45^\circ)}{20 \angle 60^\circ} \end{aligned}$$

$$\begin{aligned}
&= \frac{200\angle 90^\circ + 400\angle 105^\circ + 200\angle 75^\circ}{20\angle 60^\circ} \\
&= \frac{200(0 + j1) + 400(-0.26 + j0.966) + 200(0.26 + j0.966)}{20\angle 60^\circ} \\
&= \frac{j200 - 104 + j386.4 + 52 + j193.2}{20\angle 60^\circ} \\
&= \frac{-52 + j779.6}{20\angle 60^\circ} = \frac{731.3\angle 93.8^\circ}{20\angle 60^\circ} = 39.06\angle 33.8^\circ \Omega
\end{aligned}$$

$$Z_{YB} = Z_Y + Z_B + \frac{Z_Y Z_B}{Z_R} = \frac{Z_Y Z_R + Z_B Z_R + Z_Y Z_B}{Z_R}$$

$$= \frac{(20\angle 45^\circ)(10\angle 30^\circ) + (20\angle 60^\circ)(10\angle 30^\circ) + (20\angle 45^\circ)(20\angle 60^\circ)}{10\angle 30^\circ}$$

$$= \frac{200\angle 75^\circ + 200\angle 90^\circ + 400\angle 105^\circ}{10\angle 30^\circ}$$

$$= \frac{200(0.62 + j0.966) + j200 + 400(-0.26 + j0.966)}{10\angle 30^\circ}$$

$$= \frac{52 + j193.2 + j200 - 104 + j386.4}{10\angle 30^\circ}$$

$$= \frac{-52 + j779.6}{10\angle 30^\circ} = \frac{781.3\angle 93.8^\circ}{10\angle 30^\circ} = 78.13\angle 63.8^\circ \Omega$$

$$Z_{YB} = Z_Y + Z_B + \frac{Z_Y Z_B}{Z_R} = \frac{Z_Y Z_R + Z_B Z_R + Z_Y Z_B}{Z_R}$$

$$= \frac{(20\angle 45^\circ)(10\angle 30^\circ) + (20\angle 60^\circ)(10\angle 30^\circ) + (20\angle 45^\circ)(20\angle 60^\circ)}{10\angle 30^\circ}$$

$$= \frac{200\angle 75^\circ + 200\angle 90^\circ + 400\angle 105^\circ}{10\angle 30^\circ}$$

$$= \frac{200(0.62 + j0.966) + j200 + 400(-0.26 + j0.966)}{10\angle 30^\circ}$$

$$= \frac{52 + j193.2 + j200 - 104 + j386.4}{10\angle 30^\circ}$$

$$= \frac{-52 + j779.6}{10\angle 30^\circ} = \frac{781.3\angle 93.8^\circ}{10\angle 30^\circ} = 78.13\angle 63.8^\circ \Omega$$

$$Z_{BR} = Z_B + Z_R + \frac{Z_B Z_R}{Z_Y} = \frac{Z_B Z_Y + Z_R Z_Y + Z_B Z_R}{Z_Y}$$

$$= \frac{(20\angle 60^\circ)(20\angle 45^\circ) + (10\angle 30^\circ)(20\angle 45^\circ) + (20\angle 60^\circ)(10\angle 30^\circ)}{20\angle 45^\circ}$$

$$= \frac{400\angle 105^\circ + 200\angle 75^\circ + 200\angle 90^\circ}{20\angle 45^\circ}$$

$$= \frac{-52 + j779.6}{20\angle 45^\circ} = \frac{781.3\angle 93.8^\circ}{20\angle 45^\circ} = 39.06\angle 48.8^\circ \Omega$$

$$I_{RY} = \frac{E_{RY}}{Z_{RY}} = \frac{440\angle 0^\circ}{39.06\angle 33.8^\circ} = 11.26\angle -33.8^\circ A$$


$$= 11.26(0.83 - i0.56) = (9.34 - i6.3)A. \quad (\text{Ans.})$$

$$I_{YB} = \frac{E_{YB}}{Z_{YR}} = \frac{440\angle -120^\circ}{78.13\angle 63.8^\circ} = 5.63\angle -183.8^\circ A$$

$$= 5.63(-0.998 + j0.066) = (-5.62 - j0.37)A. \text{ (Ans.)}$$

$$I_{BR} = \frac{E_{BR}}{Z_{RR}} = \frac{440\angle 120^\circ}{39.06\angle 48.8^\circ} = 11.26\angle 71.2^\circ A$$
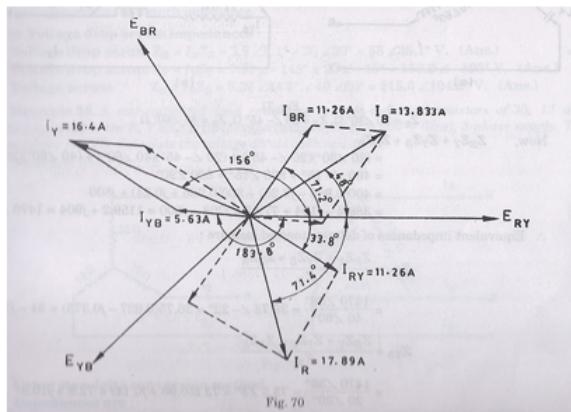
$$= 11.26(0.322 + j0.947) = (3.625 - j10.66)A. \text{ (Ans.)}$$



(i) Line currents:

$$I_R = I_{RY} - I_{BR} = (9.34 - j6.3) - (3.625 + j10.66)$$

$$= 5.715 - j16.96 = 17.89 - 71.4^\circ A. \text{ (Ans.)}$$

$$I_Y = I_{YB} - I_{RY} = (-5.62 + j0.37) - (9.34 - j6.3)$$

$$= -14.96 + j6.67 = 16.4 156^\circ A. \text{ (Ans.)}$$

$$I_B = I_{BR} - I_{YB} = (3.625 + j10.66) - (-5.62 + j0.37)$$

$$= 9.245 + j10.29 = 13.833 48^\circ A. \text{ (Ans.)}$$

These are the currents in the phases of the star-connected unbalanced load. Let us find voltage drop across each star-connected branch impedance.

(ii) Voltage across impedances :

$$\text{Voltage across } Z_R = I_R \times Z_R$$

$$= 17.89 - 71.4^\circ \times 10 30^\circ = 178.9 - 41.4^\circ V. \text{ (Ans.)}$$

$$\text{Voltage across } Z_Y = I_Y \times Z_Y = 16.4 156^\circ \times 20 45^\circ$$

$$= 328 L210^\circ V. \text{ (Ans.)}$$

$$\text{Voltage across } Z_B = I_B \times Z_B = 13.833 48^\circ \times 20 60^\circ$$

$$= 276.67 108^\circ V. \text{ (Ans.)}$$

The phasor diagram is shown in Fig. 70.

Example 54. The branch impedances of an unbalanced star-connected load are: $Z_R = 20 30^\circ \Omega$, $Z_Y = 20 - 45^\circ \Omega$, $Z_B = 40 60^\circ \Omega$. It is connected across a balanced 3-phase, 3-wire supply of 200 V. Find:

(i) Line currents, and

(ii) Voltage across each impedance.

(iii) Use star-delta conversion method.

Solution. The unbalanced star-connected load and its equivalent delta-connected load are shown in Fig. 71.

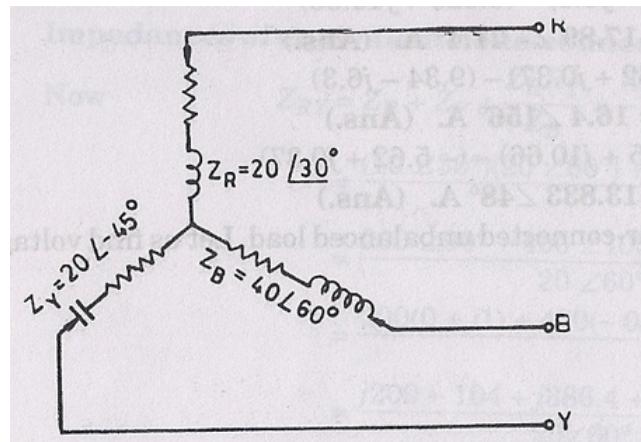


Fig. 71 (a)

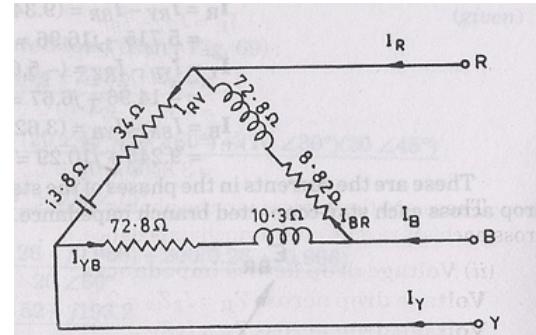


Fig. 71 (b)

$$Z_R = 20 \angle 30^\circ \Omega, Z_Y = 20 \angle -45^\circ \Omega, Z_B = 40 \angle 60^\circ \Omega$$

$$\text{Now } Z_R Z_Y + Z_Y Z_B + Z_B Z_R$$

$$= (20 \angle 30^\circ)(20 \angle -45^\circ) + (20 \angle -45^\circ)(40 \angle 60^\circ) + (40 \angle 60^\circ)(20 \angle 30^\circ)$$

$$= 400 \angle -15^\circ + 800 \angle 15^\circ + 800 \angle 90^\circ$$

$$= 400(0.966 - j0.26) + 800(0.966 + j0.24) + j800$$

$$= 386.4 - j104 + 772.8 + j208 + j800 = 1159.2 + j904 = 1470 \angle 38^\circ$$

Equivalent impedances of delta-connected load are:

$$Z_{RY} = \frac{Z_R Z_Y + Z_Y Z_B + Z_B Z_R}{Z_B}$$

$$= \frac{1470 \angle 38^\circ}{40 \angle 60^\circ} = 36.75 \angle -22^\circ = 36.75(0.927 - j0.375) = 34 - j13.8$$

$$Z_{YB} = \frac{Z_R Z_Y + Z_Y Z_B + Z_B Z_R}{Z_R}$$

$$= \frac{1470 \angle 38^\circ}{20 \angle 30^\circ} = 73.5 \angle 8^\circ = 73.5(0.99 - j0.14) = 72.8 + j10.3$$

$$Z_{BR} = \frac{Z_R Z_Y + Z_Y Z_B + Z_B Z_R}{Z_Y}$$

$$= \frac{1470 \angle 38^\circ}{20 \angle -45^\circ} = 73.5 \angle 83^\circ = 73.5(0.12 - j0.99) = 8.82 + j72.8$$

Taking E_{RY} as the difference vector and assuming sequence as $R \rightarrow Y \rightarrow B$,

$$E_{RY} = 200 \angle 0^\circ, E_{YB} = 200 \angle -120^\circ, E_{BR} = 200 \angle 120^\circ$$

$$E_{RY} = 200 \angle 0^\circ, E_{YB} = 200 \angle -120^\circ, E_{BR} = 200 \angle 120^\circ$$

$$I_{RY} = \frac{E_{RY}}{Z_{RY}} = \frac{200 \angle 0^\circ}{36.75 \angle -22^\circ} = 5.44 \angle 22^\circ$$

$$= 5.44(0.927 + j0.375) = 5.04 + j2.04$$

$$I_{YB} = \frac{E_{YB}}{Z_{YB}} = \frac{200 \angle -120^\circ}{73.5 \angle 8^\circ} = 2.72 \angle -128^\circ$$

$$= 2.72(-0.616 - j0.79) = -1.67 - j2.15$$

$$I_{BR} = \frac{E_{BR}}{Z_{BR}} = \frac{200 \angle 120^\circ}{73.5 \angle 83^\circ} = 2.72 \angle 37^\circ = 2.72(0.8 + j0.6) = 2.17 + j1.63$$

(i) Line Currents:

$$I_R = I_{RY} - I_{BR}$$

$$= (5.04 + j2.04) - (2.17 + j1.63) = 2.87 + j0.41 = 2.9 \angle 8.1^\circ \text{ A. (Ans.)}$$

$$I_Y = I_{YB} - I_{RY} = (-1.67 - j2.15) - (5.04 + j2.04)$$

$$= -6.71 - j4.19 = 7.91 \angle -148^\circ \text{ A. (Ans.)}$$

$$I_B = I_{BR} - I_{YB} = (2.17 + j1.63) - (-1.67 - j2.15)$$

(ii) Line Currents:

$$I_R = I_{RY} - I_{BR}$$

$$= (5.04 + j2.04) - (2.17 + j1.63) = 2.87 + j0.41 = 2.9 \angle 8.1^\circ \text{ A. (Ans.)}$$

$$I_Y = I_{YB} - I_{RY} = (-1.67 - j2.15) - (5.04 + j2.04)$$

$$= -6.71 - j4.19 = 7.91 \angle -148^\circ \text{ A. (Ans.)}$$

$$I_B = I_{BR} - I_{YB} = (2.17 + j1.63) - (-1.67 - j2.15)$$

$$= 3.84 + j3.78 = 5.39 \text{ } 44.5^\circ \text{ A. (Ans.)}$$

These are the currents in the phases of star-connected unbalanced load. Let us find the drop across each star-connected branch impedance.

(ii) Voltage drop across impedances:

$$\text{Voltage drop across } Z_R = I_R Z_R = 2.9 \text{ } 8.1^\circ \times 20 \text{ } 30^\circ = 58 \text{ } 38.1^\circ \text{ V. (Ans.)}$$

$$\text{Voltage drop across } Z_Y = I_Y Z_Y = 7.91 \text{ } -148^\circ \times 20 \text{ } -45^\circ = 158.2 \text{ } -193^\circ \text{ V. (Ans.)}$$

$$\text{Voltage across } Z_B = I_B Z_B = 5.39 \text{ } 44.5^\circ \times 40 \text{ } 60^\circ = 215.6 \text{ } 104.5^\circ \text{ V. (Ans.)}$$

Example 55. A star-connected load consisting of non-inductive resistors of 30, 12 and 20 ohms connected to the R, Y and B lines respectively is fed by a 300 V (line), 3-phase supply. The phase sequence is RYB. Calculate the voltage across each resistor.

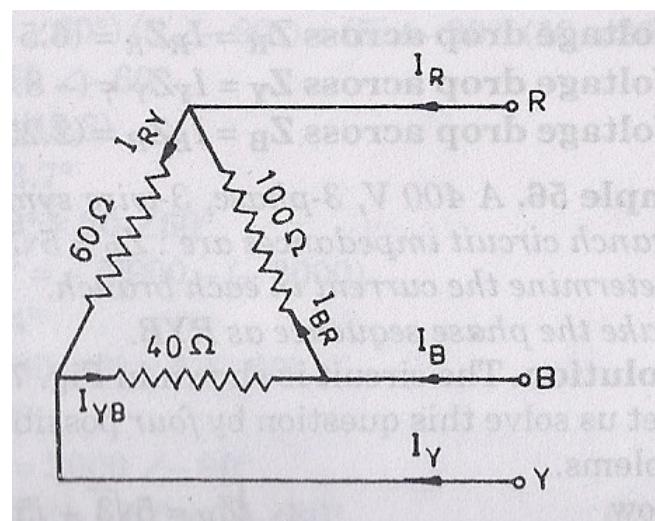
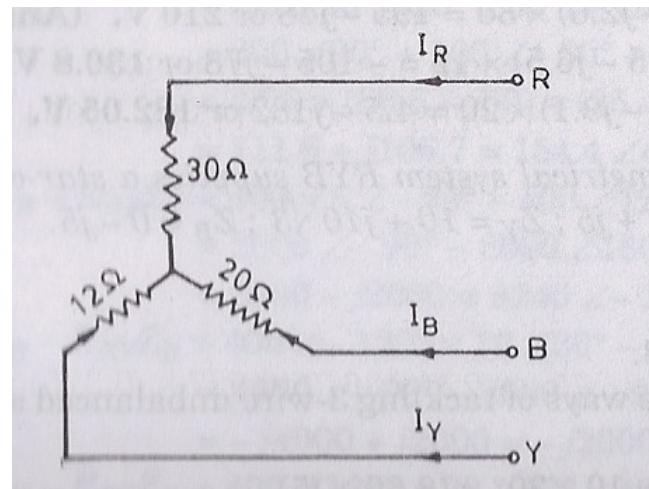


Fig.72

Using star-delta conversion method,

Impedances are :

$$Z_R = 30 \Omega, Z_Y = 12 \Omega, Z_B = 20 \Omega$$

$$\text{Now } Z_R Z_Y + Z_Y Z_B + Z_B Z_R = 30 \times 12 + 12 \times 20 + 20 \times 30 = 360 + 240 + 600 = 1200 \Omega$$

Equivalent impedances of delta-connected load are:

$$Z_{RY} = \frac{Z_R Z_Y + Z_Y Z_B + Z_B Z_R}{Z_R} = \frac{1200}{20} = 60 \Omega$$

$$Z_{YB} = \frac{Z_R Z_Y + Z_Y Z_B + Z_B Z_R}{Z_Y} = \frac{1200}{30} = 40 \Omega$$

$$Z_{BR} = \frac{Z_R Z_Y + Z_Y Z_B + Z_B Z_R}{Z_B} = \frac{1200}{12} = 100 \Omega$$

Phase currents are:

$$I_{RY} = \frac{E_{RY}}{Z_{RY}} = \frac{300}{60} = 5 A$$

$$I_{YB} = \frac{E_{YB}}{Z_{YB}} = \frac{300}{40} = 7.5 A$$

$$I_{BR} = \frac{E_{BR}}{Z_{BR}} = \frac{300}{100} = 3 A$$

Each current is in phase with its own voltage because the load is purely resistive.

To find line currents for delta-connection using vector algebra and choosing E_{RY} as the reference axis, we get

$$I_{RY} = 5 + j0$$

$$I_{YB} = 7.5(-0.5 - j0.866) = -3.75 - j6.5$$

$$I_{BR} = 3(-0.5 + j0.866) = -1.5 + j2.6$$

Line currents for delta-connection are:

$$I_R = I_{RY} - I_{BR}$$

$$= (5 + j0) - (-1.5 + j2.6) = (6.5 - j2.6) \text{ or } 7 A \text{ in magnitude}$$

$$I_Y = I_{YB} - I_{RY}$$

$$= (-3.75 - j6.5) - (5 + j0) = -8.75 - j6.5 \text{ or } 10.9 \text{ A in magnitude}$$

$$I_B = I_{BR} = I_{YB} = (-1.5 + j2.6) - (-3.75 - j6.5)$$

$$= 2.25 - j9.1 \text{ or } 9.37 \text{ A in magnitude}$$

These line currents for delta-connection are the phase currents for star-connection.

Voltage drop across each limb of star-connected load is :

$$\text{Voltage drop across } Z_R = I_R Z_R = (6.5 - j2.6) \times 30 = 195 - j78 \text{ or } 210 \text{ V. (Ans.)}$$

$$\text{Voltage drop across } Z_Y = I_Y Z_Y = (-8.75 - j6.5) \times 12 = -105 - j78 \text{ or } 130.8 \text{ V. (Ans.)}$$

$$\text{Voltage drop across } Z_B = I_B Z_B = (2.25 - j9.1) \times 20 = 4.5 - j182 \text{ or } 182.05 \text{ V. (Ans.)}$$

Example 56. A 400 V, 3-phase, 3-wire symmetrical system R_{YB} supplies a star-connected load whose branch circuit impedances are: $Z_R = 5\sqrt{3} + j5$; $Z_Y = 10 + j10\sqrt{3}$; $Z_B = 0 - j5$.

Determine the current in each branch.

Take the phase sequence as RYB.

Solution. The circuit is shown in Fig. 73.

Let us solve this question by four possible ways of tackling 3-wire unbalanced star-connected load problems.

$$\text{Now } Z_R = 5\sqrt{3} + j5 = 10\angle 30^\circ = (8.66 + j5)$$

$$Z_Y = 10 + j10\sqrt{3} = 20\angle 60^\circ = (10 + j17.32)$$

$$Z_B = 0 - j5 = 5\angle -90^\circ = -j5$$

$$\text{Also, let } E_{RY} = 400\angle 0^\circ = (400 + j0)$$

$$E_{YB} = 400\angle -120^\circ = (-200 - j346)$$

$$E_{BR} = 400\angle 120^\circ = (-200 + j346)$$

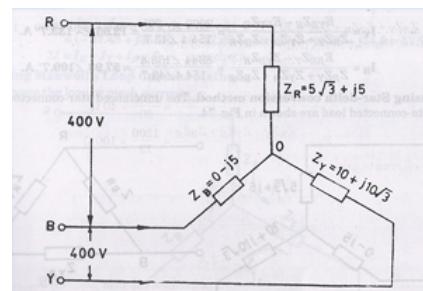


Fig.73

1. By using Kirchhoff's law :

We know that

We know that

$$I_R = \frac{E_{RY}}{Z_R + Z_Y + \frac{Z_R Z_Y}{Z_B}} - \frac{E_{BR}}{Z_B + Z_R + \frac{Z_B Z_R}{Z_Y}}$$

$$= \frac{E_{RY} Z_B}{Z_R Z_B + Z_Y Z_B + Z_R Z_Y} - \frac{E_{BR} Z_Y}{Z_{RY} + Z_{YB} + Z_{BR}} \quad \dots (i)$$

$$I_Y = \frac{E_{YB} Z_Y}{Z_R Z_Y + Z_Y Z_B + Z_B Z_R} - \frac{E_{RY} Z_B}{Z_{RY} + Z_{YB} + Z_{BR}} \quad \dots (ii)$$

and $I_B = \frac{E_{BR} Z_Y}{Z_R Z_Y + Z_Y Z_B + Z_B Z_R} - \frac{E_{RY} Z_B}{Z_{RY} + Z_{YB} + Z_{BR}} \quad \dots (iii)$

Now $Z_R Z_Y + Z_Y Z_B + Z_B Z_R$

$$= (10 \angle 30^\circ) (20 \angle 60^\circ) + (20 \angle 60^\circ) (5 \angle -90^\circ) + (5 \angle -90^\circ) (10 \angle 30^\circ)$$

$$= 200 \angle 90^\circ + 100 \angle -30^\circ + 50 \angle -60^\circ$$

$$= j200 + (86.6 - j50) + (25 - j43.3)$$

$$= 111.6 + j106.7 = 154.4 \angle 43.7^\circ$$

$$E_{RY} Z_B - E_{BR} Z_Y = 400 \angle 5 \angle -90^\circ - 400 \angle 120^\circ \times 20 \angle 60^\circ$$

$$= 2000 \angle -90^\circ - 8000 \angle 180^\circ = -j2000 - (-8000)$$

$$= 8000 - j2000 = 8246 \angle -14^\circ$$

$$E_{YB} Z_R - E_{RY} Z_B = 400 \angle -120^\circ \times 10 \angle 30^\circ - 400 \angle 0^\circ \times 5 \angle -90^\circ$$

$$= 4000 \angle -90^\circ - 2000 \angle -90^\circ$$

$$= -j4000 + j2000 = -j2000 = 2000 \angle -90^\circ$$

$$E_{BR} Z_Y - E_{YB} Z_R = 400 \angle 120^\circ \times 20 \angle 60^\circ - 400 \angle -120^\circ \times 10 \angle 30^\circ$$

$$= 8000 \angle 180^\circ - 4000 \angle -90^\circ = -8000 + j4000 = 8944 \angle 153.4^\circ$$

Current in each branch [from (i), (ii) and (iii)]

$$I_R = \frac{E_{RY} Z_B - E_{BR} Z_Y}{Z_R Z_Y + Z_Y Z_B + Z_B Z_R} = \frac{8246 \angle -14^\circ}{154.4 \angle 43.7^\circ} = 53.4 \angle -57.7^\circ A. \quad (Ans.)$$

$$I_Y = \frac{E_{YB} Z_R - E_{RY} Z_B}{Z_R Z_Y + Z_Y Z_B + Z_B Z_R} = \frac{2000 \angle -90^\circ}{154.4 \angle 43.7^\circ} = 12.95 \angle -133.7^\circ A. \quad (Ans.)$$

$$I_B = \frac{E_{BR} Z_Y - E_{YB} Z_R}{Z_R Z_Y + Z_Y Z_B + Z_B Z_R} = \frac{8944 \angle 153.4^\circ}{154.4 \angle 43.7^\circ} = 57.93 \angle -109.7^\circ A. \quad (Ans.)$$

2. By using Star-delta conversion method: The unbalanced star-connected load and its equivalent delta-connected load are shown in Fig 74.

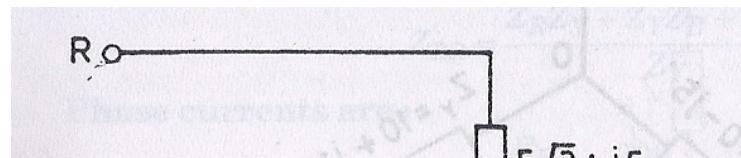


Fig.74 (a)

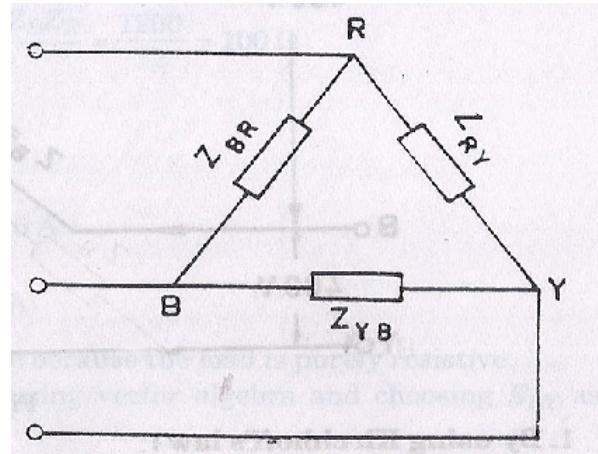


Fig.74 (b)

$$\text{Now, } Z_R Z_Y + Z_Y Z_B + Z_B Z_R = 154.4 \angle 43.7^\circ$$

[Already calculated]

Equivalent delta-connected impedances are:

$$Z_{RY} = \frac{Z_R Z_Y + Z_Y Z_B + Z_B Z_R}{Z_B} = \frac{154.4 \angle 43.7^\circ}{5 \angle -90^\circ} = 30.88 \angle 133.7^\circ$$

$$Z_{YB} = \frac{Z_R Z_Y + Z_Y Z_B + Z_B Z_R}{Z_R} = \frac{154.4 \angle 43.7^\circ}{10 \angle 30^\circ} = 15.44 \angle 13.7^\circ$$

$$Z_{BR} = \frac{Z_R Z_Y + Z_Y Z_B + Z_B Z_R}{Z_Y} = \frac{154.4 \angle 43.7^\circ}{20 \angle 60^\circ} = 7.72 \angle -16.3^\circ$$

Phase currents are:

$$I_{RY} = \frac{E_{RY}}{Z_{RY}} = \frac{400 \angle 0^\circ}{30.88 \angle 133.7^\circ} = 12.95 \angle -133.7^\circ = (-8.95 - j9.36)$$

$$I_{YB} = \frac{E_{YB}}{Z_{YB}} = \frac{400 \angle -120^\circ}{15.44 \angle 13.7^\circ} = 25.9 \angle -133.7^\circ = (-17.89 - j18.75)$$

$$I_{BR} = \frac{E_{BR}}{Z_{BR}} = \frac{400 \angle 120^\circ}{7.75 \angle -16.3^\circ} = 51.8 \angle 136.3^\circ = (-37.45 + j35.78)$$

Line currents for delta-connection are:

$$I_R = I_{RY} - I_{BR}$$

$$= (-8.95 - j9.36) - (-37.45 + j35.78)$$

$$= 28.5 - j15.11 = \mathbf{53.38 \angle 57.7^\circ A. (Ans.)}$$

$$I_Y = I_{YB} - I_{RY}$$

$$= (-17.89 - j18.75) - (-8.95 - j9.36)$$

$$= -8.94 - j9.36 = 12.94 \angle 133.7^\circ$$

$$I_B = I_{BR} - I_{YB}$$

$$= (-37.45 + j35.78) - (-17.89 - j18.75) = -19.56 + j54.5 = 57.9 \angle 109.7^\circ$$

$$\Sigma I = I_R + I_Y + I_B = 0 \dots \text{as a check.}$$

3. By using Maxwell's Loop Current Method:

Fig. 75 shows the loop or mesh currents.

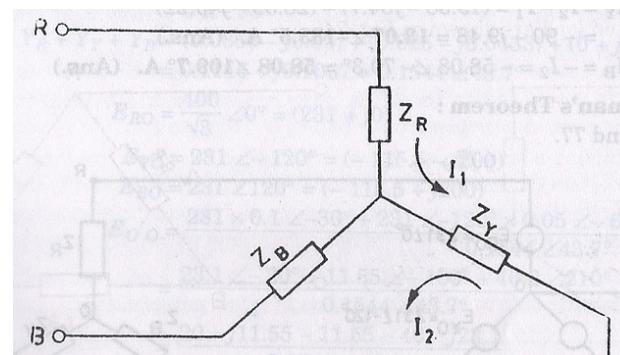


Fig. 75

It may be noted that $I_R = I_1$

$$I_Y = I_2 - I_1$$

$$\text{and} \quad I_B = -I_2$$

Considering drops across R and Y arms, we get

$$I_1 Z_R + Z_Y (I_1 - I_2) = E_{RY}$$

$$\text{or} \quad I_1 (Z_R + Z_Y) - I_2 Z_Y = E_{RY} \quad \dots(i)$$

Similarly, considering the arms Y and B, we have

$$(I_2 - I_1) Z_Y + I_2 Z_B = E_{YB}$$

$$-I_1 Z_Y + I_2 (Z_Y + Z_B) = E_{YB}$$

Solving for I_1 and I_2 , we get

... (ii)

$$I_1 = \frac{E_{RY}(Z_Y + Z_B) + E_{YB}Z_Y}{(Z_R + Z_Y)(Z_Y + Z_B) - Z_Y^2}$$

$$I_2 = \frac{E_{YB}(Z_R + Z_Y) + E_{RY}Z_Y}{(Z_R + Z_Y)(Z_Y + Z_B) - Z_Y^2}$$

$$I_1 = \frac{400(10 + j12.32) + 400\angle -120^\circ \times 20\angle 60^\circ}{(18.66 + j22.32)(10 + j12.32) - 400\angle 120^\circ}$$

$$= \frac{4000 + j4928 + 4000 - j6928}{(186.6 + j229.9 + j223.2 - 275) - (-200 + j346.4)}$$

$$= \frac{8000 - j2000}{111.6 + j106.7} = \frac{8246.2\angle -14^\circ}{154\angle 43.7^\circ}$$

$$= 53.5\angle 57.7^\circ = (28.59 - j45.22)$$

$$I_2 = \frac{(-200 - j346)(18.66 + j22.32) + 400(10 + j17.32)}{111.6 + j106.7}$$

$$= \frac{-373.2 - j4464 - j6456.4 + 7723 + 4000 + j6928}{111.6 + j106.7}$$

$$= \frac{8000 - j4000}{111.6 + j106.7} = \frac{8944\angle -26.6^\circ}{154\angle 43.7^\circ} = 58.08\angle -70.3^\circ = 19.58 - j54.7$$

$$I_R = I_1 = \mathbf{53.5 - 57.7^\circ A. (Ans.)}$$

$$I_Y = I_2 - I_1 = (19.58 - j54.7) - (28.59 - j45.22)$$

$$= -90 - j9.48 = \mathbf{13.07 - 133.5^\circ A. (Ans.)}$$

$$I_B = -I_2 = -58.08 - 70.3^\circ = \mathbf{58.08 109.7^\circ A. (Ans.)}$$

4. Using Millman's Theorem:

Refer Figs. 76 and 77.

According to Milliman's theorem, the voltage of the *load* star point $0'$ with respect to the star point or neutral 0 of the generator or supply (normally zero potential) is given by

$$E_{o'0} = \frac{E_{RO}Y_R + E_{YO}Y_Y + E_{BO}Y_B}{Y_R + Y_Y + Y_B}$$

where E_{RO} , E_{YO} and E_{BO} are the phase voltages of the generator or 3-phase supply.

Voltage across each phase of the load is

$$E_{RO'} = E_{RO} - E_{O'0}$$

$$E_{YO'} = E_{YO} - E_{O'0}$$

$$E_{BO'} = E_{BO} - E_{O'0}$$

$$\text{Now, } I_{RO'} = (E_{RO} - E_{O'0}) Y_Y$$

$$I_{YO'} = (E_{YO} - E_{O'0}) Y_Y$$

$$I_{BO'} = (E_{BO} - E_{O'0}) Y_B$$

$$\text{Here, } Y_R = \frac{1}{10\angle 30^\circ} = 0.1 \angle -30^\circ = (0.866 - j0.05)$$

$$v = \frac{1}{0.05 \angle -60^\circ} = (0.025 + j0.0125)$$

Search for: Search

Recent Posts

- [Why is it Necessary to Choose Assignment Help Solution?](#)
- [Why Look for Chemistry Homework Help?](#)
- [English and Education in Every Country Goes Parallel in Every Grade](#)
- [Use of Electrical Equipment in Commercial and Private Organisations](#)
- [Demand of Electrical Equipment in the Various Ways and Patterns](#)

Recent Comments

Archives

- [May 2014](#)
- [January 2014](#)
- [November 2013](#)
- [October 2013](#)
- [March 2013](#)

Categories

- [Blog](#)

Meta

- [Log in](#)
- [Entries RSS](#)
- [Comments RSS](#)
- [WordPress.org](#)



Copyright © 2012-18 Electrical-engineering-assignment.com All Rights Reserved | [FAQ](#) | [Privacy Policy](#) | [Terms & Conditions](#) | [Electrical Engineering Homework Help](#)

[Back to Top](#)