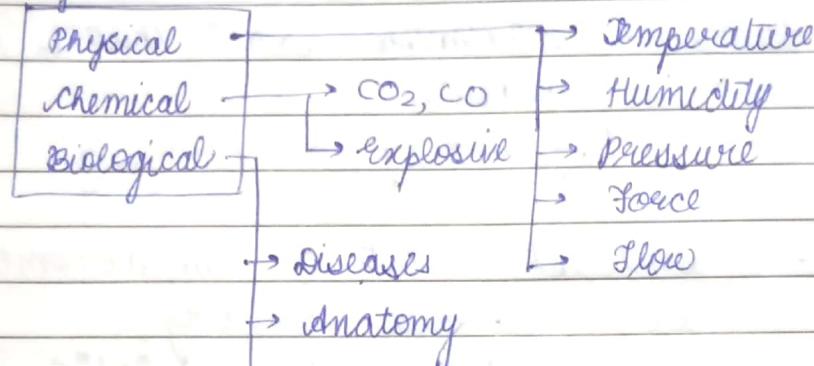
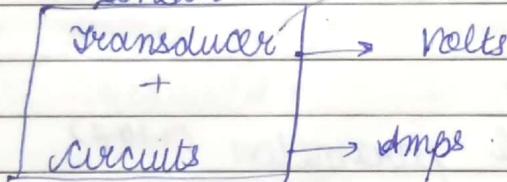


Chapter 1sensorPhysical Domainsensor

page converts one form of energy to other

actuator

opposite of transducer

electrical input & physical output

e.g. → Motor, relay

A sensor is always a transducer but vice versa is not always true.

- Table 1.1 in book

accelerometer

(measures acceleration)

$$F = m a$$

measures force & as m is constant, we get acc.



- capacitive accelerometer

Parameters in accelerometer:-

1. Dynamic range - Maximum "acc" that it can measure.

Range $\rightarrow \pm 1g : \pm 2g, \pm 5g, \pm 16g$

2. Resolution / \rightarrow smallest unit of measurement it sensitivity can measure reliably

e.g. \rightarrow Thermometer $\rightarrow 0.1^\circ C$ is resolution

unit of resolution is same as that of dynamic range.

3. Sensitivity to external parameters (1.10.2)

unit depends on external parameter

4. Accuracy

How close is measured value to actual value.

5. Stability

Over time how stable the data is


Bias Drift.

\downarrow change in bias / e.g. with change in temp.
difference b/w measured & actual value bias changes

Constant / Predictable in nature

Bias Instability \rightarrow

Random in nature.

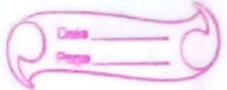

6. Scale Factor

Errors
↳ Additive
↳ Multiplicative

$$y \rightarrow y = s.f(x) + b$$

↓
actual thing
that should be measured

additive error
Bias

Scale factor
(Additive error)
Multiplicative

- Actual value $\rightarrow 10 \text{ m/s}^2$
Measured " $\rightarrow 12 \text{ m/s}^2$ \rightarrow It can be bias of 2
or scale factors of 1.2

Reverse the scale accelerometre.

$$\begin{aligned} -10 \text{ m/s}^2 &\rightarrow -8 \quad \text{Bias of 2} \\ +12 \text{ m/s}^2 &\rightarrow \quad \quad \quad \text{scale factors of 1.2} \end{aligned}$$

7. Noise Floor ($\sqrt{\text{Hz}}$)

8. Repeatability


$$= \frac{\text{Max} - \text{Min value}}{\text{Full Range}} \times 100\%$$



6/08/19

Smart Sensor -

Smart sensor system

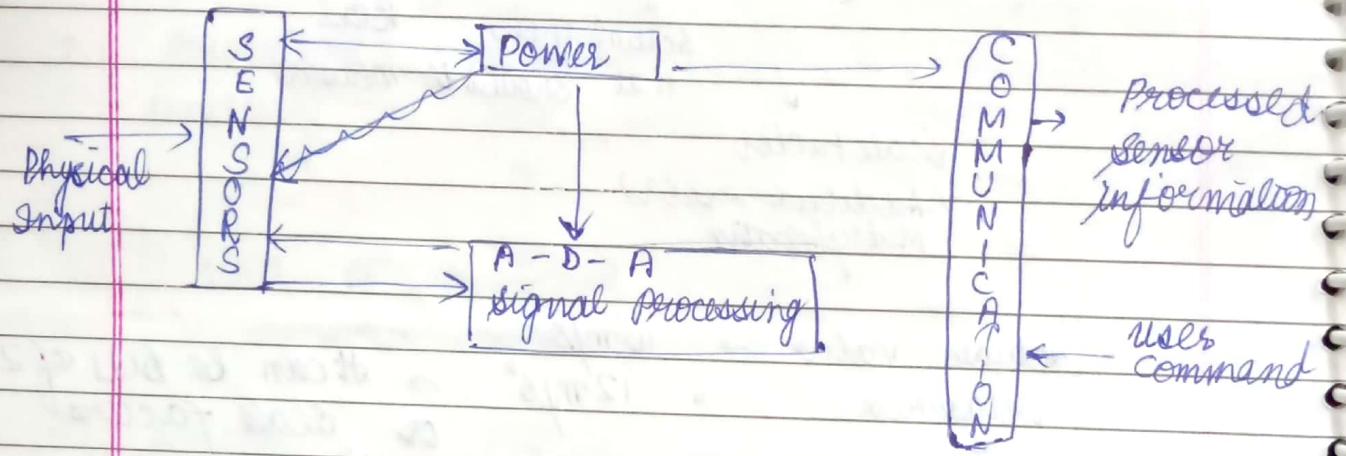

Using sensors, now we can regenerate power.

1. Low Powered sensing elements
2. Power battery / Energy harvesting
3. High speed wireless Comm. (5G)

Temperature / Thermal sensor

- Degree of how hotness or coldness is temperature

Temperature scales

1. Kelvin scale.

1 the part or fraction of triple point of water

273.16

water can \downarrow coexist as water, liquid & gas at this point

2. Celsius scale (centigrade)

took 2 reference pts \rightarrow boiling 0°C & freezing pt. 100°C

after 1 yr

$\rightarrow 100^\circ\text{C}$

0°C .

100° Scale \Rightarrow contd.

3. ~~Faren~~ Fahrenheit scale

Ice pt. (Freezing pt.) 32°F

Avg body temp of human 96°F

\downarrow later

93.8°F

4. Re'aumur scale

Freezing pt 0°

Boiling pt 80°

used in beer industry

5. Rankine scale

$273.16\text{ K} \approx 491.69^\circ\text{ Rankine}$



6. International Practical Temp Scale (IPTS)


multiple reference pts

Ice pt

Steam pt

Triple pt of N₂


Thermocouples

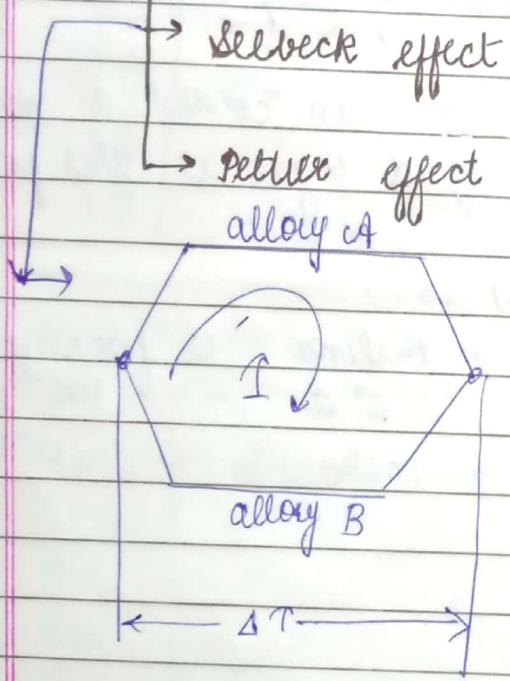

- If temp. difference is introduced b/w the 2 junction pts, there will be a current flowing from hot junction to cold junction
- Both junctions have diff temp.

Peltier effect

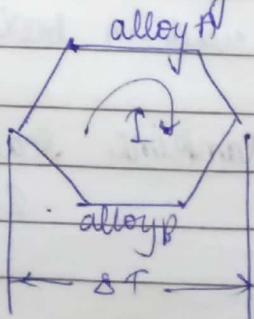- can make Peltier heater, cooler
- If there is a current flowing b/w 2 junctions then 1 junction is at high temp & other at low temp.





Types of thermocouples →
J, K, T.

R TD (Resistance Temp. Detector)

$$R_t = R_0(1 + a t + b t^2 + c t^3 + \dots)$$

Calibration curve

2 curves → 1 expected & other observed curve
then match the 2 curves.
→ To bring real world behaviour to expected behaviour!

a → Temp coefficient

b, c, ... → Higher order temp coeff

most common RTD →

Platinum RTD

$$\alpha_0 = 0.00385 \text{ } \Omega/\Omega \text{ valid for } (0-100^\circ\text{C})$$

$$R_0 = 25.5 \Omega$$

can be used to measure from triple pt of hydrogen
(13.81K) to freezing pt of antimony (730.75°C)


For $> 100^\circ\text{C}$, Callendar's eqn →

$$\frac{t}{R_{100} - R_0} = \frac{100(R_t - R_0)}{R_{100} - R_0} + S \left(\frac{t}{100} - 1 \right) \frac{t}{100}$$

$$S \approx 1.5 \text{ (Callendar's coefficient)}$$



Messingstern
bridge

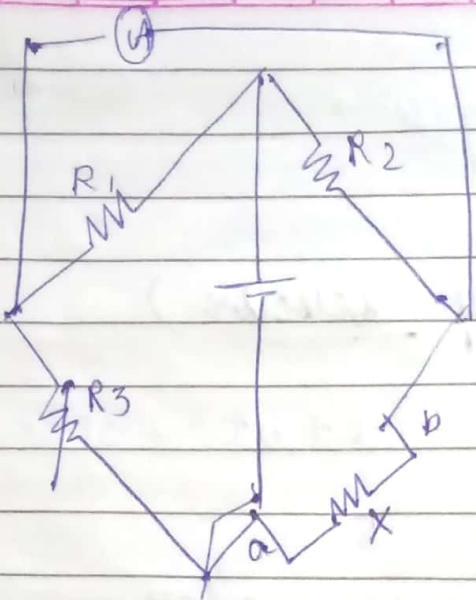

$$R_1 + R_3 = R_2 + x + a + b$$


$$\text{if } R_1 = R_2$$

$$R_3 = x + a + b$$

Measures res. of x
with error of a & b

To remove this error, we
have 3 terminal RTD
instead of 2 terminal
RTD.

3 terminal RTD \rightarrow

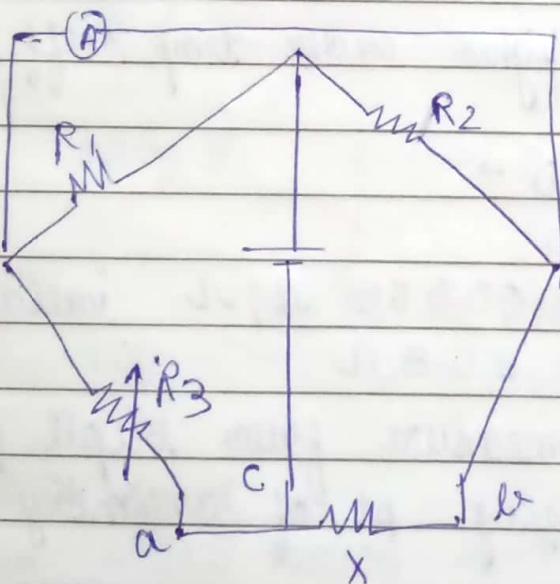

- length of $a \&$
length of b must
be same.

- Also material of
 a & b or
need to
be same.

$$c + R_1 + R_3 + a = R_2 + b + x + c$$

$$R_1 + R_3 + a = R_2 + b + x$$



Thermistors

not widely used
high temp. coefficient


- made of semiconductor

$$B \left(\frac{1}{T} - \frac{1}{T_0} \right)$$

$$R_t = R_0 e^B$$

$B \rightarrow$ manufacturer defined constant.
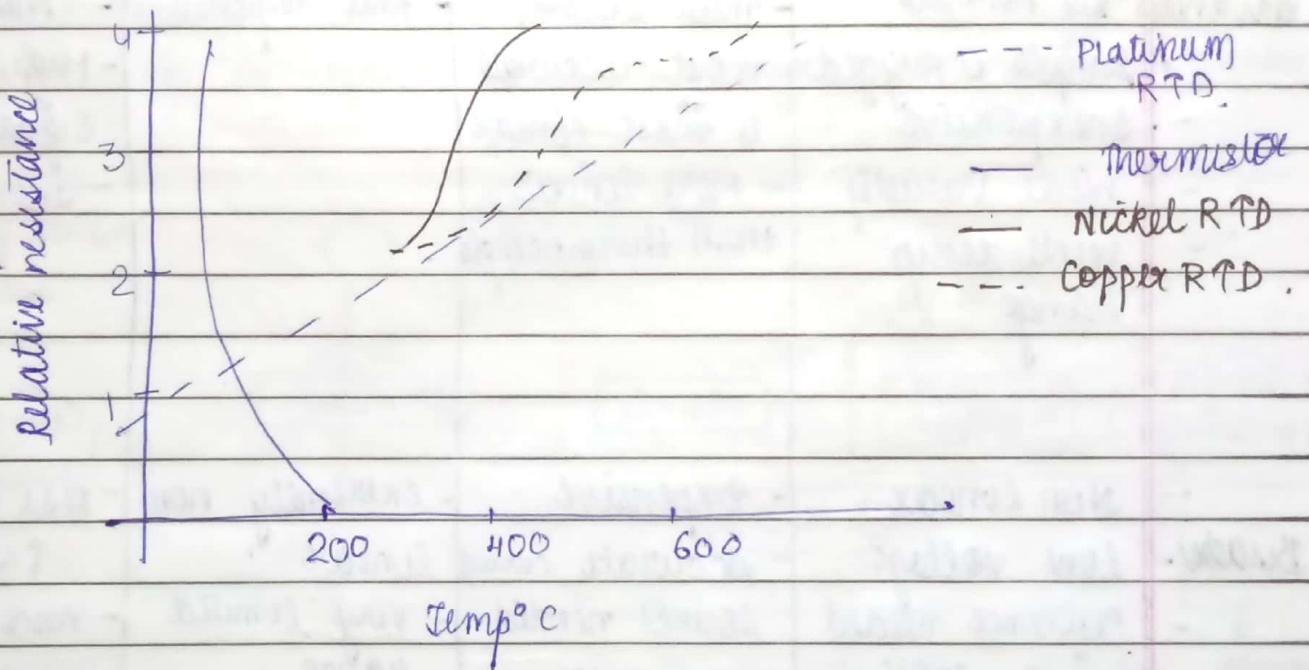
$$B \propto \frac{E}{K} \rightarrow \text{energy level in } \text{eV}$$



Platinum RTD \rightarrow linear behaviour \therefore most preferred.

By adding ckt like A/D, etc \rightarrow convert non linear into linear.


$$\frac{R_x}{R_0} = \frac{U}{6}$$

$$\begin{aligned} & R_x = R_0 \cdot \frac{U}{6} \\ & R_x = R_0 \cdot \frac{U}{6} \\ & R_x = R_0 \cdot \frac{U}{6} \\ & R_x = R_0 \cdot \frac{U}{6} \end{aligned}$$



IC Sensor (Smart)

CR & sensing
element on
same substrate

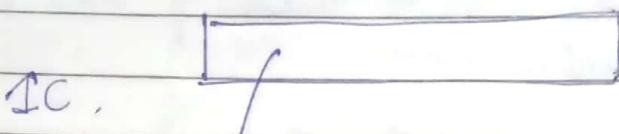

mostly thermistor as it is made of semicond.
can be RTD / thermocouple

Thermocouple	RTD	Thermistor	IC Sensor
<ul style="list-style-type: none"> - Self Powered - Simple & rugged - Inexpensive - Wide Variety - Wide temp range 	<ul style="list-style-type: none"> - most stable - most accurate - most linear - More linear than thermocouple. 	<ul style="list-style-type: none"> - Fast response 	<ul style="list-style-type: none"> - most linear - Highest off signal - inexpensive
<ul style="list-style-type: none"> - Non linear - low voltage - Reference needed - least stable - least sensitive 	<ul style="list-style-type: none"> - expensive - accurate current source needed - ΔR is very small. - self heating 	<ul style="list-style-type: none"> - extremely non linear - very limited range - very fragile 	<ul style="list-style-type: none"> - less range $T < 200^\circ C$ - need power supply - slow


Biomedical Instrumentation

- measures physiological parameter related to body
- measure / determine presence of some physical quantity
Electronic →
EEG, ECG, X Ray, BP Monitor, Glucose monitor

Mechanical Instruments

BP Monitor, Gas gauge

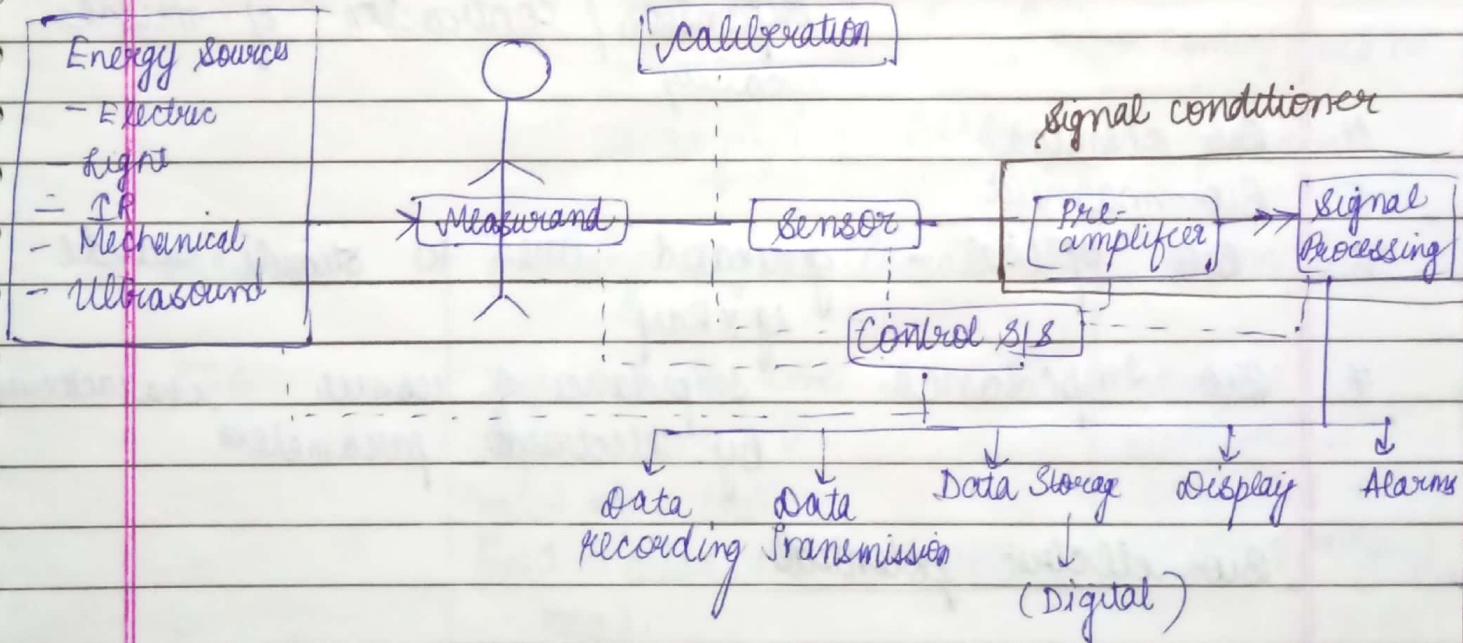pressure in eyes → pressure gauge (to measure tension
in eyes)
(Glaucoma)



- sensor errors → tolerance level is 0. For this active calibration S/W is needed.

Measurand → Physical qty to measured.

Signal cond. → Imp Matching | DAC |

→ vary from simple resistor to multistage amplifier to ADC



In Vivo

- Inside the body measurement
- BP eg → BP, Thermometer temp.



In Vitro

- Measurement is outside
- eg glucose measurement,
In Vitro fertilisation.

Different sources of biomedical signals

1. Bioelectric - eg Measurement of membrane potential
2. Bio acoustic - sound measurement
3. Bio mechanical - any type of motion / disp done due to expansion / contraction of muscle cavity
4. Bio chemical
5. Bio magnetic
6. Bio optical → generated due to stimuli outside
eg X Ray
7. Bio impedance. - Impedance of tissue characterised by electrical parameters

Bio electric potential

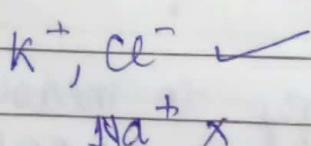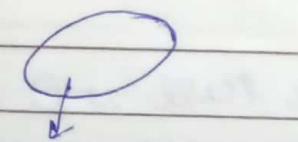


Each cell has lots of ions inside. It has membrane called cell membrane


- Responsible for any type of - ?



Rest potential

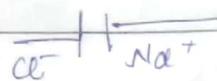

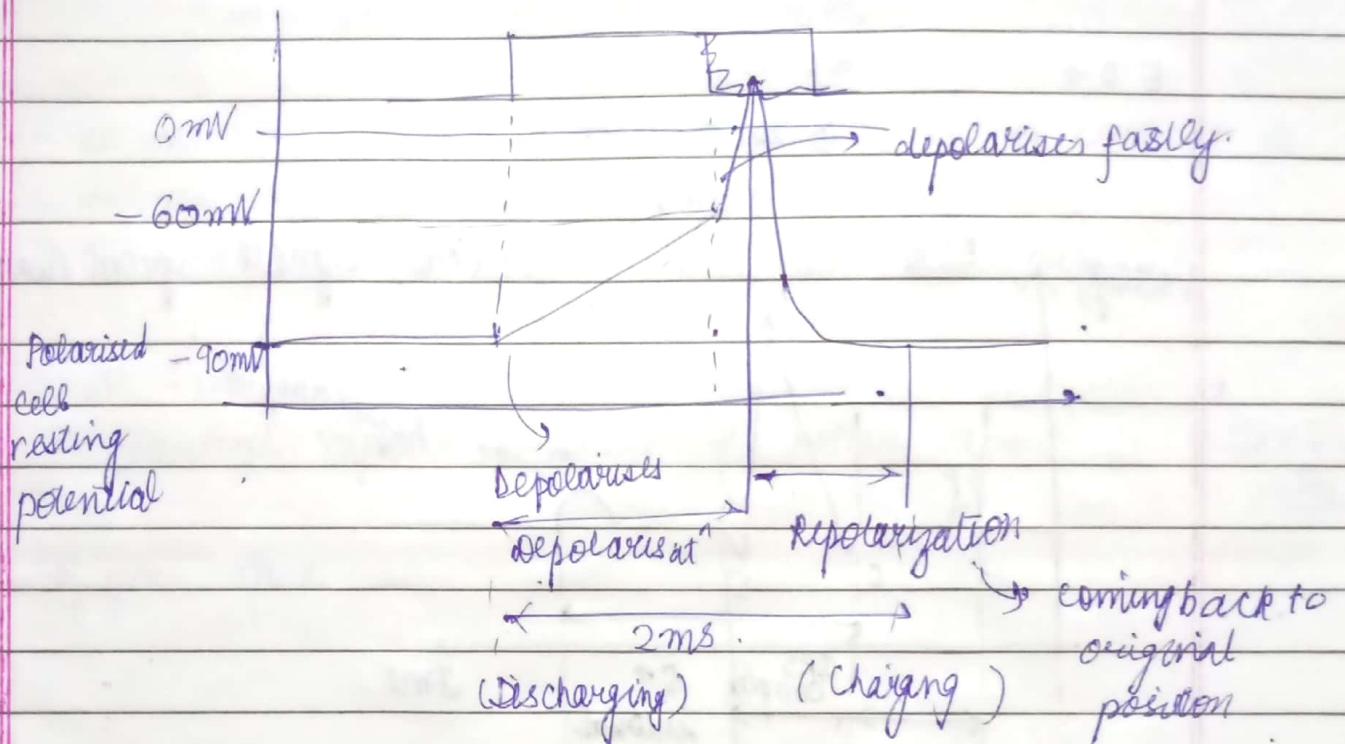Rest condition \rightarrow Polarized condition



Parameter	Primary signal characteristic	Transducer
EGG	Freq 0.05 to 120Hz Amp 0.1 to 5 mV Typical amp: 1mV. (need to build LPF with gain of 1000)	Surface electrode is connected to surface of body
EEG	0.1 to 50Hz 2 to 200 μV 50 μV	Surface
EMG	5 to 2KHz 0.05 to 5mV 1mV	needle



13/08

ERG


DC TO 20Hz
0.5 μV to 1mV
0.5 mV

contact
electrodes

EDG

AC TO 100Hz
10 to 3500 μV
0.5 mV

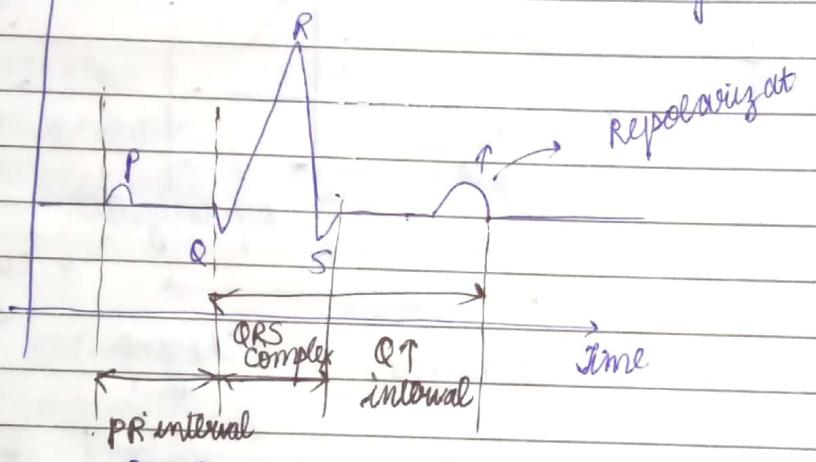Voltage ↑ ECG → electrical signals from heart.



- Read ECG,

EEG

Brain waves

S	0.5 - 4
θ	4 - 8
α	8 - 13
β	13 - 22
γ	22 - 30

From scalp → signal's amp is 100 μV or less
In the cortex → 1mV

~~13/08/19~~



Humidity / Moisture Measurement

Water in liquid form \rightarrow moisture
in gaseous form \rightarrow humidity


- To measure humidity, condense it & cool it & see the temperature
- To quantify moisture, we use humidity

at -112°C

Partial vapour pressure of water vapour $\approx 0.8 \times 10^6 \text{ mm Hg}$

- If you mix

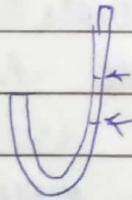- Barometer \rightarrow mercury. Mercury is filled in it



Just for 200°C

10^9 orders


change in partial
vapour pressure.

at 100°C -

Partial vapour pressure of water vapour $\approx 760 \text{ mm Hg}$

Applications :-

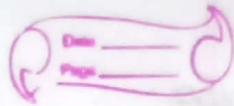1. Tobacco & paper industry.
2. Human comfort \rightarrow air conditioner (HVAC)
3. Semiconductor industry (moisture in clean rooms has to be maintained 10-50% RH)



4. Food & Warehouse. (Refrigerator)
 5. Agriculture (soil moisture content has to be maintained at a specific level)
- Metallurgy (- mixing alloys)
 - Sensor needs to robust to survive a huge dynamic range

Common parameters

- 1 - Dry bulb temperature
- 2 - Wet bulb temperature
 - In humid areas, wet bulb temp is high.
 - Perceived temp > Real temp (when humidity is high)
 - Real temp > Perceived temp (when low humidity)
- 3 - Dew Point Temp
 - Temp" when Sat" occurs.
 - Temp at which humidity becomes 100% RH.
 - + Dew point night in areas where humidity is very high.
 - eg From AC room when you move out fogging on specs?
 - Max temp" at which fogging will happen.
- 4 - %RH, water vapour
 - max water vap at given temp.

at 10°C dew pt \rightarrow the partial vap pressure is 2276.76
 $25^\circ \text{C} \rightarrow$ 3074.41 Pa

$$\frac{2276.76}{3074.41} = 74\% \text{ RH}$$

Measurement of humidity

Secondary measurement is required

Primary Measurement - measuring directly the qty

Eg calculating Measure a correlated qty
e.g. to find force, you first measure
accn.

Instruments to measure RH

1. wet bulb / dry bulb

↓
primary instrument → two thermometers.

Psychrometric Charts

2. Mechanical expansion

{ Silica gel → humidity absorbant
in shoe pouches

how much the size is changing

3. Dunmore element. (set of 2 wires)

Bifilar wound wire on insulating substrate,
coated with LiCl

salt for humidity sensing

4. Pope cell

There is a conductive polymer which is humidity sensitive



5. Bulk effect - thin film of sulfonated polymer

6. Surface Resistance.


7. Strain Gauge - It's gauge change to some deformation induced.

8. Capacitance - Two plates b/w them we have dielectric & use a dielectric which is sensitive to humidity.
Humidity changes \rightarrow dielectric const changes.

Measurement of dew point



1. Condensation type hygrometer \rightarrow chilled surface. A small mirror is cooled down & check whether it is getting condensed or not moment that happens.

2. Heated saturated salt

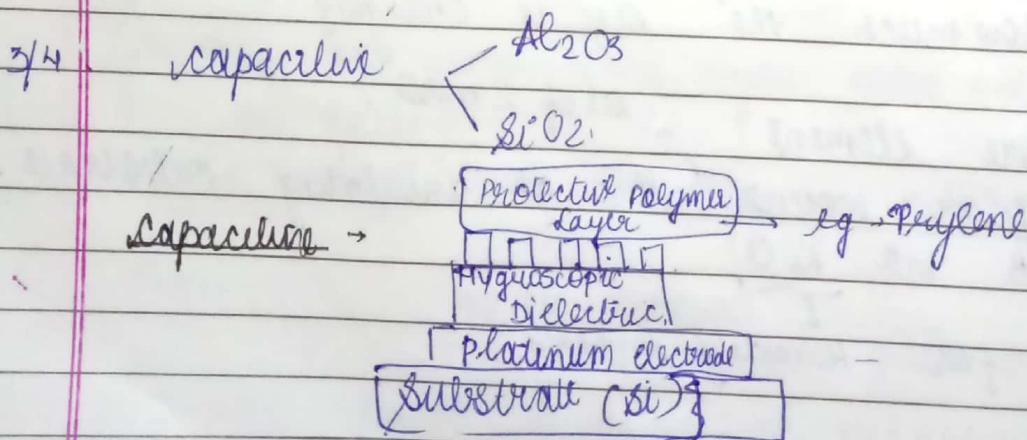

side view

Measuring Capacitance

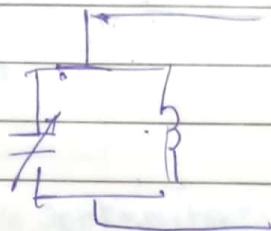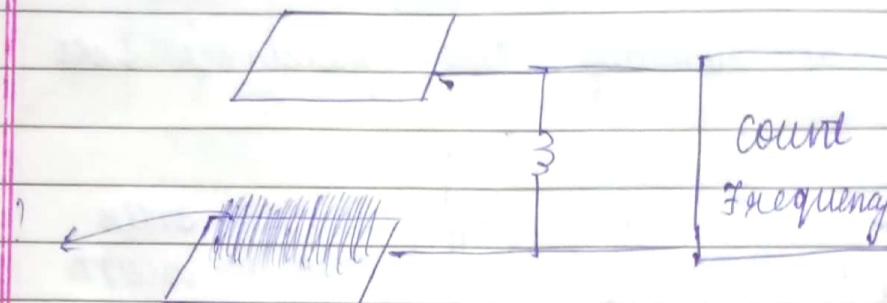

Advantages :-

1. O/p voltage is linear
2. stable results for big dynamic range
3. can detect wide range of RF

long range sensing is not possible using
capacitance


Eg: HVAC, printers, automobiles

20/08/19





Resistive Humidity Sensors

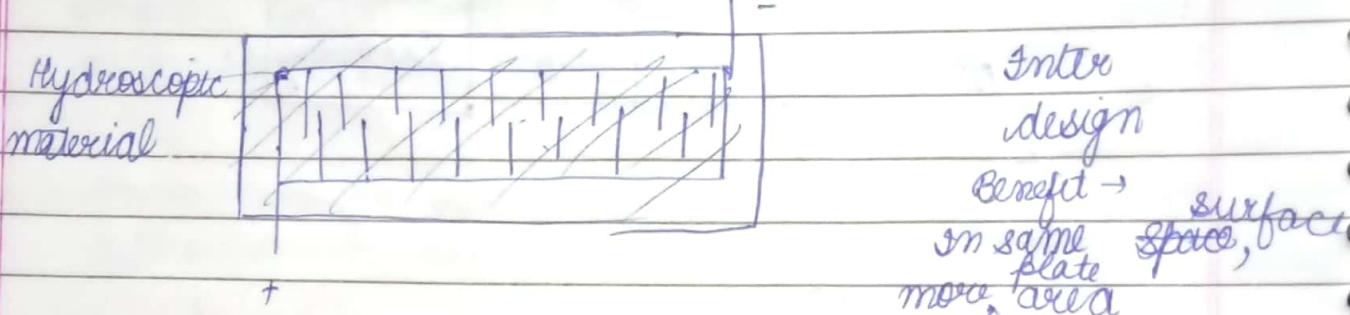more often, as humidity rises, resistance less.



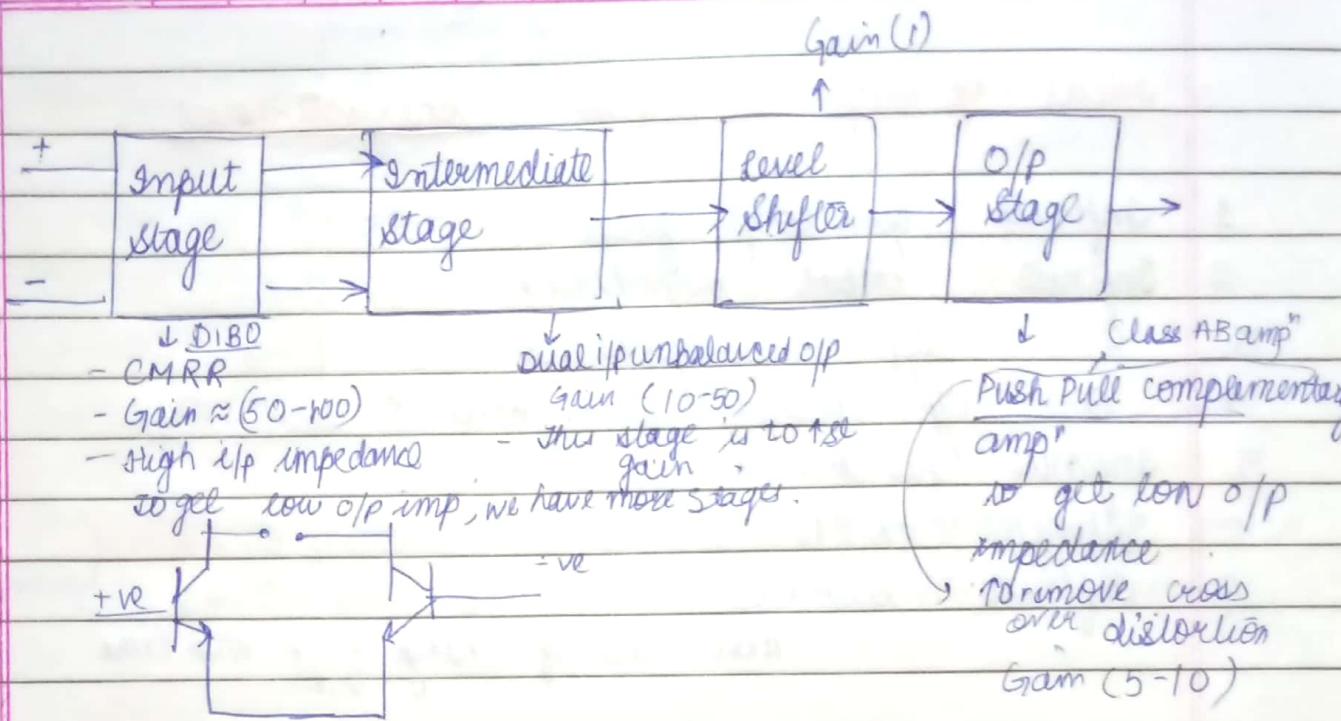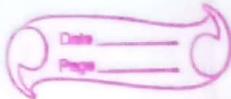- extremely cost effective] Advantage
- susceptible to environment] disadvantage
- measuring humidity in already humid region is difficult
- easily interchangeable] Advantage
- used for places where we don't need accuracy & can not spend much.
- why is there a need of op amp for making amp?
why not resistor?
resistor requires large i/p current which is not practically possible to give so op amp.




- dual i/p Balanced o/p

- Only differential i/p is capable of giving CMRR


- CMRR should be high

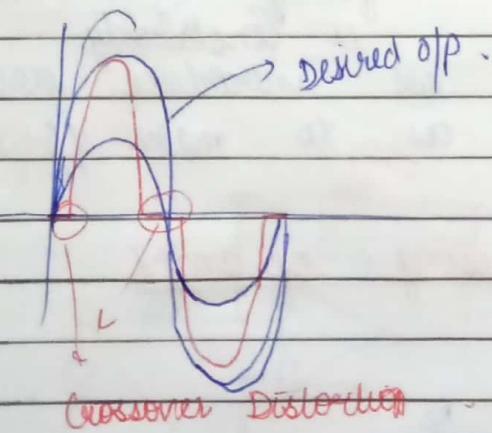→ Here we are using direct coupling, not cap coupling
so DC is not blocked, we need to shift DC. ∴ we use level shifter



Ideal op amp electrical characteristics

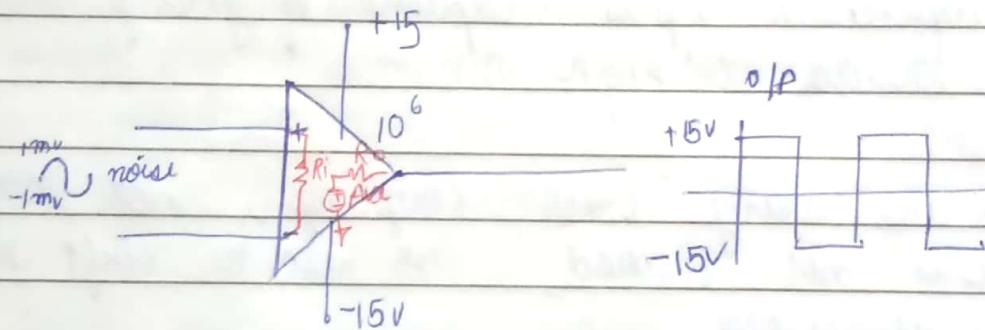
1. Infinite open loop gain
2. Infinite input impedance
3. 0 o/p impedance
4. 0 o/p voltage when input = 0.
5. Infinite bandwidth
6. Infinite CMRR
7. Infinite slew rate,
max rate of change of o/p with time




no o/p only noise & we are getting oscillations this is instability
we introduce feedback so as to make it stable.

Signal Conditioning using op amps

1. Non Inverting Amp

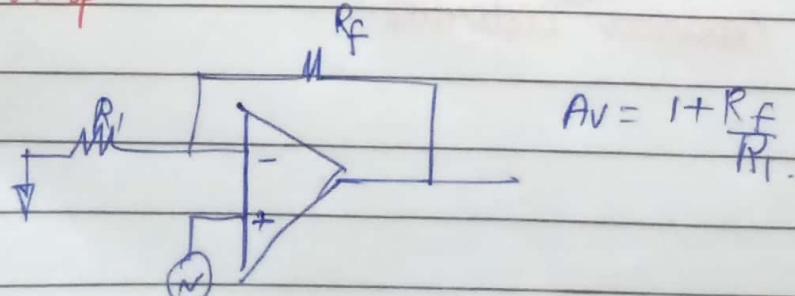


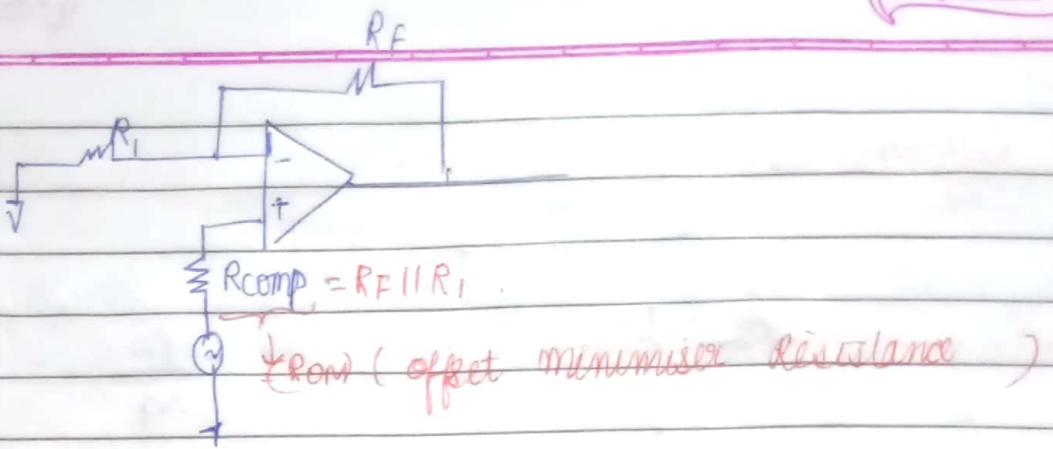


Practical Op Amp -

$R_{comp} \rightarrow$ To ensure that small amt of current going into +ve terminal
 ∇R_{comp} small amt of current going into -ve terminal

2. Inverting amplifier

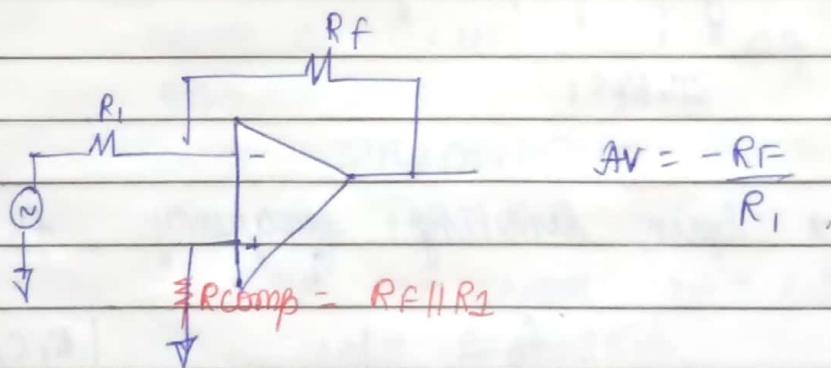


3. Integrator

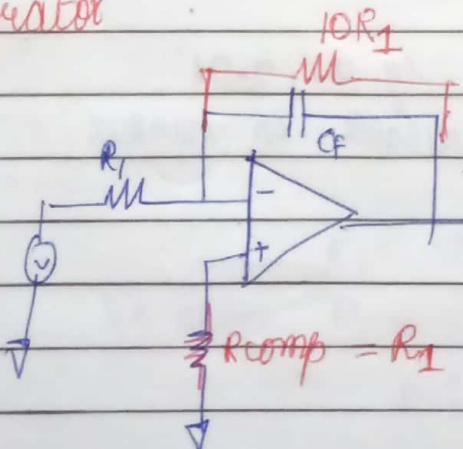


For low freq cap \rightarrow OC
 So instability
 So we put resistor in parallel with capacitor C_F .

- Fix R_1 & find R_f

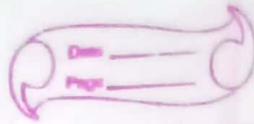

4. Differentiator

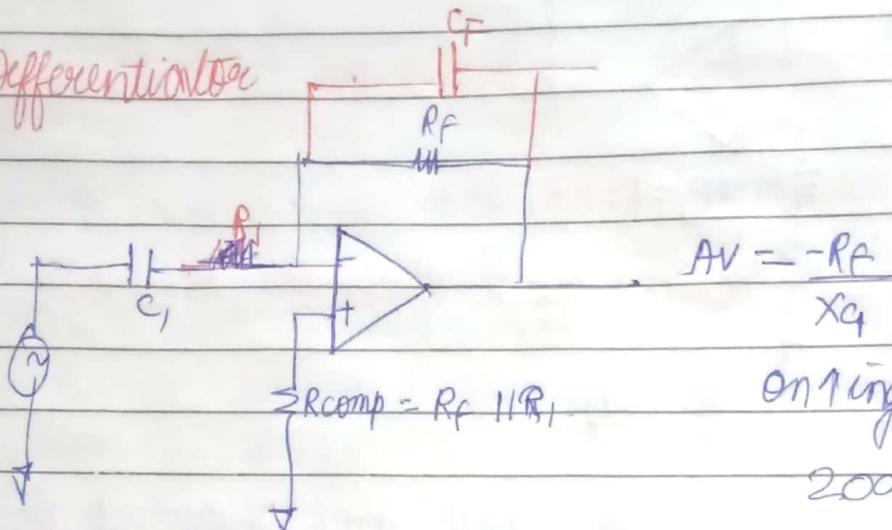

$$R_1 \propto 0.01 R_f - 0.1 R_f$$

Steps to design a practical differentiator

1. $f_a \rightarrow$ highest frequency that needs to be differentiated

$$f_a = \frac{1}{2\pi R_f C_1}$$

2. $f_b \rightarrow$ gain limiting frequency $f_b \approx 20 f_a$.

$$f_b = \frac{1}{2\pi R_1 C_1} \quad [R_1 C_1 = R_f C_f]$$

choose $C_f \rightarrow \mu F$ e.g. 0.1, 0.01

choose values available in market

Typical values

Standard -

E-12 scale

1, 1.2, 1.5, 1.8, 2.2, 2.7, 3.3, 3.9, 4.7, 5.6, 6.8, 8.2, 10

Any multiple of 10 of these 12 nos is also standard

every no. is $\frac{1}{10}$ more of previous no.

- Any device \rightarrow 10% tolerance
round off to these resistors' value.

Ques Design a differentiator that frequency is 20 Hz - 800 Hz

$$f_a = 800 \text{ Hz} = \frac{1}{2\pi C_1 R_F}$$

$$\text{choose } C_1 = 0.1 \mu\text{F}$$

$$800 = \frac{1}{2\pi \times 0.1 \times 10^{-6} R_F}$$

$$R_F = 1.98 \text{ k}\Omega$$

We can choose $R_F = 1.8 \text{ k}\Omega$ or $2.2 \text{ k}\Omega$

We choose $R_F = 2.2 \text{ k}\Omega$.

$$f_b = 16 \text{ kHz} = \frac{1}{2\pi R_1 C_1}$$

~~$$R_F \approx 10 R_1$$~~

$$R_1 = 99.5 \text{ k}\Omega$$


We choose $R_1 = 100 \text{ }\Omega$.

$$R_1 C_1 = R_F C_F$$

$$C_F = 0.0045 \mu\text{F}$$

We choose $C_F = 0.0047 \mu\text{F}$.


summry, sub, comp

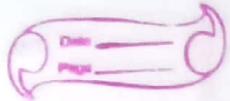


21/08/19

Instrumentation amplifier

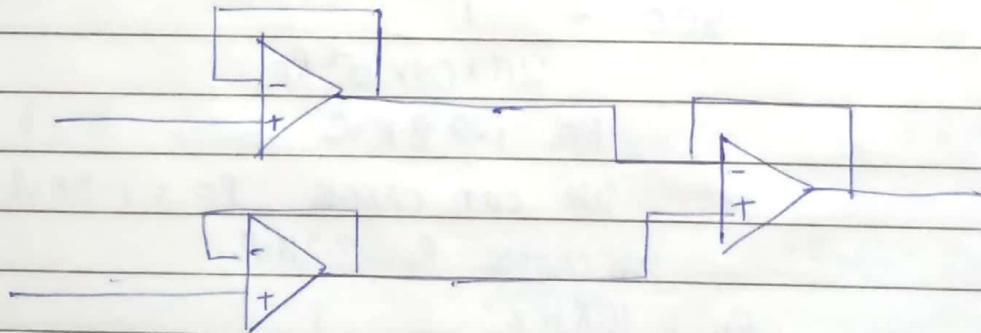- In "instrumentat" amp, gain can be externally set
- CMRR is very high
- Accuracy is very high
- Stable passive resistive feedback n/w is there.
- Package consisting of multiple of amps, wares with accurate & stable resistive / capacitive feedback.
- Gain can be selected externally
- High gain accuracy, gain stability & CMRR
- All the op amps are on same substrate



Wheatstone Bridge \rightarrow

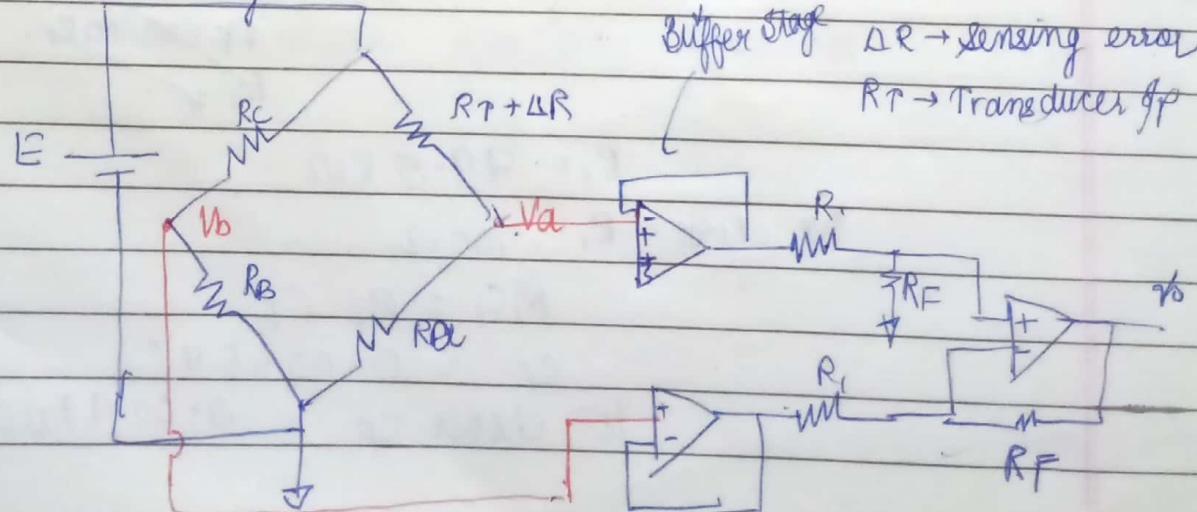



Buffer stage \rightarrow Gain of unity

$$A_v = \frac{R_F}{R_1}$$

at zero condition, bridge is balanced

$$\frac{R_C}{R_B} = \frac{R_T}{R_A}, \Delta R = 0, V_a = V_b \therefore V_{ab} = 0$$

Design a bridge in accordance with transducer.

$$V_a = \frac{E \times R_A}{R_A + R_T + \Delta R}$$

$$V_b = \frac{E \times R_B}{R_B + R_C}$$

$$\therefore V_{ab} = E \left(\frac{R_A}{R_A + R_T + \Delta R} - \frac{R_B}{R_B + R_C} \right)$$

If $R_A = R_B = R_C = R_T = R$

$$V_{ab} = E \left(\frac{\frac{R_A}{2R + \Delta R}}{\frac{R_A}{2R + \Delta R} - \frac{R}{2R}} \right)$$

$$V_{ab} = E \left(\frac{R}{2R + \Delta R} - \frac{1}{2} \right)$$

$$V_{ab} = \frac{-\Delta R \cdot E}{2(2R + \Delta R)} \rightarrow \text{input to instrumental amp'}$$

$$V_o = \frac{R_F}{R_1} \times V_{ab}$$

Ques

Assume a thermistor is connected to a bridge circuit with $R_A = R_B = R_C = 120\text{ k}\Omega$. Excited by $E = +5$.

The thermistor has nominal resistance $= 120\text{ k}\Omega$.

at reference temp $= 25^\circ\text{C}$ & temp coefficient of $-1\text{ k}\Omega/\text{ }^\circ\text{C}$. Determine o/p voltage at $T = 0^\circ\text{C}$ &

$T = 100^\circ\text{C}$. If $R_F = 10\text{ k}\Omega$, $R_1 = 2.2\text{ k}\Omega$.

$$R_T = R_0 (1 + \alpha \Delta T)$$

$$R_A = R_B = R_C = 120\text{ k}$$

$$E = +5\text{ V}$$

$$\text{for } 0^\circ\text{C} \rightarrow$$

$$\Delta R = 120(1 - 25\text{ k}\Omega)$$

$$\begin{aligned} \text{o/p voltage} &= \frac{-1RE}{2(2R + \Delta R)} \times \frac{RF}{R_1} \\ &= \frac{-25 \times 10^5}{2(2(120\text{k}) + 25\text{k})} \times \frac{10}{2.2} \\ &= -1.07\text{V}. \end{aligned}$$

$$\text{For } T = 100^\circ\text{C} \rightarrow$$

$$\Delta R = -75\text{ k}\Omega \quad \text{as } \Delta T = 75^\circ\text{C}.$$

$$\begin{aligned} \text{o/p voltage} &= \frac{-75 \times 5}{2(240 - 75)} \times \frac{10^5}{22} \\ &= \frac{75 \times 5 \times 5 \times 10}{22 \times 165} = 5.17\text{V} \end{aligned}$$


30
25
65



Filters → device that raises SNR


- └→ passband (zero attenuation)
- └→ stopband (infinite attenuation)

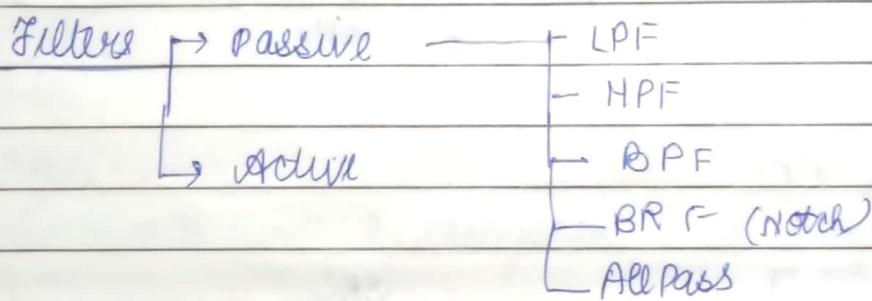- response time
- bandwidth over which measurement is desired.



- Passive low pass

M^R

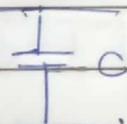

$$\frac{V_o}{V_{in}} = \frac{1}{1 + \omega RC}$$

$$\left| \frac{V_o}{V_{in}} \right| = \frac{1}{\sqrt{1 + (\omega RC)^2}}$$

Gain


-
- $3dB (0.707)$

At $3dB \rightarrow$ half power freq.


-20dB/decade $[C = RC]$

$$f_C = \frac{1}{2\pi RC}$$


Ideal Responses

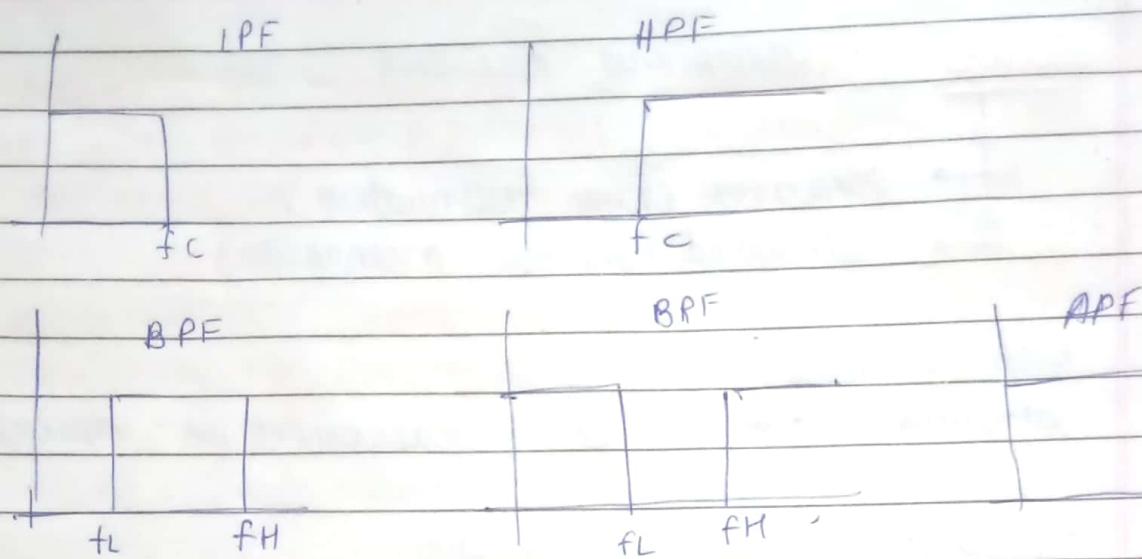

Practical HPF

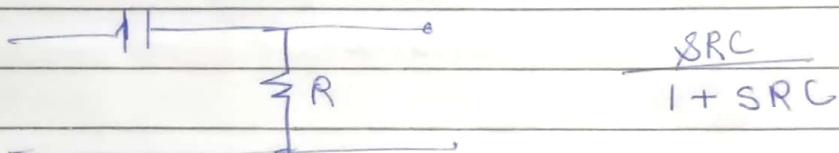

$$\left| \frac{V_o}{V_{in}} \right| = \frac{WRC}{\sqrt{1 + (WRC)^2}}$$

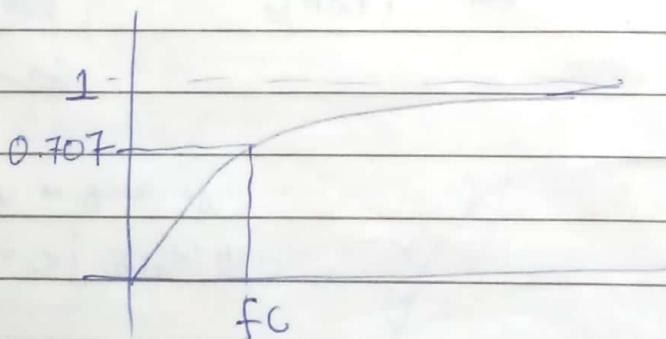

Active Filters

- In passive filters gain is not more than 1 & we can not have gain of our choice. \therefore we need active filters.

- Gain & frequency control
- Due to high input impedance & low o/p impedance
loading effect




make $R_o = 0$ no loading effect; V won't reduce for any value of R_L

- cheap (cheaper than inductor or not cap).

Types:-

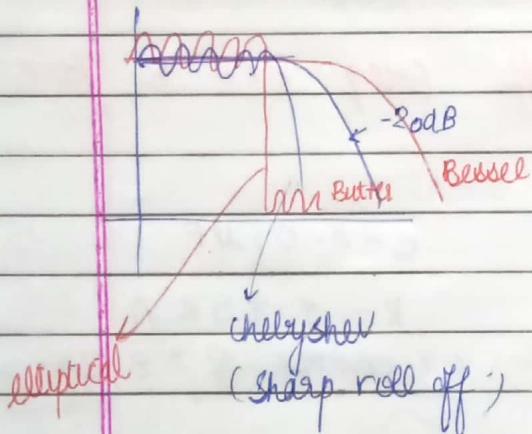
1. Butterworth
2. Chebyshev
3. Elliptical
4. Bessel



Best stop band resp \rightarrow elliptical
A bit tradeoff \rightarrow Butterworth

First order LP Butterworth

(maximally flat) (flat f_{cut})

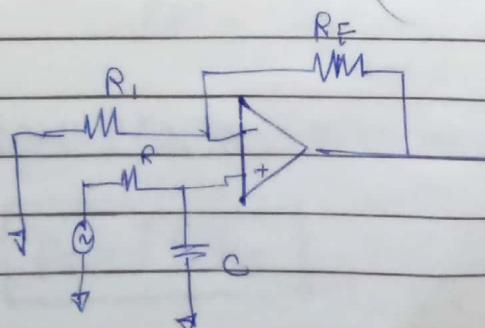

$$f_c = \frac{1}{2\pi R C}$$

$$\text{Gain} = 1 + \frac{R_F}{R_1}$$

$$TF = \frac{Af}{1 + \mu DRC}$$

↑ cap will introduce phase diff
(phase lag)

- Phase angle compensation is lesser.
- Phase lag in Butterworth. If phase lag is not a problem use Butterworth.

$$\text{At } f = f_c \quad \text{Gain} = 0.707 Af$$

$$f < f_c, \quad \text{Gain} = Af$$

$$f > f_c, \quad \text{Gain} < Af$$

Ques. Design a LPF with cutoff freq 2kHz & gain = 2

$$f_c = 2 \text{ kHz}$$

$$f_c = \frac{1}{2\pi RC}$$

$$C = 0.01 \mu F$$



$$R = 4.95 k\Omega$$

We choose $R = 8.2 k\Omega$

$$1 + \frac{RF}{R_1} = 2$$

$$\frac{RF}{R_1} = 1$$

$$\text{Choose } RF = R_1 = 10 k\Omega$$

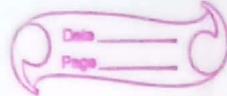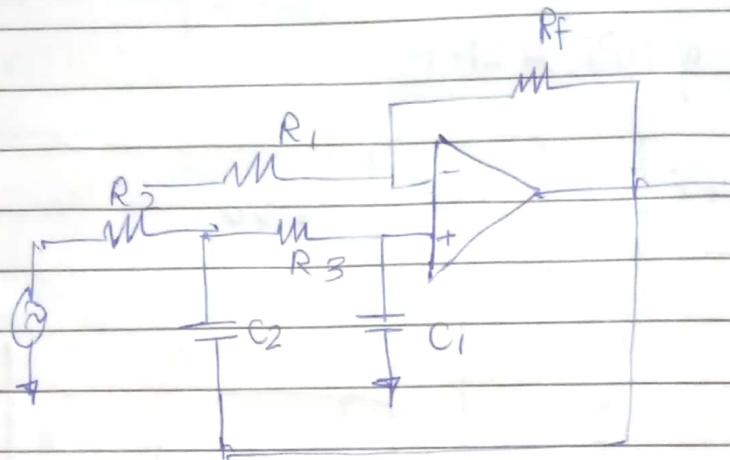Second Order LP Butterworth

$$AF = 1 + \frac{RF}{R_1}$$

$$f_c = \frac{1}{2\pi R_2 C_2 R_3 C_1}$$

Ques design 2nd order filter with $f_c = 2 \text{ kHz}$


$$\text{choose } R_2 = R_3 = R \quad C_1 = C_2 = C$$

$$f_c = \frac{1}{2\pi RC}$$

$$\text{choose } C = 0.0033 \mu\text{F}$$

$$R = 24 \text{ k}\Omega \quad (22 \text{ k}\Omega)$$

3/08/19

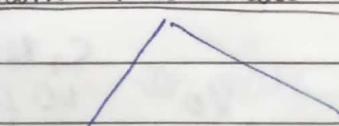Band Pass Filter

Wide Band
 $Q < 10$

Narrow Band
 $Q > 10$

Resonant
Circuit


→ Wide BPF
→ Narrow BPF


$$\underline{Q \text{ factor}} = \frac{f_c}{B.W.}$$

$$B.W. = f_H - f_L$$

Higher Q factor \Rightarrow more selective



$$f_c = \sqrt{f_L f_H}$$

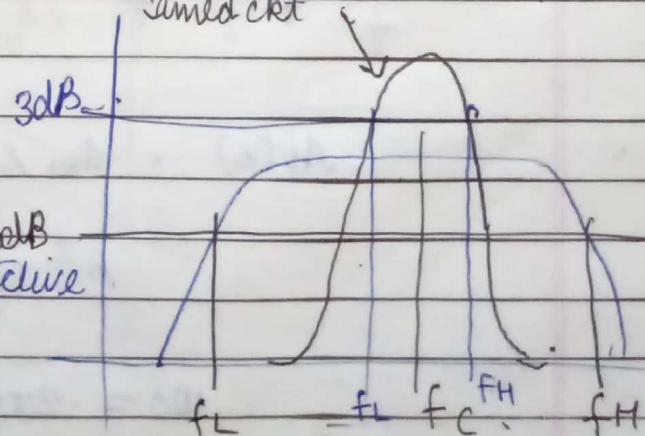

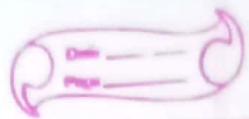

Nwide BPF

Cascading of HPF & LPF

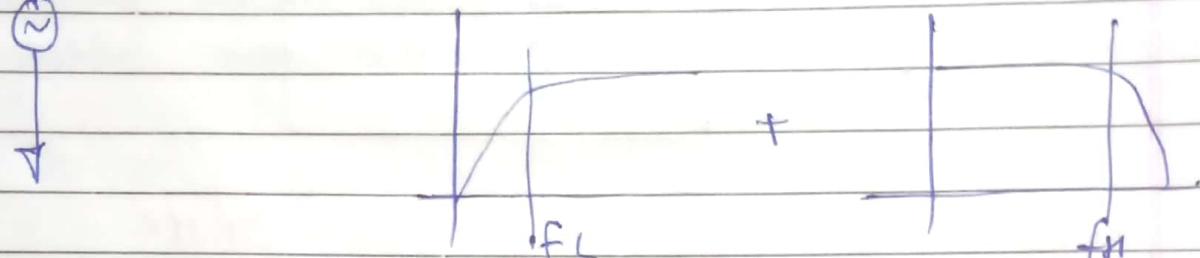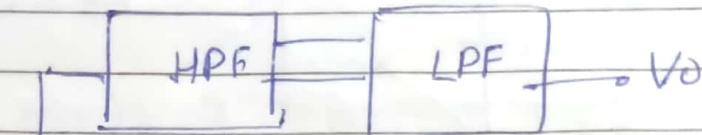

f_L decides HPF


f_H decides LPF



Narrow BPF

$V_1 \rightarrow$ Pot b/w A & D

$V_2 \rightarrow$ Pot b/w C & D.


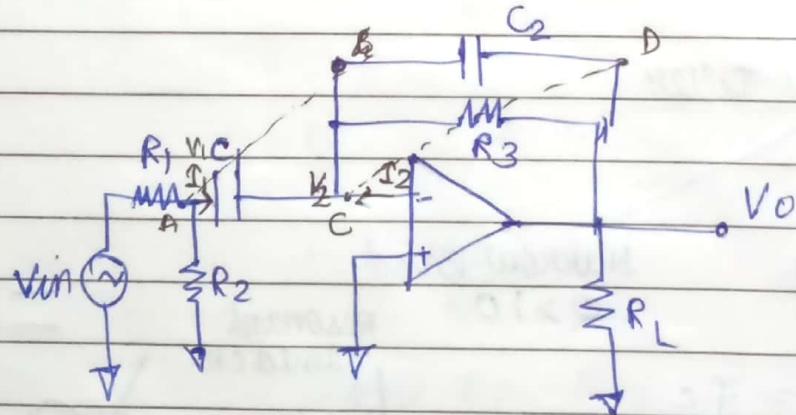


C_1 & R_3 combine
to form HPF


C_2 & R_1 , R_2 combine
to form LPF.

$$Av(s) = \frac{V_o}{V_{in}} \propto \left(\frac{\omega_0}{s} \right) \frac{s^2 + \left(\frac{\omega_0}{Q} \right) s + \omega_0^2}{s^2}$$

$$\omega_0 = 2\pi f_c$$

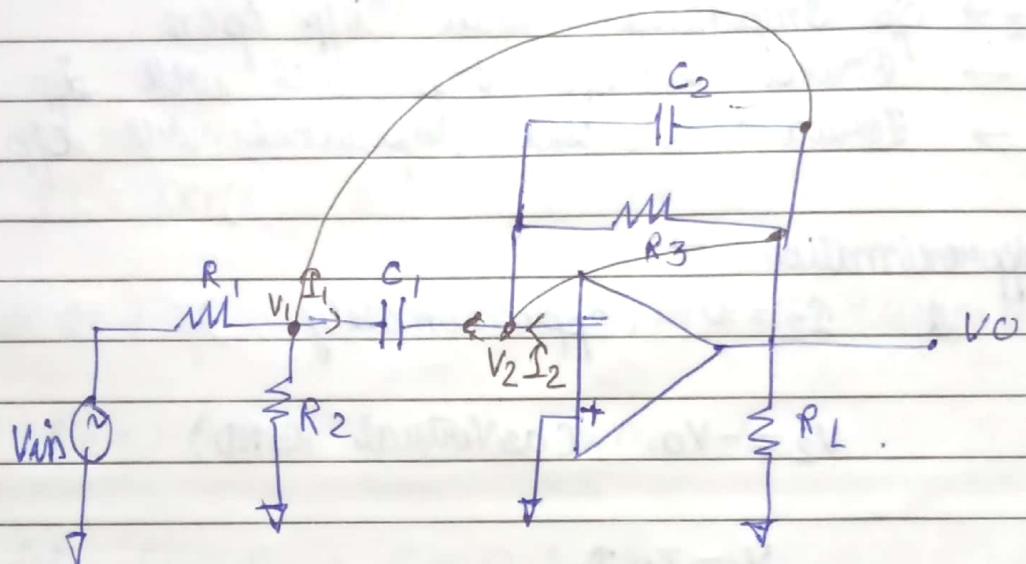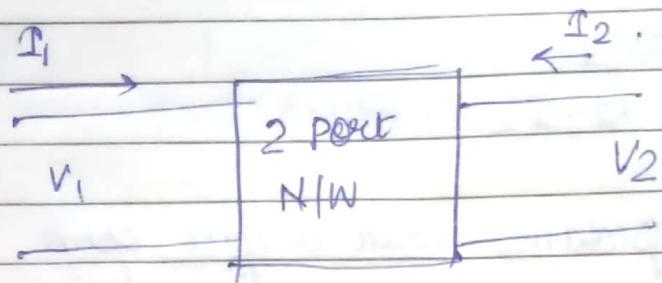

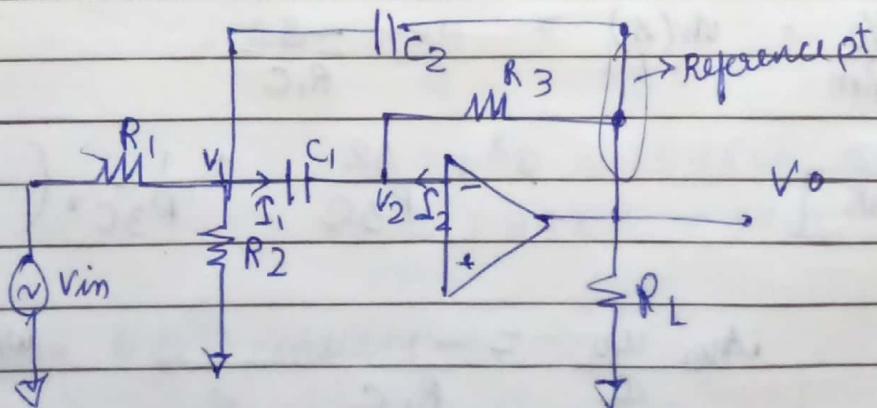To make circuit consistent with two port, put C2 b/w V1 & common pt.



$\text{Q} = \frac{V_o}{V_i}$

$$V_1 = Z_{11} I_1 + Z_{12} I_2$$

$$V_2 = Z_{21} I_1 + Z_{22} I_2$$

$Z_{11} \rightarrow \text{I/p Impedance with output open}$

$Z_{22} \rightarrow \text{O/p Impedance with i/p open}$

$Z_{12} \rightarrow \text{Reverse Transfer Impedance with i/p open}$

$Z_{21} \rightarrow \text{Forward Transfer Impedance with O/p open}$


approximation \rightarrow

$$\therefore I_2 = 0 \quad (\text{approximately})$$

$$V_2 = -V_0 \quad (\text{as Virtual GND})$$

$$V_1 = Z_{11} I_1$$

$$-V_0 = Z_{21} I_1$$

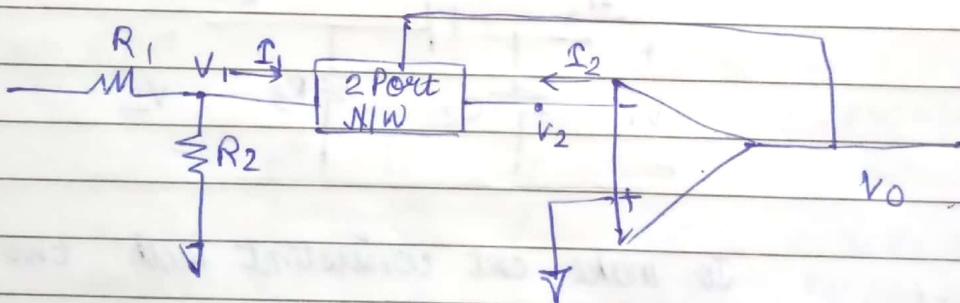

$$\frac{V_0}{V_m} = \frac{dV(\delta)}{d\delta} = \frac{-\delta}{R_1 C}$$

$$\text{Derivative in LCR} \quad \frac{s^2 + \frac{\delta^2}{R_3 C}}{R_3 C} + \frac{1}{R_3 C^2} \left(\frac{R_1 + R_2}{R_1 R_2} \right)$$

$$\frac{dV_0}{d\omega} \frac{\omega_0}{Q} = -\frac{1}{R_1 C} \quad \omega_0 = 2\pi f_c$$

$$\frac{\omega_0}{Q} = \frac{2}{R_3 C}$$

$$\omega_0^2 = \frac{1}{R_3 C (R_1 || R_2) C}$$

$$\omega_0 = -\frac{R_3}{2R_1}$$

Ques Design Narrow BPF with

i) $f_C = 1 \text{ kHz}$, $Q = 5$, $A_{VO} = 8$

as $Q = 5$ if not mentioned, we will design a wide BPF

ii) $f_C = 1.5 \text{ kHz}$, $Q = 5$, $A_{VO} = 8$

i) Let $C_1 = C_2 = C = 0.1 \mu\text{F}$

$$\frac{\omega_0}{f_C} = -\frac{1}{R_1 C}$$

$$R_1 = -\frac{Q}{2\pi f_C \times C}$$

$$= -\frac{5}{2\pi \times 10^3 \times 0.1 \times 10^{-6}}$$

$$= 159 \text{ k}\Omega \approx 160 \text{ k}\Omega$$

$$R_3 = \frac{\omega_0}{Q} = \frac{2}{R_1 C}$$

$$R_3 = 159 \text{ k}\Omega \approx 160 \text{ k}\Omega$$

$$R_2 = 1.89 \text{ k}\Omega \approx 2 \text{ k}\Omega$$

ii) Gain & f_C constant.

$$\text{In } \omega_0^2 = \frac{1}{R_3 C (R_1 || R_2)}$$

Substitute same R_1 , R_2 , $f_C = 1.5 \text{ kHz}$ & find R_3

Q8

$$(2\pi f_c)^2 = \frac{1}{R_3 C^2 (R_1 || R_2)}$$

$$f_{c1}^2 = \frac{R_1 + R_{21}}{R_3 C^2 (R_1 R_{21})} 2\pi^2$$

$$f_{c2}^2 = \frac{R_1 + R_{22}}{R_3 C^2 (R_1 R_{22})} (2\pi)^2$$

$$\frac{R_{22}}{R_{21}} = \left(\frac{f_{c1}}{f_{c2}} \right)^2 \quad (\text{after manipulation})$$

$$\frac{R_{22}}{20} = \left(\frac{1}{1.5} \right)^2$$

$$R_{22} = \frac{2}{1.5 \times 1.5}$$


$$R_{22} = \frac{200}{225}$$


$$R_2 = \frac{Q}{2\pi f_c C (2Q^2 - A_v)}$$

Band Reject Filter (Notch Filter)

LPF in parallel with HPF



Wide Band Rejected filter

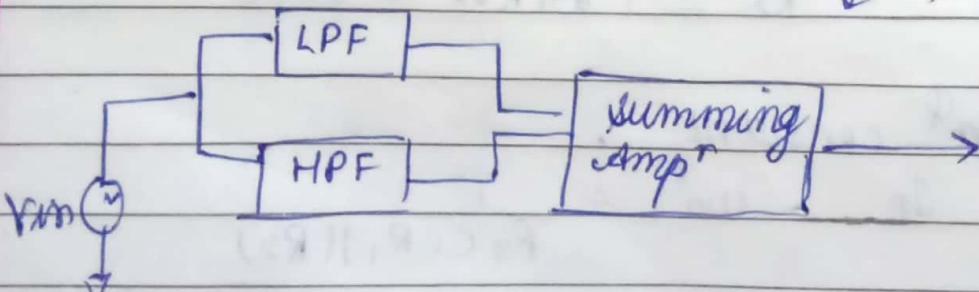

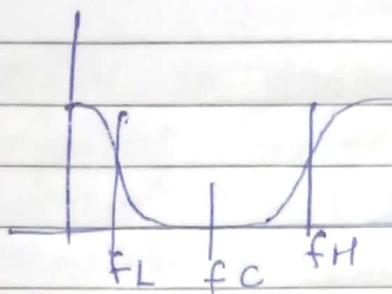


$f_L \rightarrow$ determined by LPF
 $f_H \rightarrow$ " " HPF.

Narrow Band Reject Filter (Notch Filter)

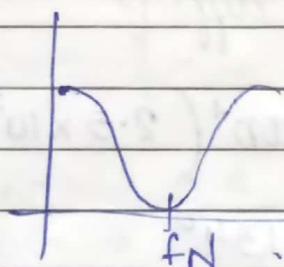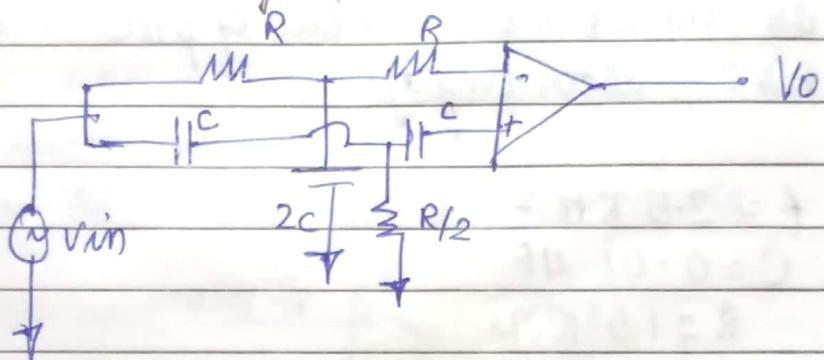

All Pass Filter

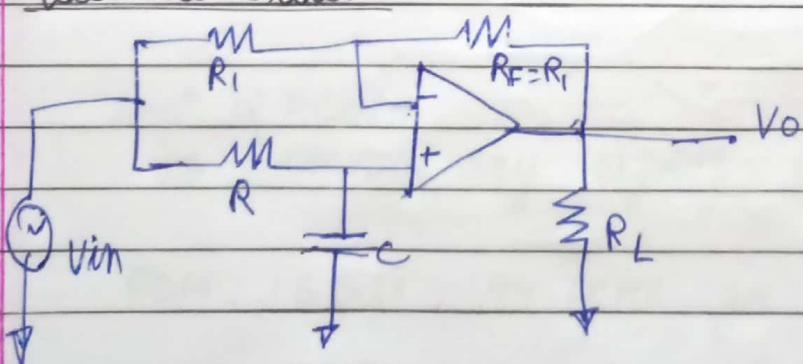

$$\frac{V_o}{V_{in}} = \frac{1 - j2\pi f RC}{1 + j2\pi f RC} = \frac{1 - j2\pi f RC}{1 + j2\pi f RC}$$

(if $R_1 = R$)



$$|dv| = 1$$

$$\text{Phase } \phi = 2 \tan^{-1}(2\pi f RC)$$
$$\phi = 2 \tan^{-1}(\omega RC)$$

This filter is used for phase connection.
eg \rightarrow In transformer \rightarrow out of phase. So choose R & C accordingly.

Ques

$$\text{If } f = 2.5 \text{ kHz}$$

$$C = 0.01 \mu F$$

$$R = 15 \text{ k}\Omega$$

Type of phase diff?

$$\phi = 2 \tan^{-1} \left(2.5 \times 10^3 \times 0.01 \times 10^{-6} \times 15 \times 10^3 \right)$$

$$\phi = -134^\circ$$

One lecture missing



Digital to analog converters


Important characteristics :

1. Resolution
2. Maximum sampling Rate
3. Total harmonic distortion + noise
4. Dynamic range

1 Bit ADC \rightarrow

2 levels.

- can be made using comparator

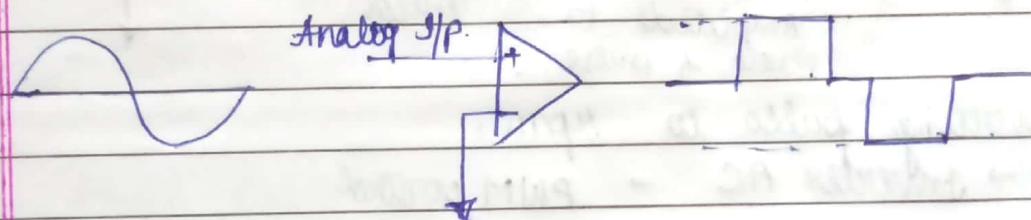

1 bit ADC \rightarrow 0, 1

2 bit ADC \rightarrow (0,0), (0,1), (1,0), (1,1)

\downarrow

v_1

\downarrow

v_2

\downarrow

v_3

\downarrow

v_4

App" of PCM \rightarrow

to convert any signal to .wav file.

PCM, 16 bits, 44.1KHz for CD audio.

DVD, Blue Ray \rightarrow 24 bits per sample.


O/p \rightarrow DAC.

I/P \rightarrow DAC

Telephone \rightarrow 300 Hz to 3 kHz
 fs for telephone \rightarrow 8 kHz.

Different types of DAC



1. L.P.F.

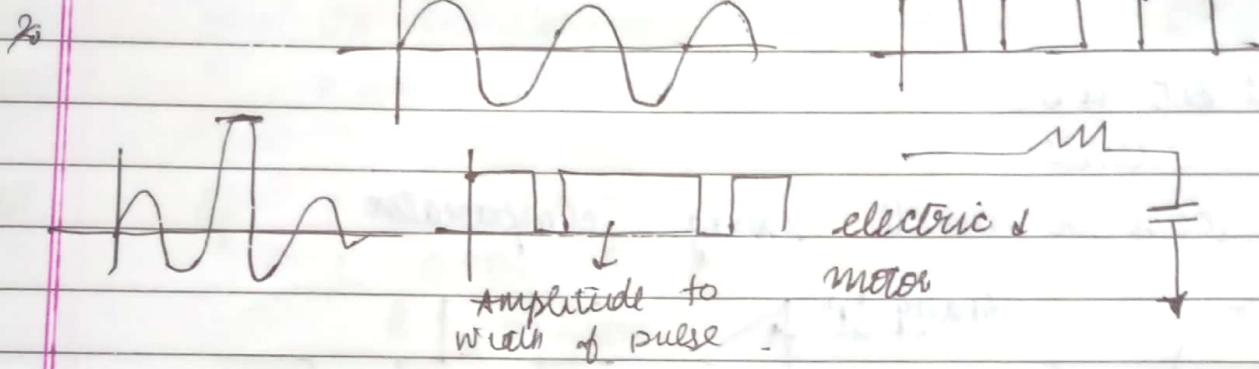

converting pulses to rpm.

App" \rightarrow inverter AC \rightarrow PWM control

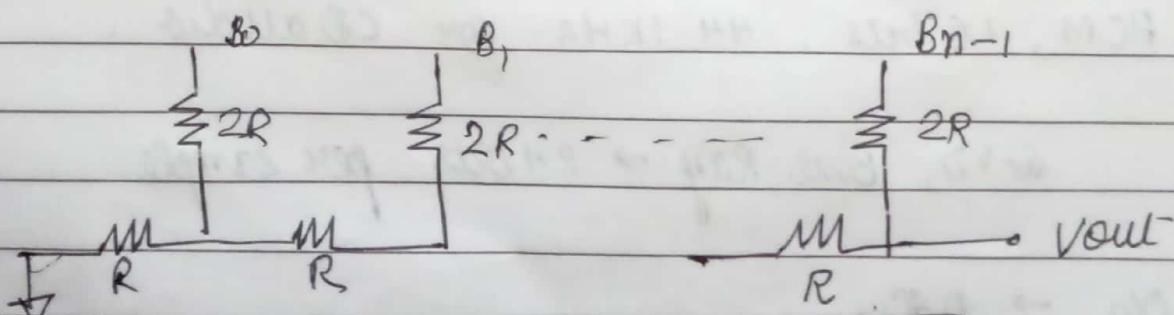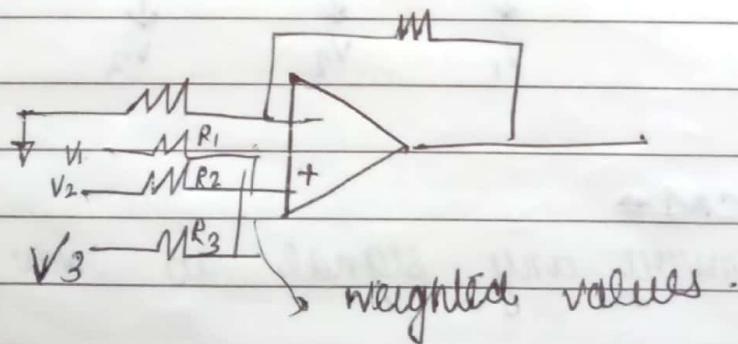2. Binary weighted DCA motors \rightarrow R2R ladder



$$V_{out} = \frac{V_{ref}}{2^N} \times \text{Bit value}$$

$N \rightarrow \text{no. of bits}$
 (resolution)



$V_{ref} = 3.3V$, 5-bit DAC.

00000 11111
0 31

$$V_{out} = 0$$


$$V_{out} = \frac{3.3 \times 81}{2^5} = 3.1969 V.$$

0 to 3.1969V \rightarrow Dynamic Range.


$$\text{Resolution} = \frac{3.1969}{2^5} = 0.10 V.$$

$$\text{Resolution} \approx \frac{V_{ref}}{2^N} = \frac{3.3}{2^5} \text{ (Approximate)}$$

cyclic DAC

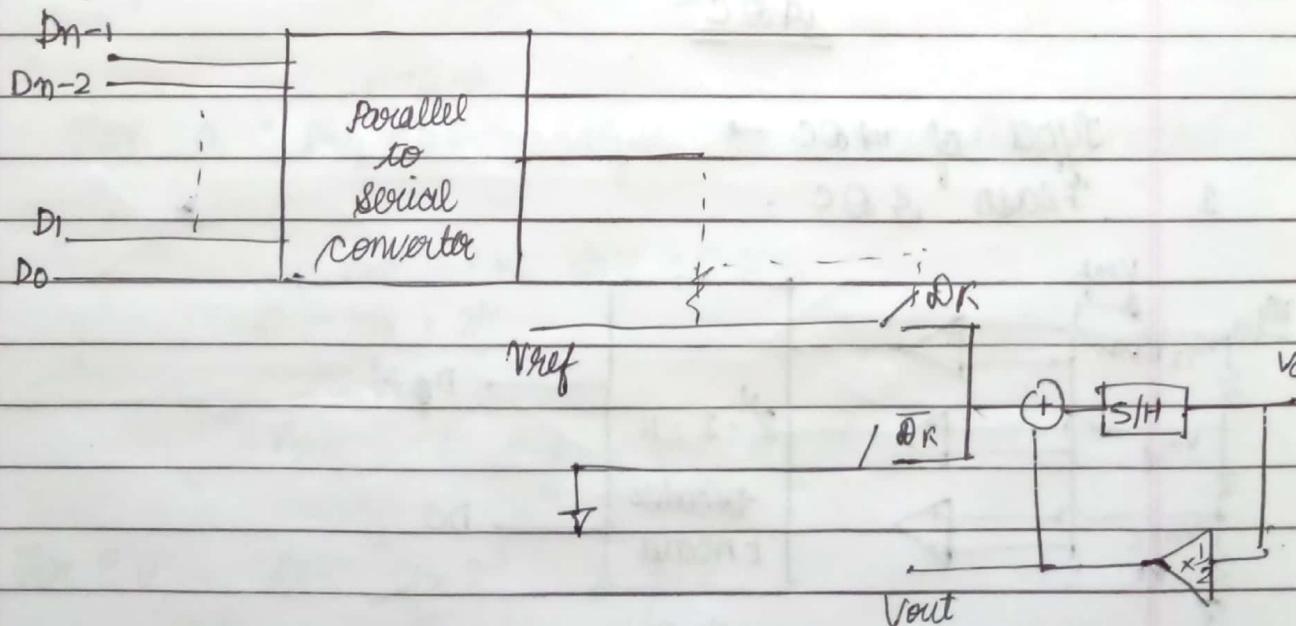

simple sample & hold ckt \rightarrow

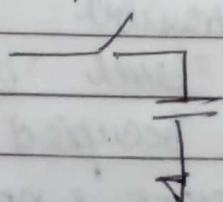



Ques Find o/p voltage at end of each cycle for a 4 bit cyclic DAC.

$$D = 1101 \quad V_{ref} = 5V$$

$$V_{out} = V_{ref} \times \frac{\text{Bit word}}{2^N} = \frac{5 \times 13}{2^4}$$


$$= 4.0625V$$

clock cycle	D _{N-1}	V _{out[initial]}	V _{out}
1	1		$\frac{1}{2}[1 \times 5 + 0] = 2.5V$
2	0		$\frac{1}{2}[0 \times 5 + 2.5] = 1.25V$
3	1		$\frac{1}{2}[1 \times 5 + 1.25] = 3.125$
4	1		$\frac{1}{2}[1 \times 5 + 3.125] = 4.0625V$

ADC

Types of ADC →

1. Flash ADC

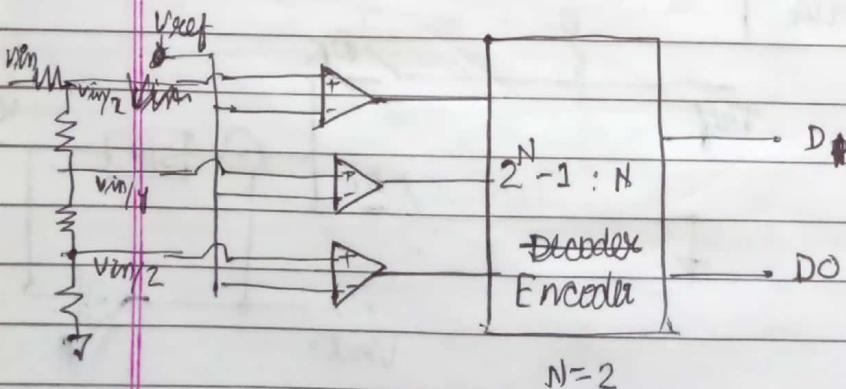

2 Bit Flash ADC


Fastest ADC possible

But for each level 2 resistors are needed

60 to 70% space occupied by resistor

Not space efficient & not power efficient

2. Pipeline ADC

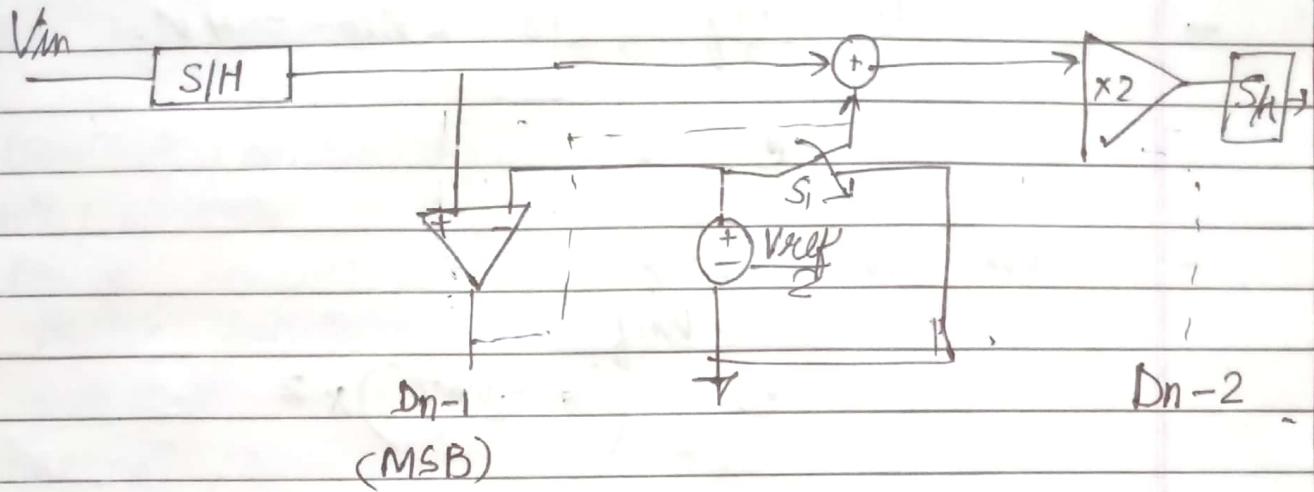

If $V_{in} < \frac{V_{ref}}{2}$, S_1 closed. O/P = $2V_{in}$.

If $V_{in} > \frac{V_{ref}}{2}$ $\left(\frac{V - V_{ref}}{2}\right) \times 2$

pipeline

Ques For a 3 bit ADC, analyse the conversion process

$$V_{in} = 2V, V_{ref} = 5V$$

$$D = \frac{V_{in} \times 2^N}{V_{ref}}$$

$$V_{out} = \frac{V_{ref} \times \text{bit word}}{2^N}$$

$$\text{For } 2V, D = \frac{2 \times 2^3}{5} = 3.2$$

011

$$\begin{array}{rcl}
 4V & \rightarrow & \frac{4 \times 8}{5} = 6.4 \\
 & & \downarrow \\
 5V & \rightarrow & 8 \quad \leftarrow \text{Quantization error}
 \end{array}$$

$$V_{in} = 2V \quad V_{ref} = 5V$$

$$V_{in} < \frac{V_{ref}}{2}, \quad V_o = 2V_{in} = 4V.$$

$$\Phi_2 = 0$$

$$V_{in} = 4V \quad V_{ref}$$

$$V_{in} > V_{ref}$$

$$V_o = \left(V_{in} - \frac{V_{ref}}{2} \right) \times 2$$

$$= (4 - 2.5) \times 2 = 3V$$


$$\Phi_1 = 1$$

$$V_{in} 3V$$

$$\Phi_0 = 1$$

-ve feedback

sigma Delta ADC ($\Sigma\Delta$)

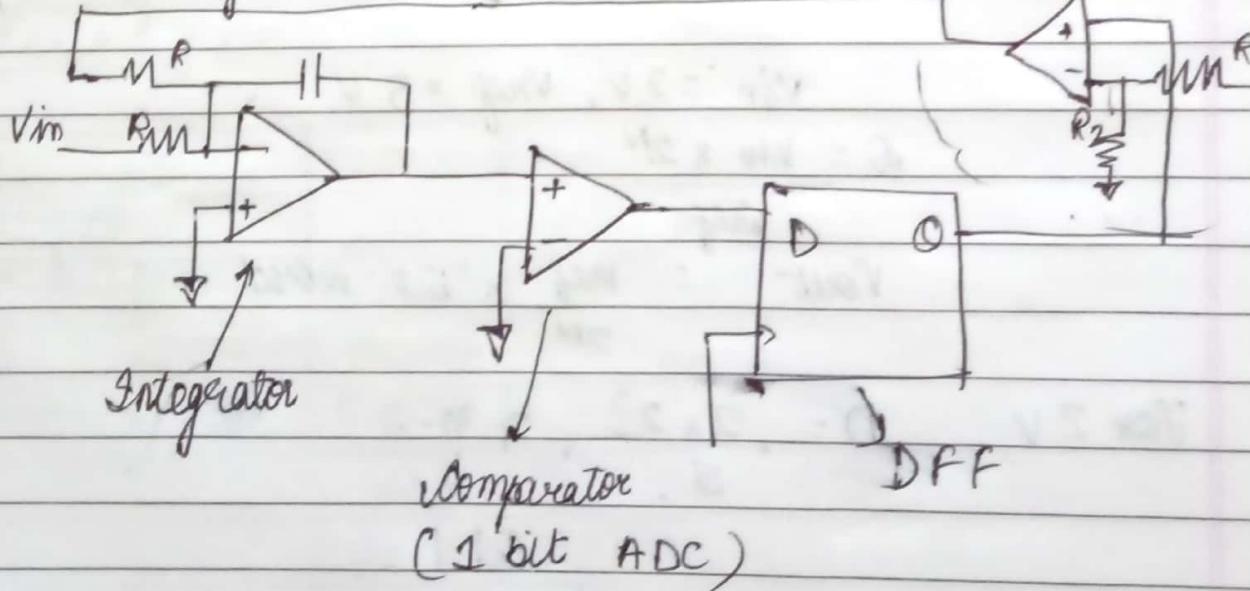

5/9/19



Semiconductor Device characterization

some key parameters

1. Resistivity / conductivity
2. Hole / electron density / mobility
3. Doping concentration / profile
4. Miller Orientation
5. Dielectric quality / thickness
6. thickness / resistivity / conductivity of thin sheets


┌── metal
 └── polymer
 └── Poly Si



Book: Schroeder: 3Ed. ch-1

Resistivity

why?

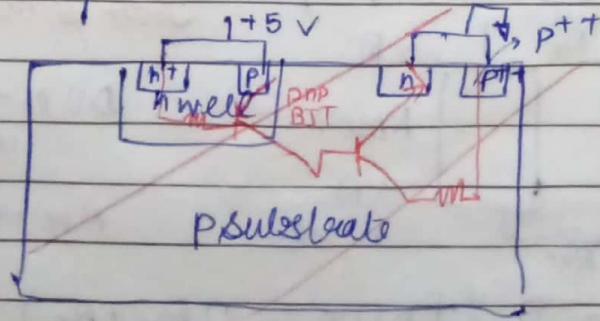1. series resistance
2. capacitance $\rightarrow C = \frac{\epsilon A}{d}$ wet \Rightarrow more permittivity
dry \Rightarrow less permittivity
3. Threshold voltage
4. hot carrier degradation
carrier carrying
high kinetic energy
 ∇ resistivity $\uparrow \Rightarrow$ $\text{KE} \downarrow \Rightarrow$ hot carrier deg. \downarrow
5. latch up in CMOS.




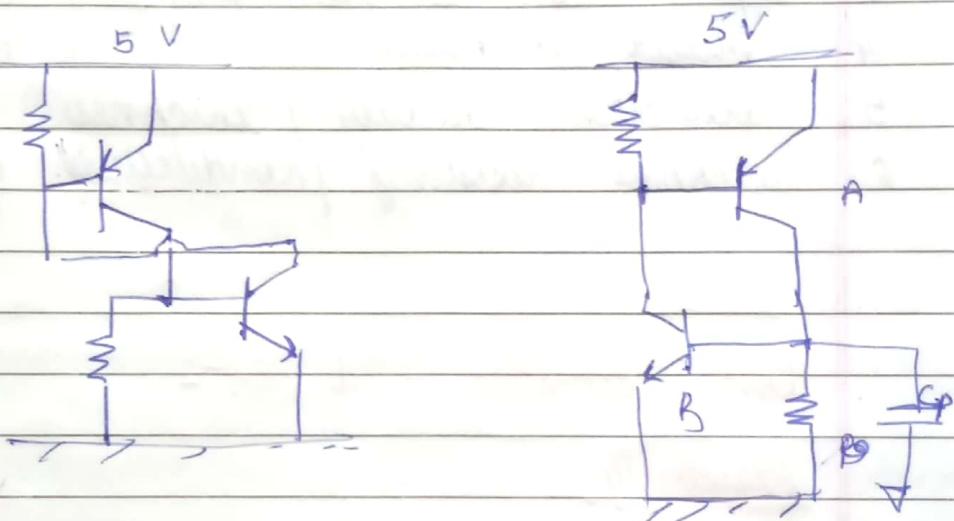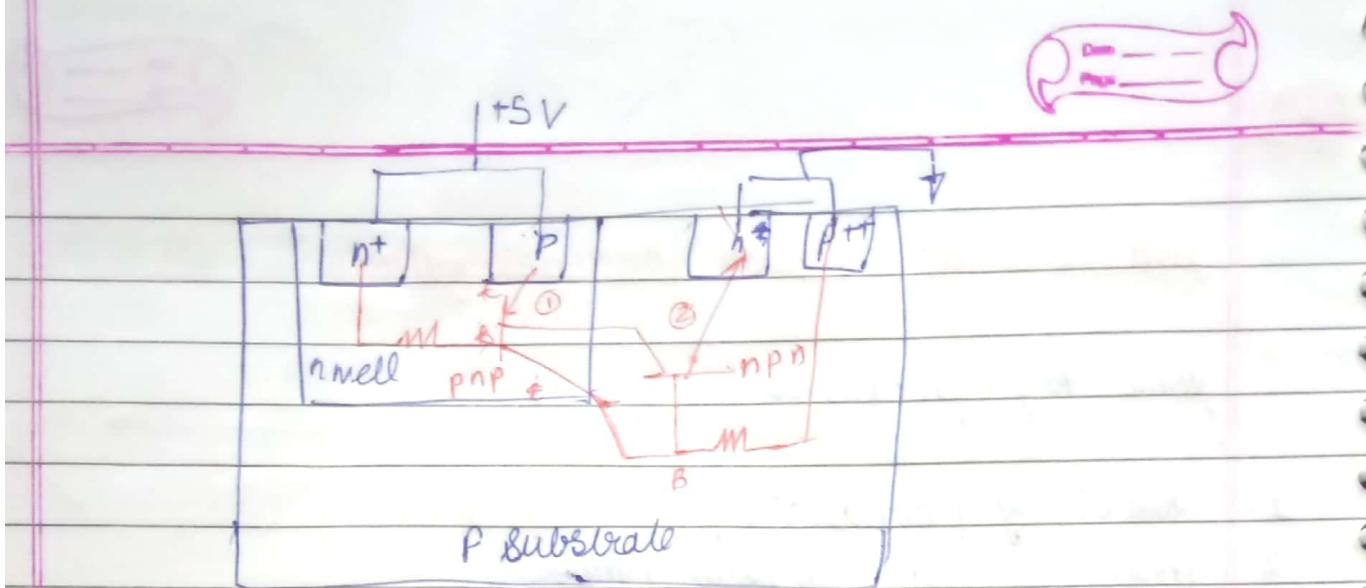

Initially both A & B are off then C_p gets charged $\Rightarrow A$ is on now. Then B is ON.

If resistivity is high \Rightarrow gain of that stage is high
 \Rightarrow Problem of latch up arises.
 Reduce resistivity to solve problem of latch up.

$$P = \frac{1}{q(n\mu_m + p\mu_p)}$$

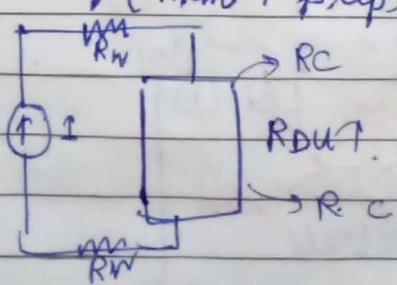


Two probe measurement

DUT \rightarrow Device under testing

R_W \rightarrow Resistance of wire

$$V = I (R_{DUT} + 2R_W + R_C)$$

4 probe measurement (Kelvin's Probe)

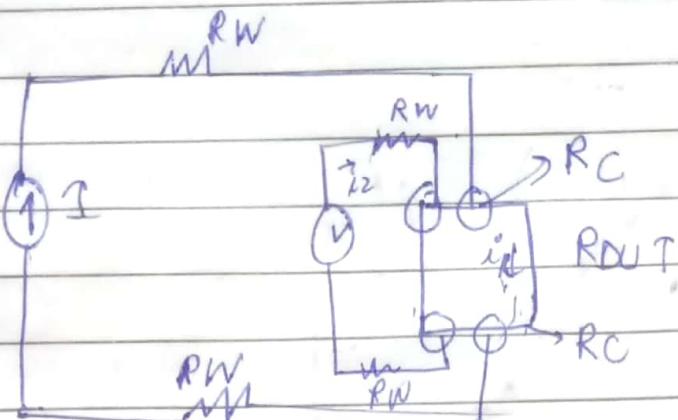


$$V = I(R_{DUT} + 2R_W + 2R_C)$$

$$V_{AB} = i_1 R_{DUT} + i_2 (R_{DUT} + 2R_W + 2R_C)$$

$$V_{AB} \approx i_1 R_{DUT} \quad \text{as } i_2 \text{ is negligible}$$

single probe

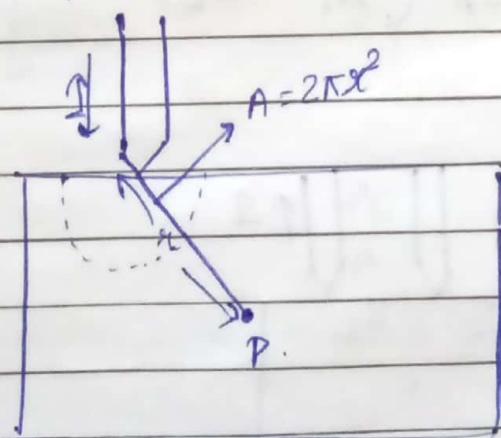

vector Ohm's law

$$\vec{E} = \rho \vec{J} = -\frac{dV}{dx}$$

$$J = \frac{I}{2\pi x^2} \cdot A / \text{cm}^2$$


$$V_p = \int_{\infty}^x \frac{dV}{\rho} = - \int_{\infty}^x J \rho dx$$

$$-V_p = -J \rho x$$

$$- \frac{\pi I}{2\pi} \int_0^x \frac{1}{x^2} dx$$

$$V_p = \frac{I_p}{2\pi r}$$

Two probe

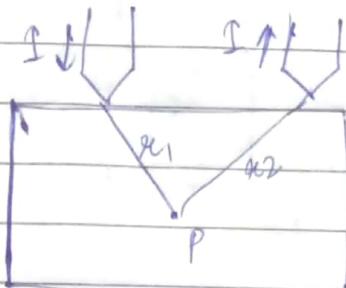


$$V_1 = \frac{I_p}{2\pi r_1}$$

$$V_2 = -\frac{I_p}{2\pi r_2}$$

$$V_t = \frac{I_p}{2\pi} \left(\frac{1}{r_1} - \frac{1}{r_2} \right)$$

Four probe

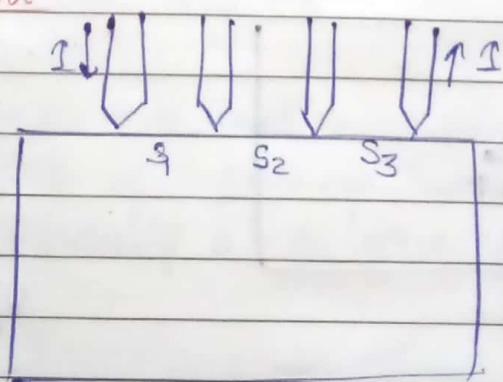

$$V_1 = \frac{I_p}{2\pi} \left(\frac{1}{S_1} - \frac{1}{S_2 + S_3} \right)$$

$$V_2 = \frac{I_p}{2\pi} \left(\frac{1}{S_1 + S_2} - \frac{1}{S_3} \right)$$

$$V_t = \frac{I_p}{2\pi} \left(\frac{1}{S_1} - \frac{1}{S_2 + S_3} - \frac{1}{S_1 + S_2} + \frac{1}{S_3} \right)$$

$$y \quad S = S_1 = S_2 = S_3$$


$$V_{12} = \frac{I P}{2 \pi s}$$

$$\boxed{P = \frac{V}{I} \times 2 \pi s}$$

$$\boxed{P = \frac{F V}{I} 2 \pi s}$$

Ideally $F = 1$
 $F \rightarrow$ correction parameter

Sheet Resistance

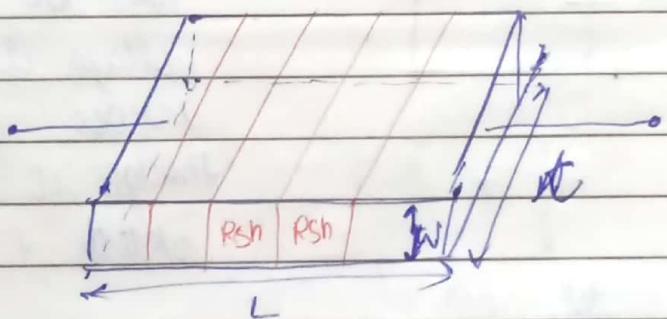


$$R = \frac{PL}{A} = \frac{PL}{wt} = \left(\frac{P}{t} \right) \left(\frac{L}{w} \right)$$

$$\boxed{\frac{P}{t}} \rightarrow R_{sh} \text{ (sheet resistance)} \quad \Omega/\square$$

$$5 \text{ blocks} \rightarrow R = 5 R_{sh}$$



12/09/19

$$T = J_0 e^{qV}$$

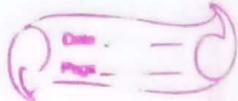

Semiconductor characterisation (Series Resistance Measurement)

IV characteristics of diode →

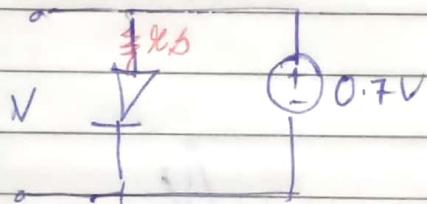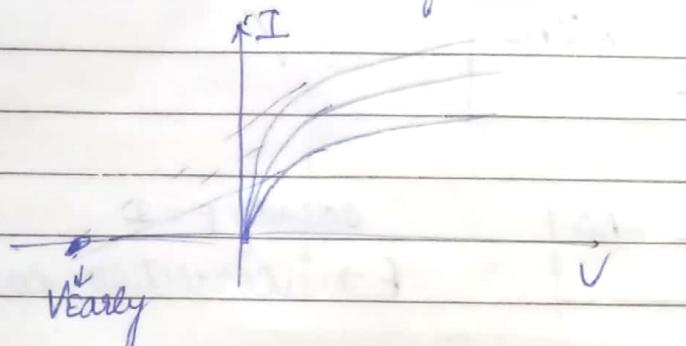


$r_s = \Delta I / \Delta V$
 $r_s \rightarrow$ series resistance


Bcz of r_s , there will be some voltage drop across diode, even though it is short circuited.

$$I = I_0 (e^{\frac{qV}{kT}} - 1)$$

→ Ideality factor .

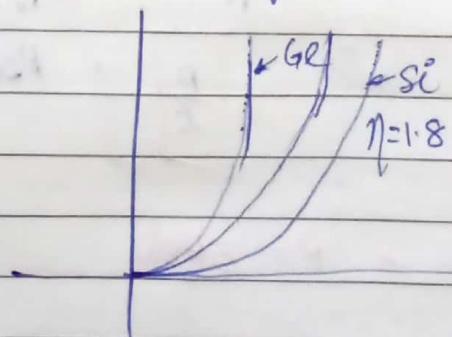

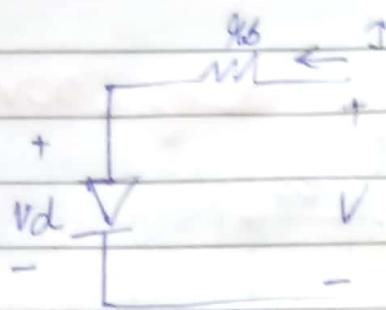$\eta \rightarrow$ to scale IV characteristics of diod



$V_d \rightarrow$ Barriär Potential
für $\delta t \rightarrow 0.7$.

$$V = Vd + T_{965}$$

$$V_{BL} = V - I_{BL} \cdot g(V - I_{BL})$$

$$I = I_0 \left(e^{-\frac{q}{kT}} - 1 \right)$$

$$T = \csc(\theta) + i \sin(\theta)$$

space charge
region
current


Quasi neutral
(Neutral but dynamic)



Space Charge region

Quasi


Neutral

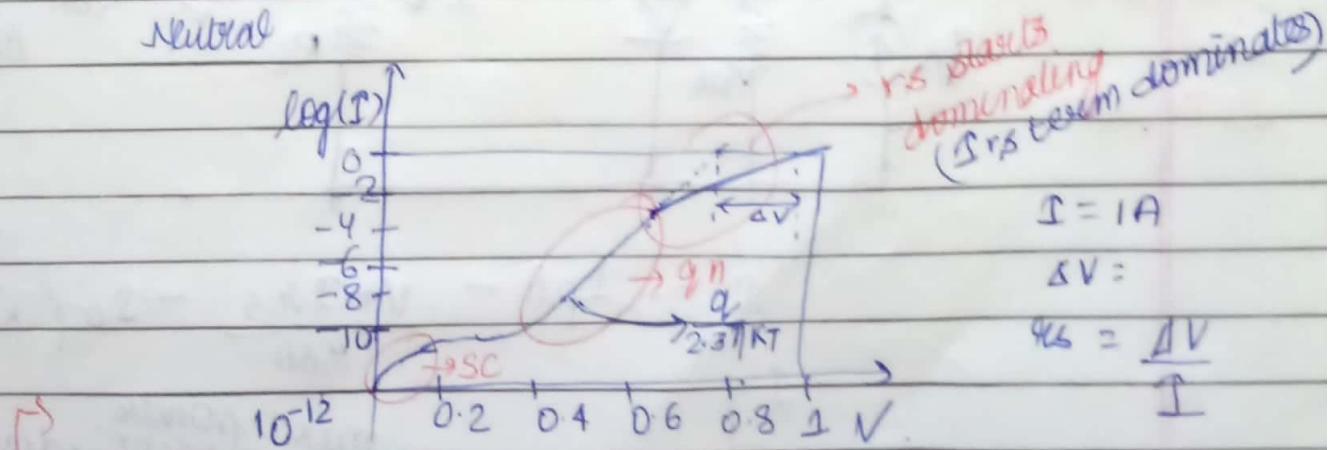

Method 1: I-V characterisation



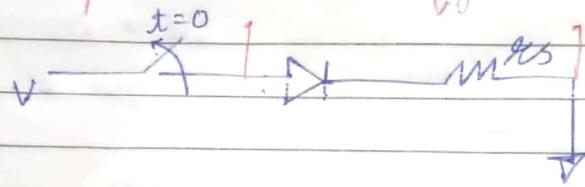Method 2: open circuit voltage delay (OCVD).




For $t < 0$, switch was closed till steady state.

$$\rightarrow V(0^-) = V_d + I_{RS} \cdot R_s$$

For time $t > 0$,

$$V(0^+) = V_d$$

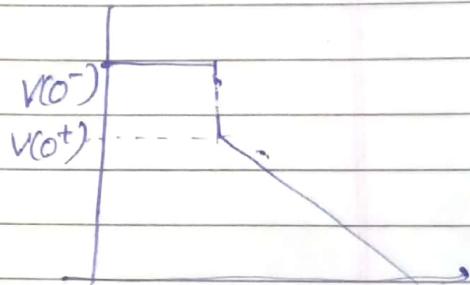


$$V(0^-) = V(0^+) + I_{RS} \cdot R_s$$


$$e_{oc} = V(0^-) - V(0^+)$$

Solar Cell

Equivalent
circuit of
Solar Cell

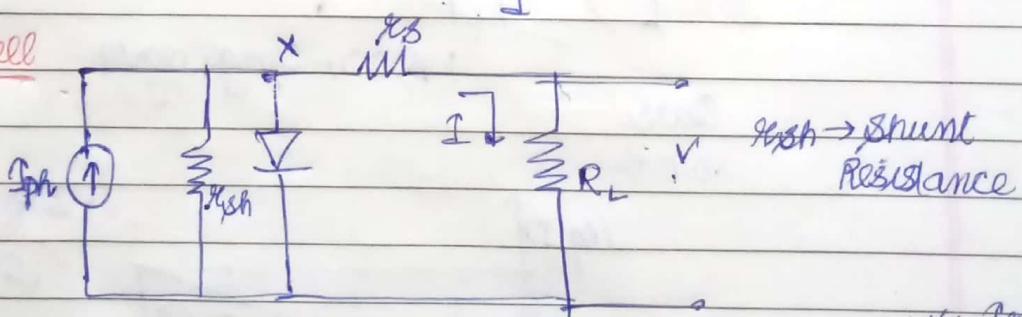

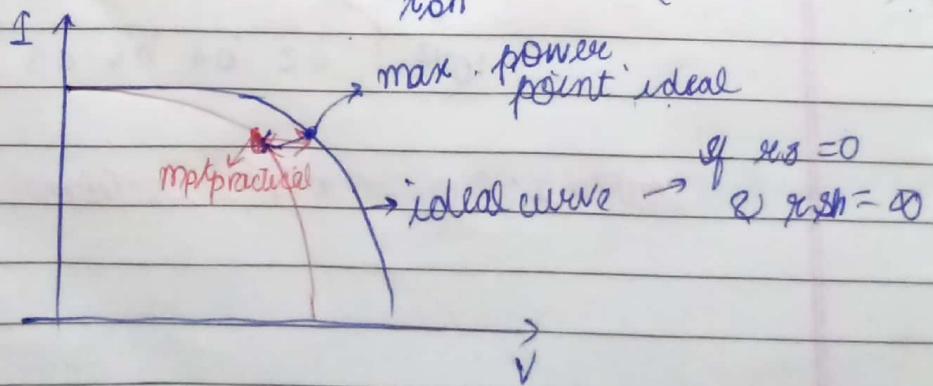
$$I = I_{ph} - \frac{V + I_{RS}}{R_{sh}} - I_0 (e^{\frac{V + I_{RS}}{R_{sh} T}} - 1)$$





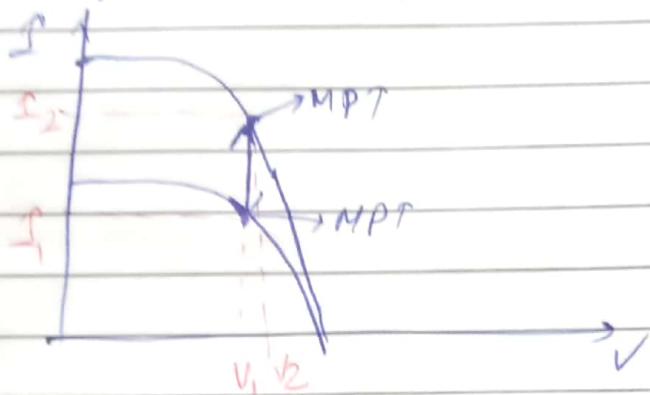To measure η_s for solar cell \rightarrow
perform experiment twice
with different light intensities



$$\frac{\Delta V}{\Delta I} = \frac{V_2 - V_1}{I_2 - I_1} = 96\text{V}$$

solar cell is a $p-n$ junction.